

## Understanding the operational impedances

### Important questions

- Why we need to introduce them?
- How their values are determined?

### The main purpose is

To have an easier way to solve analytically the d, q-axes voltage equations (involving the flux linkage equations).

The convenience offered by the 'easier way' is obtained by neglecting the rotor currents.

## Example – q-axis equations

Original equations (lecture 5, slide 12, for a generator)

$$\begin{aligned} u_q &= -Ri_q + p\lambda_q + \omega_r\lambda_d & \lambda_q &= -L_{ls}i_q + L_{mq}\left(-i_q + i'_{kq}\right) \\ u_d &= -Ri_d + p\lambda_d - \omega_r\lambda_q & \lambda_d &= -L_{ls}i_d + L_{md}\left(-i_d + i'_{fd} + i'_{kd}\right) \end{aligned}$$

It will be easier to solve the equations if e.g.  $\lambda_q$  is only related to  $i_q$  only.

This requires to get rid of  $i'_{kq}$  ... by using the rotor side voltage equation:

$$0 = u'_{kq} = R'_{kq}i'_{kq} + p\lambda'_{kq} \quad \lambda'_{kq} = L'_{lkq}i'_{kq} + L_{mq}\left(-i_q + i'_{kq}\right)$$

## What we do is to introduce an equivalent circuit

$$0 = u'_{kq} = R'_{kq} i'_{kq} + p \lambda'_{kq}$$




$$0 = \frac{u'_{kq}}{p} = \frac{R'_{kq}}{p} i'_{kq} + \lambda'_{kq}$$

$$\lambda_q = -L_{ls} i_q + L_{mq} (-i_q + i'_{kq})$$


$$\lambda'_{kq} = L'_{lkq} i'_{kq} + L_{mq} (-i_q + i'_{kq})$$

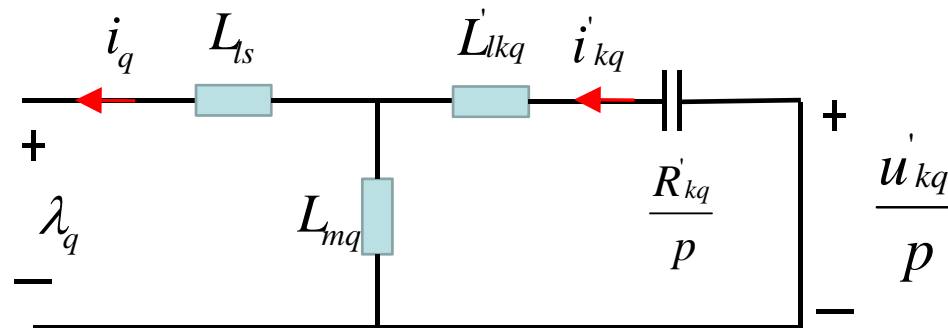Imaging the flux linkage is 'voltage' and inductance is the 'resistance', the equivalent electrical circuit can be obtained as


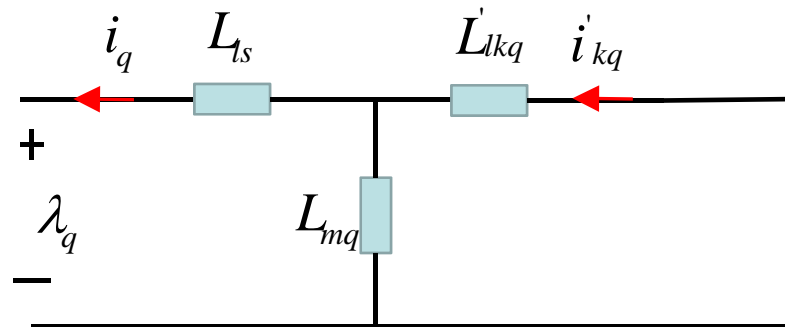
## Therefore we find the equivalent inductance

Under the assumption that the q-axis damping winding resistance is neglected, we have



The equivalent inductance of this circuit becomes

$$L_{ls} + \frac{L'_{lkq}L_{mq}}{L'_{lkq} + L_{mq}} \xrightarrow{\text{Multiplied by } \omega_e, \text{ we obtain}} X_{ls} + \frac{X'_{lkq}X_{mq}}{X'_{lkq} + X_{mq}}$$

Known as the **transient reactance**.

The relation between  $\lambda_q$  and  $i_q$  is now simply determined by this inductance.

## Similar idea for the sub-transient reactance

This corresponds to the situation that if you add one more damping winding on the q-axis and the equivalent input reactance will be the sub-transient reactance.

Note – the damping winding resistances are always neglected.

Similar idea may be applied for the d-axis.