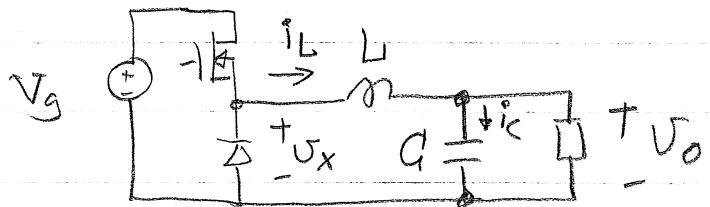


- AVERAGE MODEL } BUCK
 - STEADY STATE } BOOST

7

- ## • Transformer


- IDEAL
 - PERFECT




CAPITAL LETTERS \Rightarrow CONSTANT
SMALL LETTERS \Rightarrow DYNAMIC
(DC)

How will $U_x(t)$ look like?

$$Q_i = ON$$

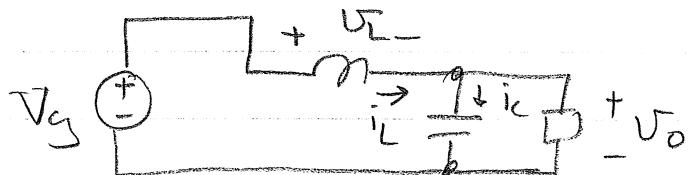


D=ON (Q=OFF)

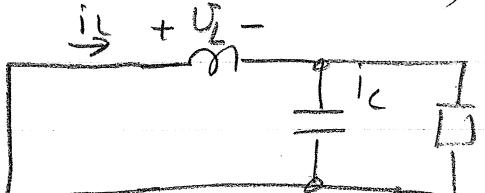

$$V_J = V_L = V_0 = 0$$

$$\langle \nabla g \rangle_B = \langle U_\theta \rangle_{T_S}$$

$$-V_L - U_0 = 0$$

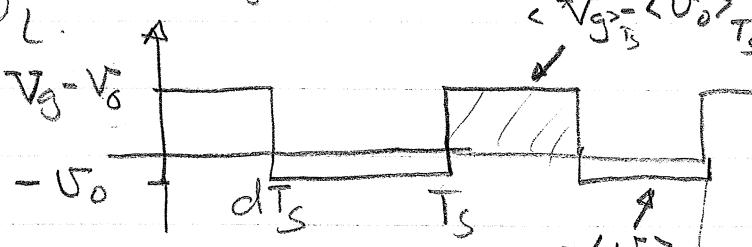

$$\langle U_L \rangle = L \frac{d \langle i_L \rangle}{dt}_{T_S}$$

$$\langle V_L \rangle_{T_S} = \frac{1}{T_S} \int_{-\infty}^{T_S} V_L dt$$

$$\langle V_L \rangle_{T_S} = \frac{1}{T_S} \int_{T_S}^{T_{sd}} \langle V_g \rangle_{T_S} - \langle V_0 \rangle_{T_S} dt$$

$$+ \frac{1}{T_S} \int_{T_S d}^{T_S^0} - \langle v_0 \rangle_{T_S} dt$$

27

$$\begin{aligned}\langle v_L \rangle_{TS} &= \langle v_g \rangle_{TS} d - \langle v_o \rangle_{TS} d \\ &= \langle v_o \rangle_{TS} (1-d) \\ &= \langle v_o \rangle_{TS} + \langle v_o \rangle_{TS} d\end{aligned}$$

$$\langle v_L \rangle_{TS} = \langle v_g \rangle_{TS} d - \langle v_o \rangle_{TS}$$

DYNAMIC EQUATION

SINCE $\langle v_L \rangle_{TS} = L \frac{d \langle i_L \rangle}{dt}$

$$L \frac{d \langle i_L \rangle_{TS}}{dt} = \langle v_g \rangle_{TS} d - \langle v_o \rangle_{TS}$$

IN STEADY STATE

WHAT HAPPENS WITH


$$\frac{d \langle i_L \rangle}{dt} ?$$

$$0 = k_1 V_g D - V_o$$

$$V_o = V_g D$$

TRANSFORMER

3/

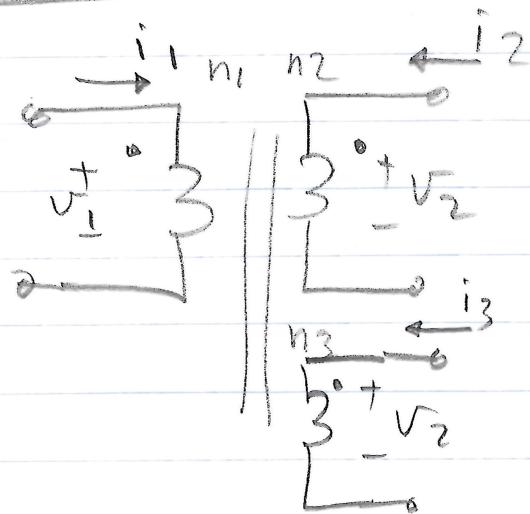

$$\frac{V_1}{n_1} = \frac{V_2}{n_2} = \frac{V_3}{n_3} \dots \dots \dots$$


$$i_1 n_1 + i_2 n_2 + i_3 n_3 \dots = 0$$

WHY DO YOU THINK IT IS
NAMED IDEAL?

$$V_1 = \frac{n_1}{n_2} V_2$$

$$i_1 \frac{n_1}{n_2} = -i_2$$

$$1 \cdot 10 = -10$$

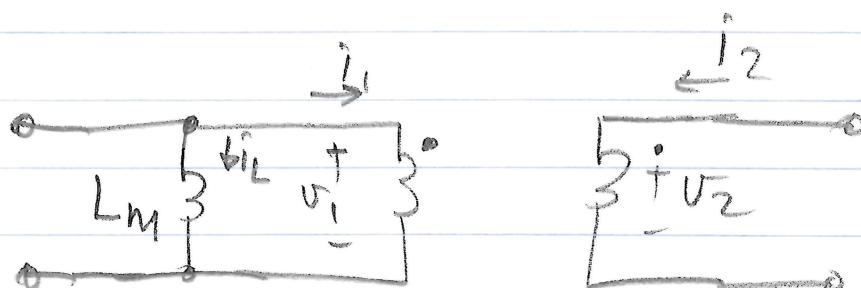



PERFECT
TRANSFORMER

V_1 and V_2 now MUST HAVE
AVERAGE VOLTAGES EQUAL TO ZERO




4)

TRANSFORMER BASED CONVERTER

FORWARD.

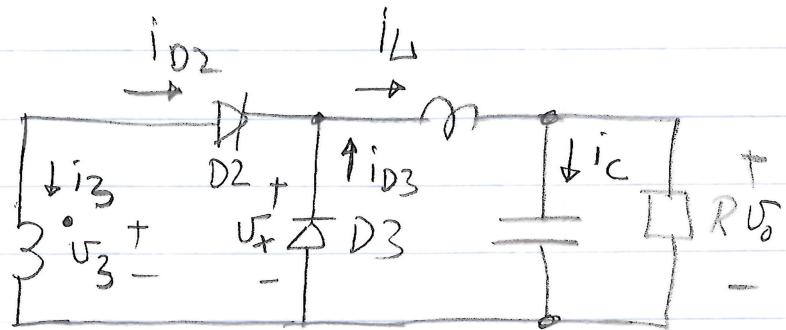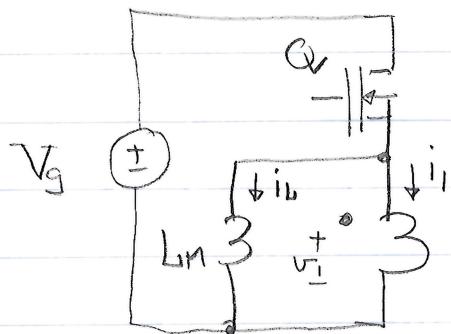


$Q = ON$

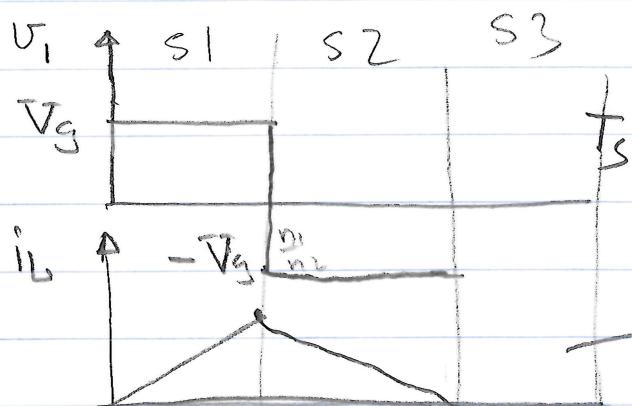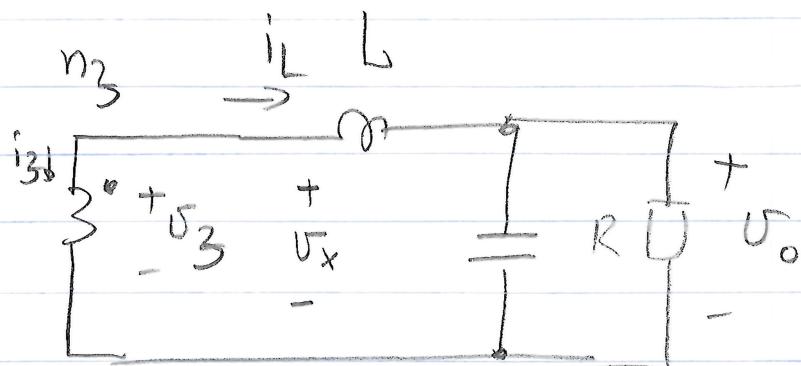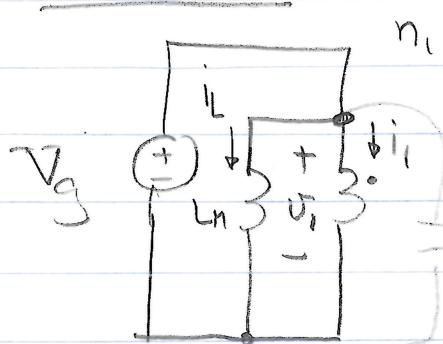

DCM

$$\frac{n_1}{n_1} \frac{n_3}{n_3} \frac{n_3}{n_1}$$

$$V_2 = \frac{n_3}{n_1} V_1$$

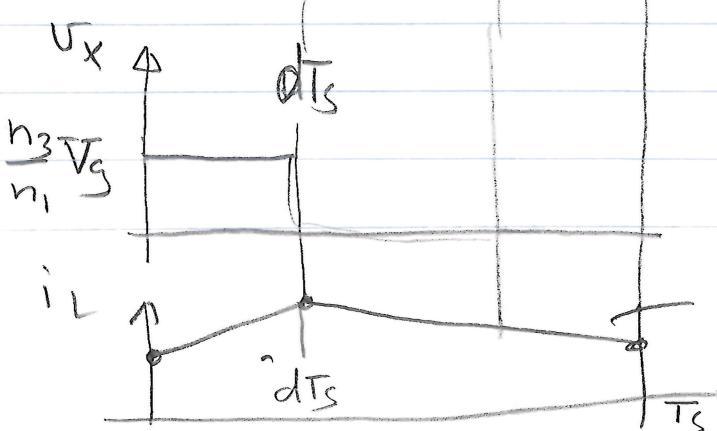

CCM


$$V_3 = \frac{n_3}{n_1} V_g$$

$Q = OFF$

WHAT HAPPENS NOW?



V_1 decrease USE SMALL CAPACITOR
try to become negative.

BUT if V_x NEGATIVE D_3 TURN ON

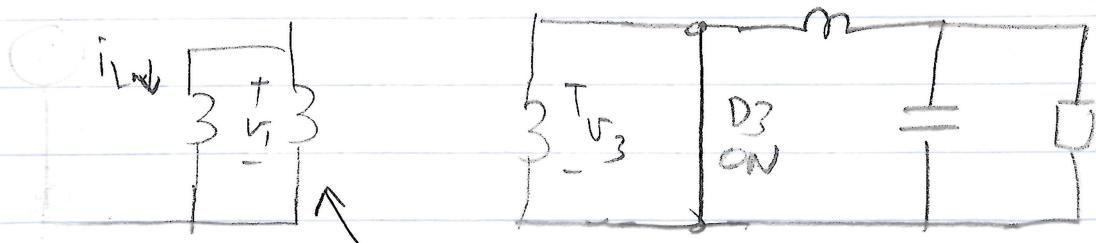

$\underline{V_1 = 0}$ SO NO DEMAGNITIS
= AT ON!

with D_2

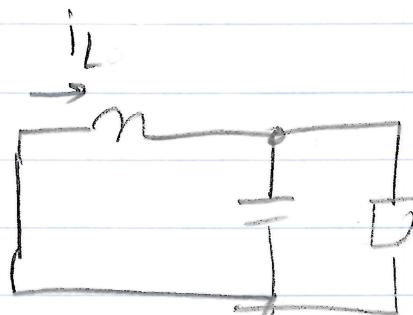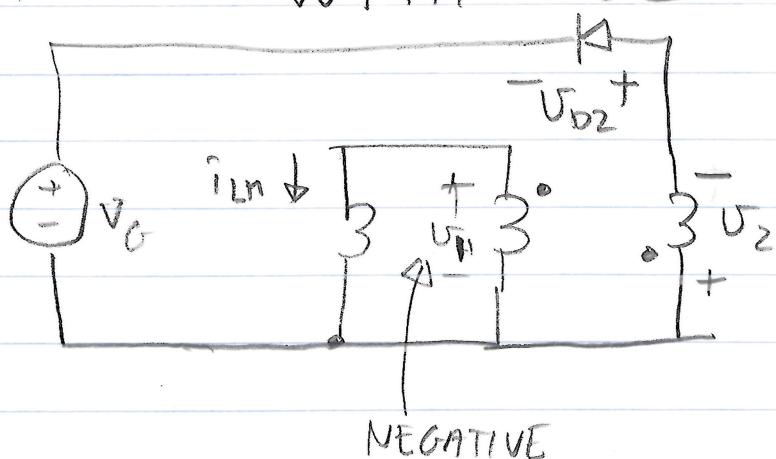

$$\frac{V_1}{n_1} = \frac{V_2}{n_2} \Rightarrow V_2 = \frac{n_2}{n_1} V_1$$

$$V_G + V_{D2} + V_2 = 0$$

$$V_1 = -V_G \frac{n_1}{n_2}$$


$$V_{D2} = -V_G - \frac{n_2}{n_1} V_1 = 0 \Rightarrow n_1 = n_2$$

$$V_1 = -V_G$$

S3:


D2 = OFF , Q_v = OFF , D3 = ON

6/

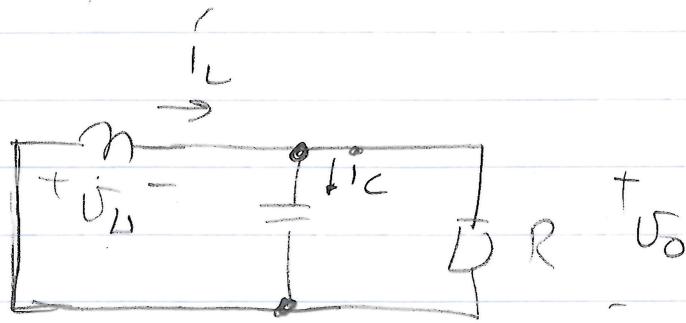

7

FBY BACK

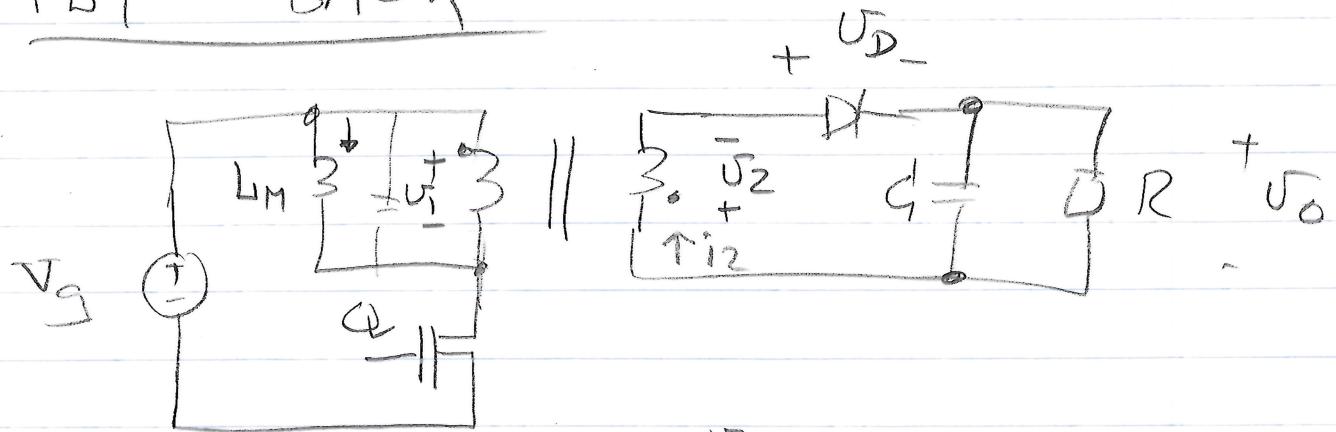

$$Q = 0 \text{ n}$$

$$\frac{V_1}{n_1} = \frac{V_2}{n_2}$$

$$V_2 = V_1 \frac{n_2}{n_1}$$

SEC:


$$-V_2 - V_0 - V_o = 0$$

$$V_o = -V_2 - V_0$$

$$\text{AT } \underline{V_0 = 0}$$

$$\underline{V_2 = -V_0}$$

$$\boxed{V_1 = \frac{n_1}{n_2} (-V_0)}$$

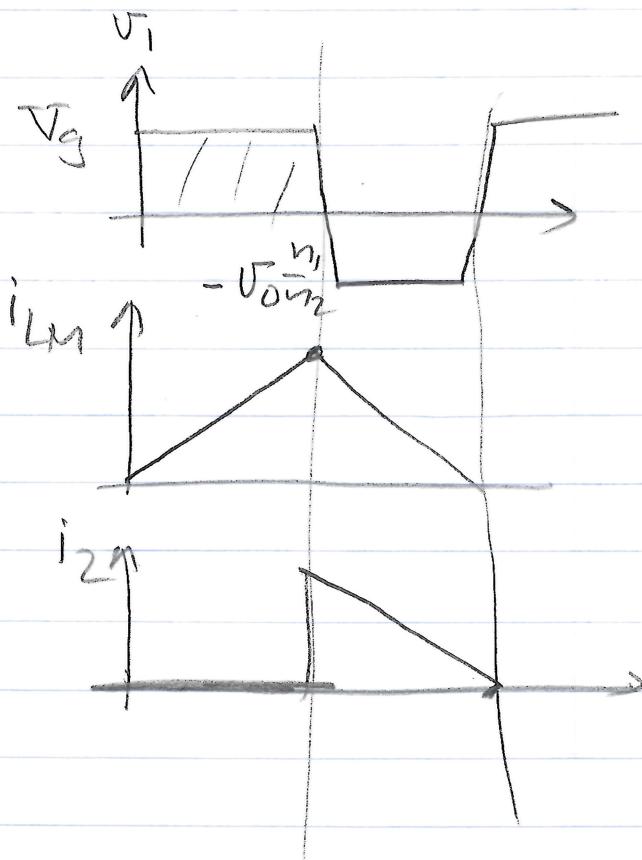

$$V_g dI_g = V_o \frac{n_1}{n_2} (1 - D)$$

$$\underline{V_o = \frac{n_2}{n_1} V_g \frac{D}{1-D}}$$

$$\underline{V_o = n V_g \frac{D}{1-D}}$$