
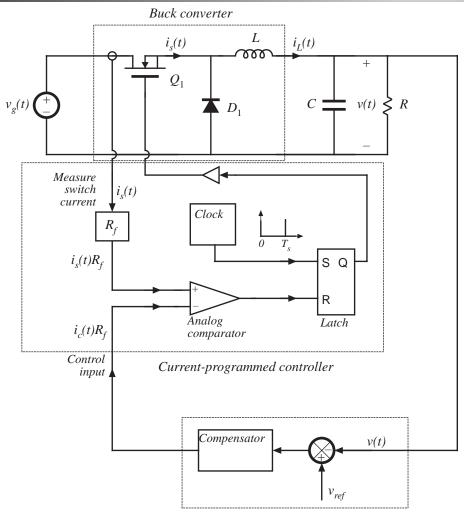
### Chapter 11 Current Programmed Control



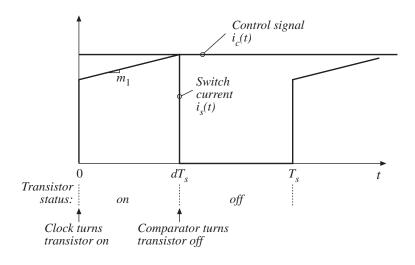The peak transistor current replaces the duty cycle as the converter control input.



Conventional output voltage controller

Chapter 11: Current Programmed Control

### Current programmed control vs. duty cycle control

#### Advantages of current programmed control:

- Simpler dynamics —inductor pole is moved to high frequency
- Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
- It is always necessary to sense the transistor current, to protect against overcurrent failures. We may as well use the information during normal operation, to obtain better control
- Transistor failures due to excessive current can be prevented simply by limiting  $i_c(t)$
- Transformer saturation problems in bridge or push-pull converters can be mitigated

A disadvantage: susceptibility to noise


### 11.1 Oscillation for D > 0.5

- The current programmed controller is inherently unstable for D > 0.5, regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp

#### Objectives of this section:

- Stability analysis
- Describe artificial ramp scheme

### Inductor current waveform, CCM

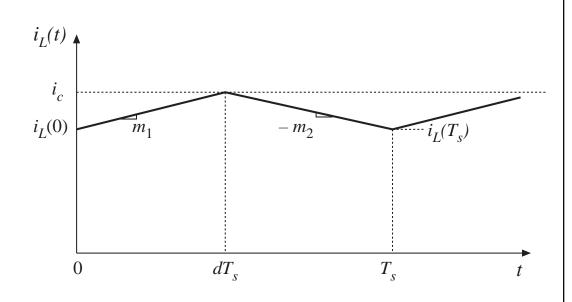

Inductor current slopes  $m_1$  and  $-m_2$ 

buck converter

$$m_1 = \frac{v_g - v}{L} - m_2 = -\frac{v}{L}$$

boost converter

$$m_1 = \frac{v_g}{L} \qquad -m_2 = \frac{v_g - v}{L}$$

buck-boost converter

$$m_1 = \frac{v_g}{L} \qquad -m_2 = \frac{v}{L}$$

### Steady-state inductor current waveform, CPM

#### First interval:


$$i_L(dT_s) = i_c = i_L(0) + m_1 dT_s$$

Solve for *d*:

$$d = \frac{i_c - i_L(0)}{m_1 T_s}$$

Second interval:

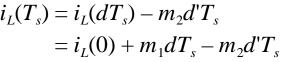
$$i_L(T_s) = i_L(dT_s) - m_2 d'T_s$$
  
=  $i_L(0) + m_1 dT_s - m_2 d'T_s$ 




In steady state:

$$0 = M_1 DT_s - M_2 D'T_s$$

$$\frac{M_2}{M_1} = \frac{D}{D'}$$

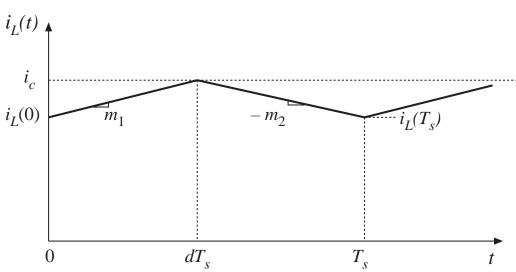


### Perturbed inductor current waveform

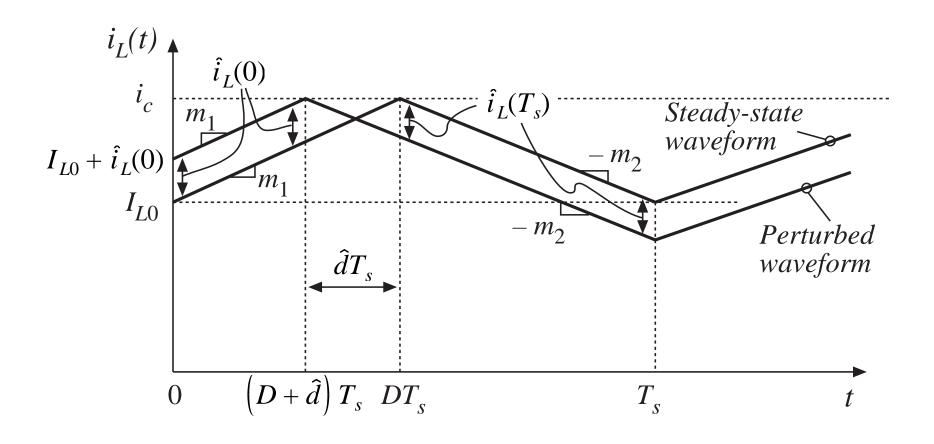

# Change in inductor current perturbation over one switching period

magnified view

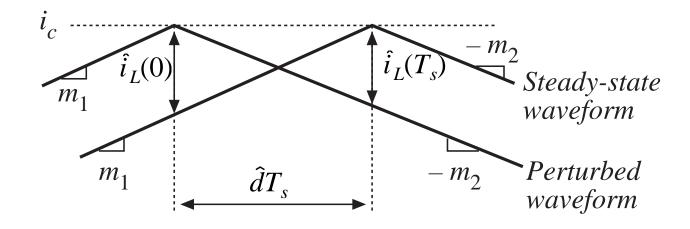

$$\hat{i}_L(0) = -m_1 \hat{d}T_s$$

$$\hat{i}_L(T_s) = m_2 \hat{d}T_s$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{D}{D'}\right)$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{m_2}{m_1}\right)$$

## Change in inductor current perturbation over many switching periods

$$\hat{i}_{L}(T_{s}) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)$$

$$\hat{i}_{L}(2T_{s}) = \hat{i}_{L}(T_{s}) \left(-\frac{D}{D'}\right) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)^{2}$$


$$\hat{i}_{L}(nT_{s}) = \hat{i}_{L}((n-1)T_{s}) \left(-\frac{D}{D'}\right) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)^{n}$$

$$\left|\hat{i}_{L}(nT_{s})\right| \rightarrow \begin{cases} 0 & \text{when } \left|-\frac{D}{D'}\right| < 1\\ \infty & \text{when } \left|-\frac{D}{D'}\right| > 1 \end{cases}$$

For stability: D < 0.5

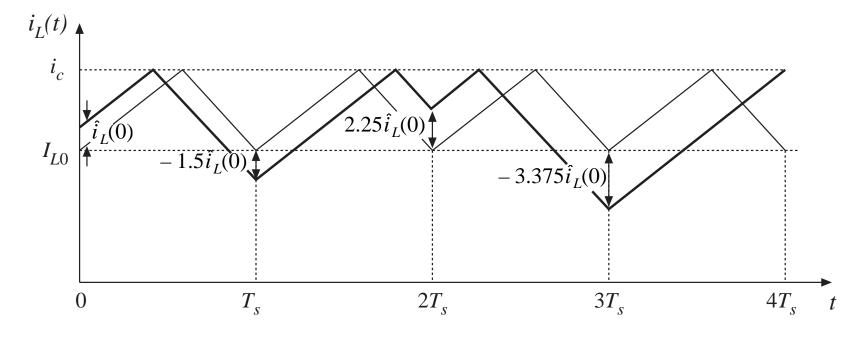
### Example: unstable operation for D = 0.6

$$\alpha = -\frac{D}{D'} = \left(-\frac{0.6}{0.4}\right) = -1.5$$




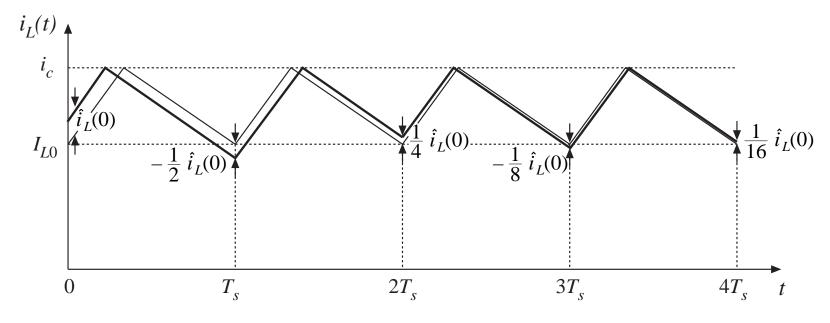
## Example: stable operation for D = 1/3

$$\alpha = -\frac{D}{D'} = \left(-\frac{1/3}{2/3}\right) = -0.5$$


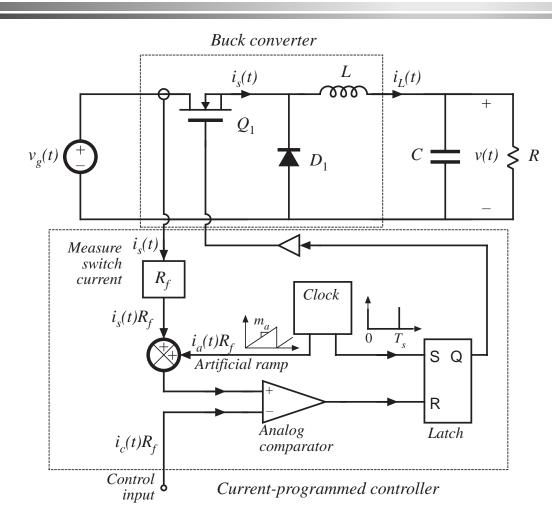
## Stabilization via addition of an artificial ramp to the measured switch current waveform



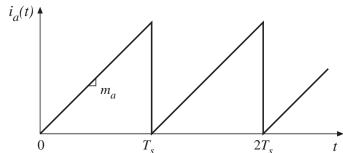

Now, transistor switches off when


$$i_a(dT_s) + i_L(dT_s) = i_c$$

or,


$$i_L(dT_s) = i_c - i_a(dT_s)$$

## Steady state waveforms with artificial ramp

$$i_L(dT_s) = i_c - i_a(dT_s)$$

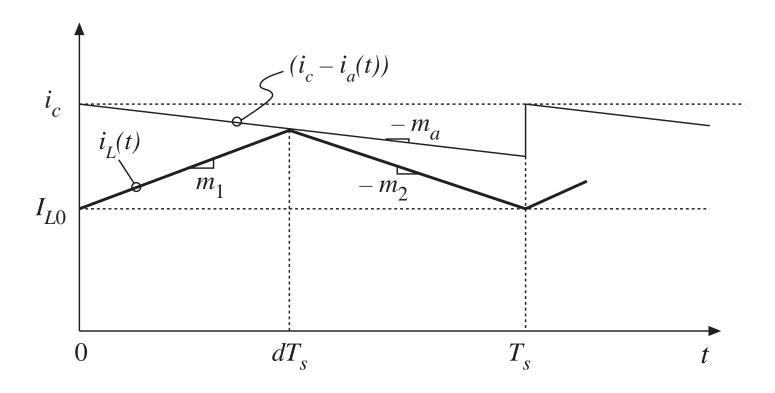
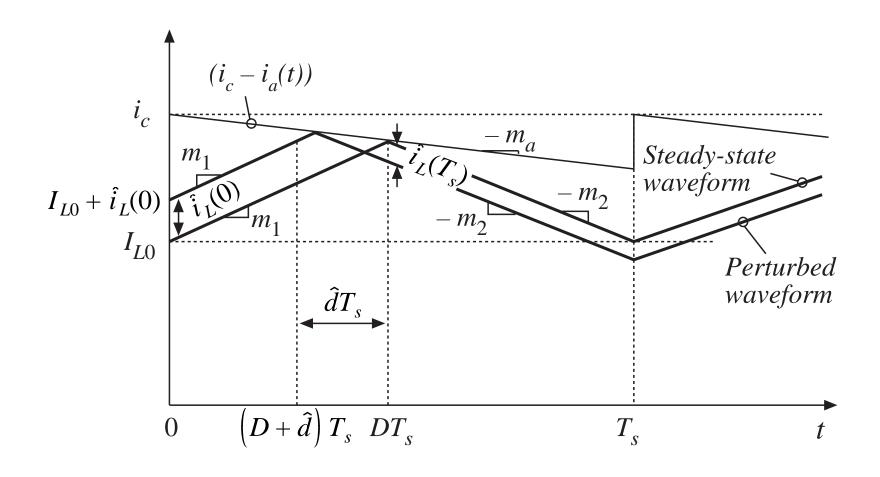
## Stability analysis: perturbed waveform



# Stability analysis: change in perturbation over complete switching periods

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s \left(m_1 + m_a\right)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s \left(m_a - m_2\right)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)$$

After *n* switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)^n = \hat{i}_L(0) \alpha^n$$

Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a} \qquad \left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$

### The characteristic value $\alpha$

$$\alpha = -\frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$

- For stability, require  $|\alpha| < 1$
- Buck and buck-boost converters:  $m_2 = -v/L$ So if v is well-regulated, then  $m_2$  is also well-regulated
- A common choice:  $m_a = 0.5 m_2$

This leads to  $\alpha = -1$  at D = 1, and  $|\alpha| < 1$  for  $0 \le D < 1$ .

The minimum  $\alpha$  that leads to stability for all D.

• Another common choice:  $m_a = m_2$ 

This leads to  $\alpha = 0$  for  $0 \le D < 1$ .

Deadbeat control, finite settling time