

COMMON-MODE BEHAVIOR OF SWITCH-MODE CONVERTERS

by Tamas Kerekes

Agenda


- DC-DC and DC-AC converters
- Differential-mode voltage and current
- Common-mode voltage and current
- PWM of switch-mode converters
- DC-DC converter applications
- DC-AC converter applications
- Exercise

Converter types

- DC-DC converters:
 - Buck, boost, buck-boost, forward, push-pull, ...
- DC-AC (AC-DC) converters
 - Half-bridge
 - H-bridge
 - Full-bridge
 - Multilevel
 - ...

What is differential mode

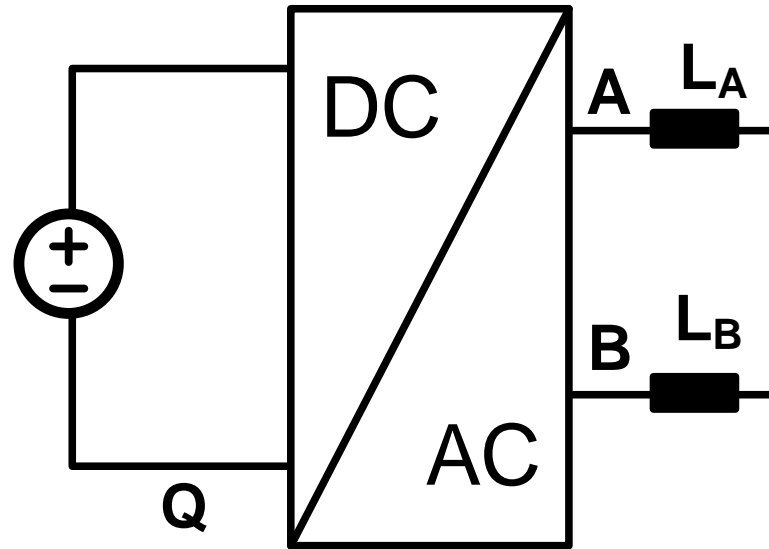- Differential mode voltage is the potential difference between two terminals
- **line to line voltage** is a differential mode voltage
- **phase voltage** is also a differential mode voltage
- Differential mode current is the current flowing due to the differential mode voltage



Differential mode

- Voltage

$$V_{dm-AB} = V_{AQ} - V_{BQ} = V_{AB}$$

- Current

What is common mode

- Common-mode voltage is the potential that is common to both terminals
- Can be a constant voltage (constant DC offset)
- Can be a changing in time (PWM or AC offset)
- Common-mode current is the current flowing due to the common-mode voltage


Common-mode

- Voltage

$$V_{cm-AB} = \frac{V_{AQ} + V_{BQ}}{2}$$


- Current

Switching states

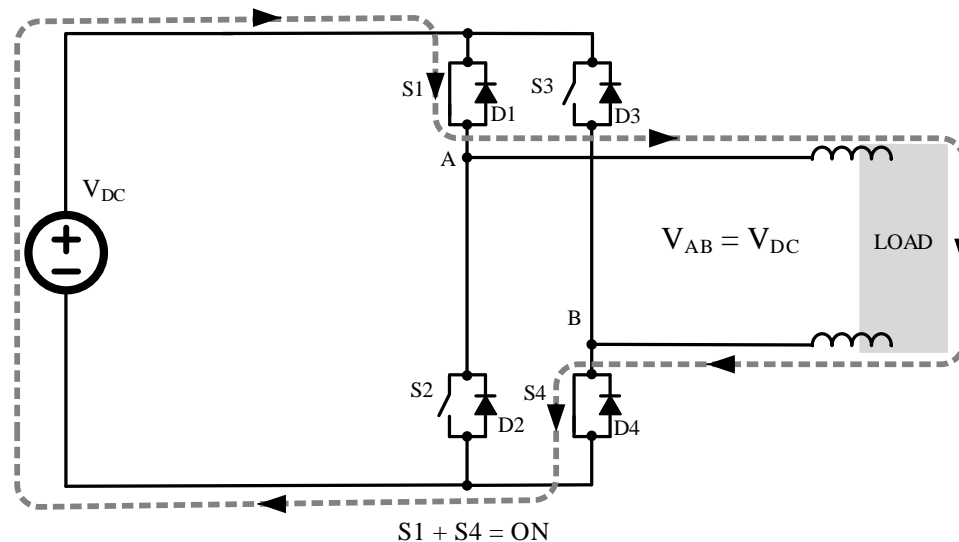




$S1 + S4$ and $S2 + S3$ are switched complementary at high frequency.

Switching states

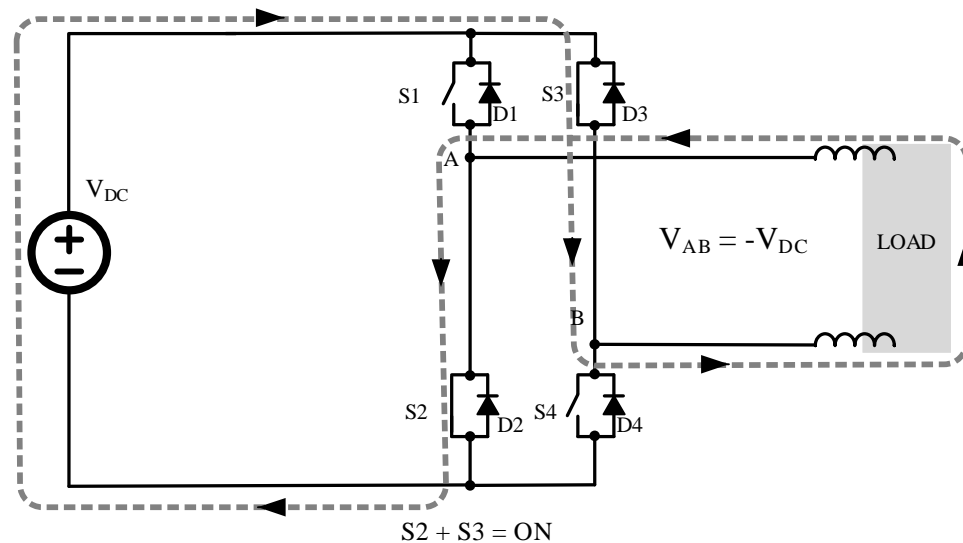


$S1 + S4$ and $S2 + S3$ are switched complementary at high frequency.

Common mode modelling

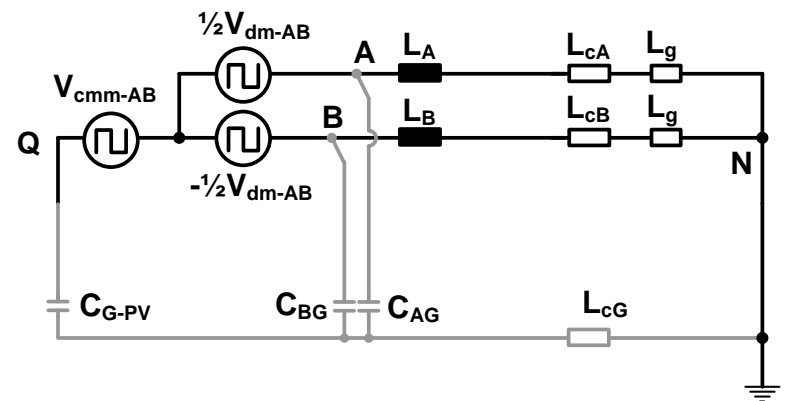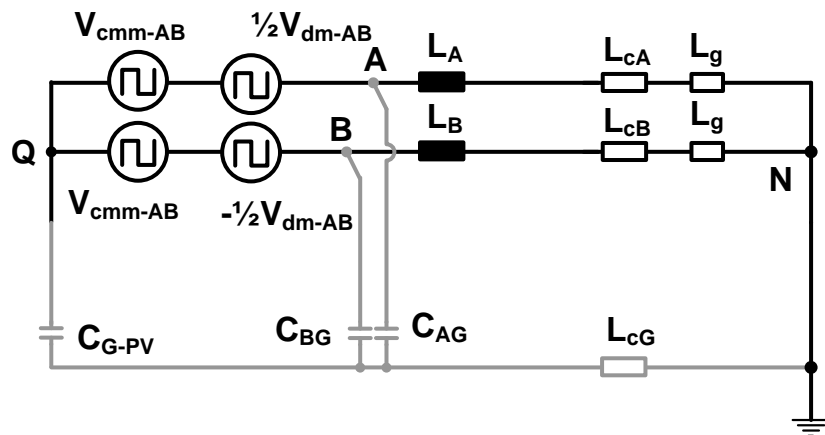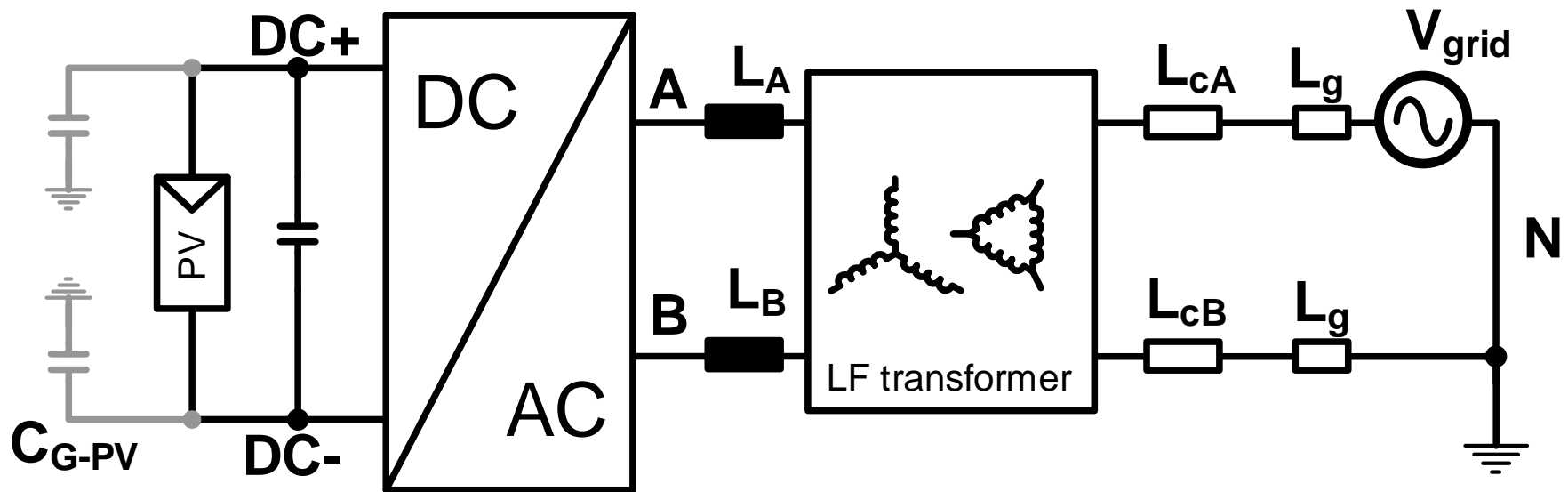

Common-mode behavior


DC-DC converter

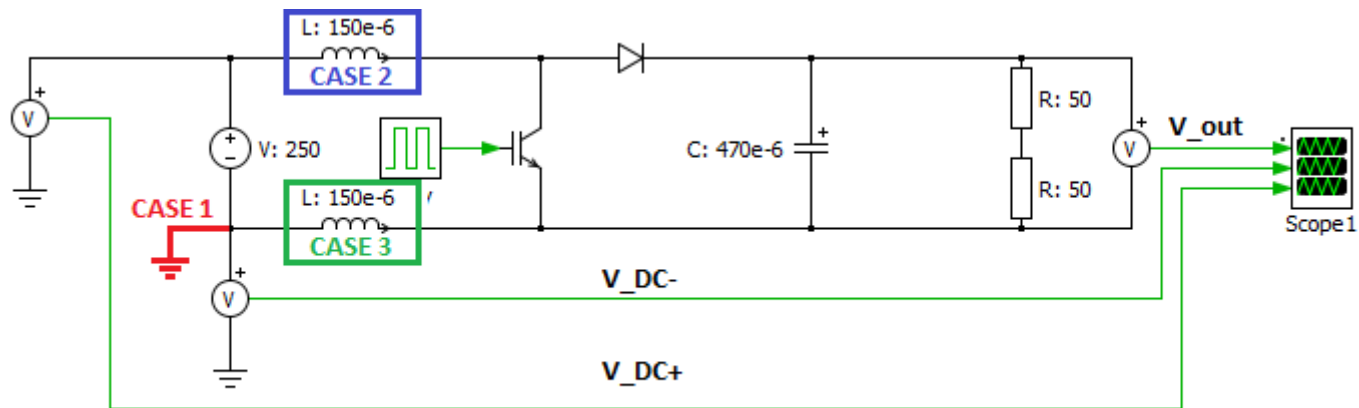

Common-mode behavior


DC-DC converter

DC- grounded

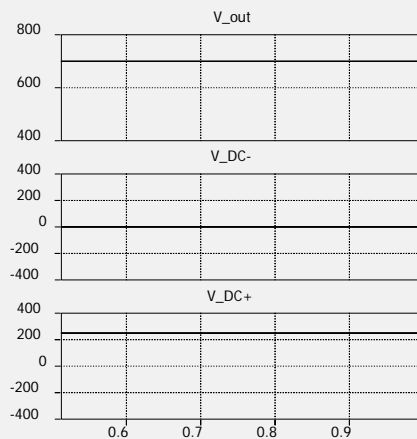


CASE 1

No ground
inductor on DC+

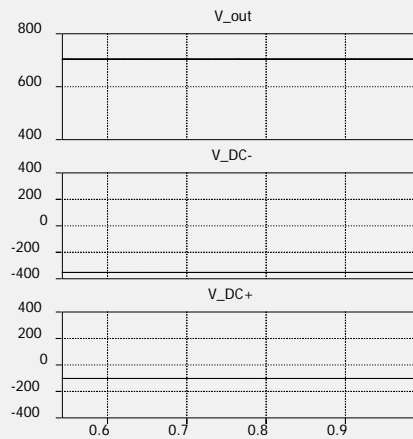

CASE 2


No ground
inductor on DC-

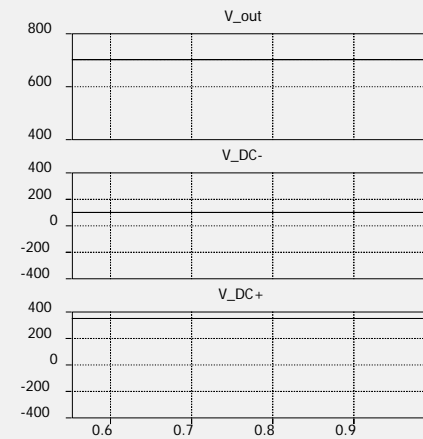



CASE 1

Common-mode behavior

- DC-AC converter

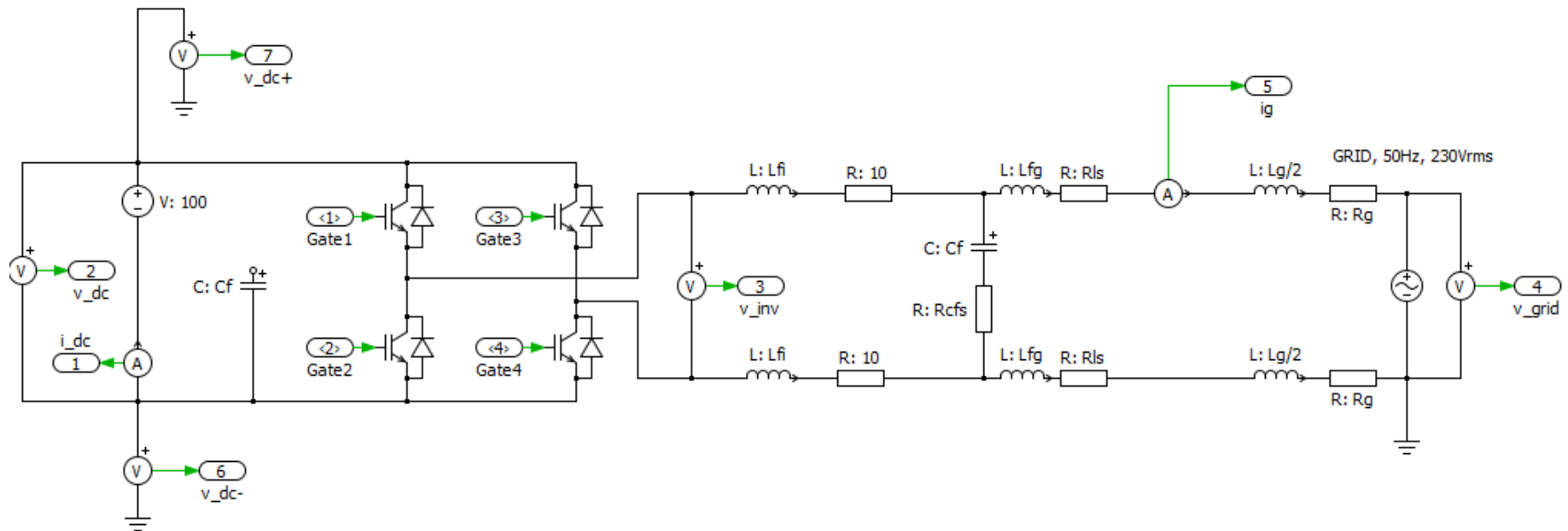


Bipolar PWM

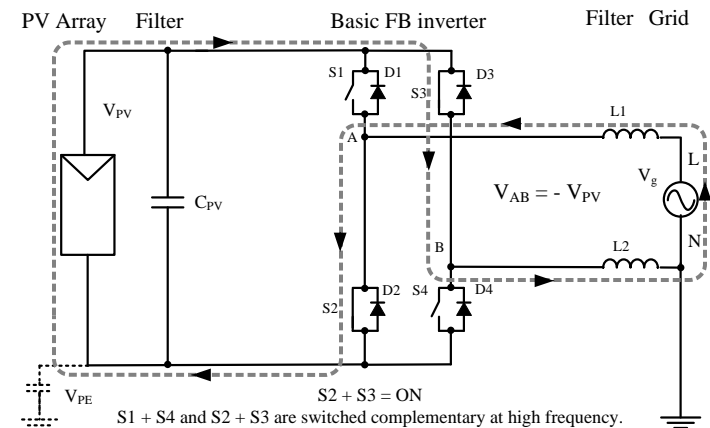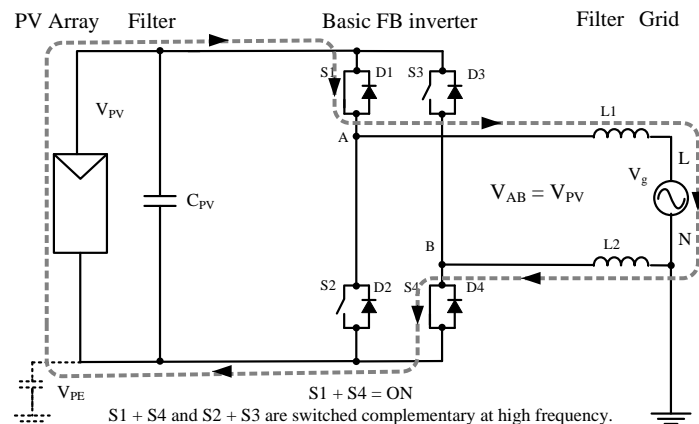

- S1 + S4 and S2 + S3 are switched complementary at high frequency (PWM)
- No 0 output voltage possible
- The switching ripple in the current equals $\frac{1}{x}$ switching frequency \rightarrow large filtering
- Voltage across filter is bipolar \rightarrow high core losses
- No common mode voltage $\rightarrow V_{PE}$ free for high frequency \rightarrow low leakage current
- Reactive power exchange $L_1(2) \leftrightarrow C_{PV}$ during freewheeling and that 2 devices are simultaneously switched every switching period

FB Unipolar PWM

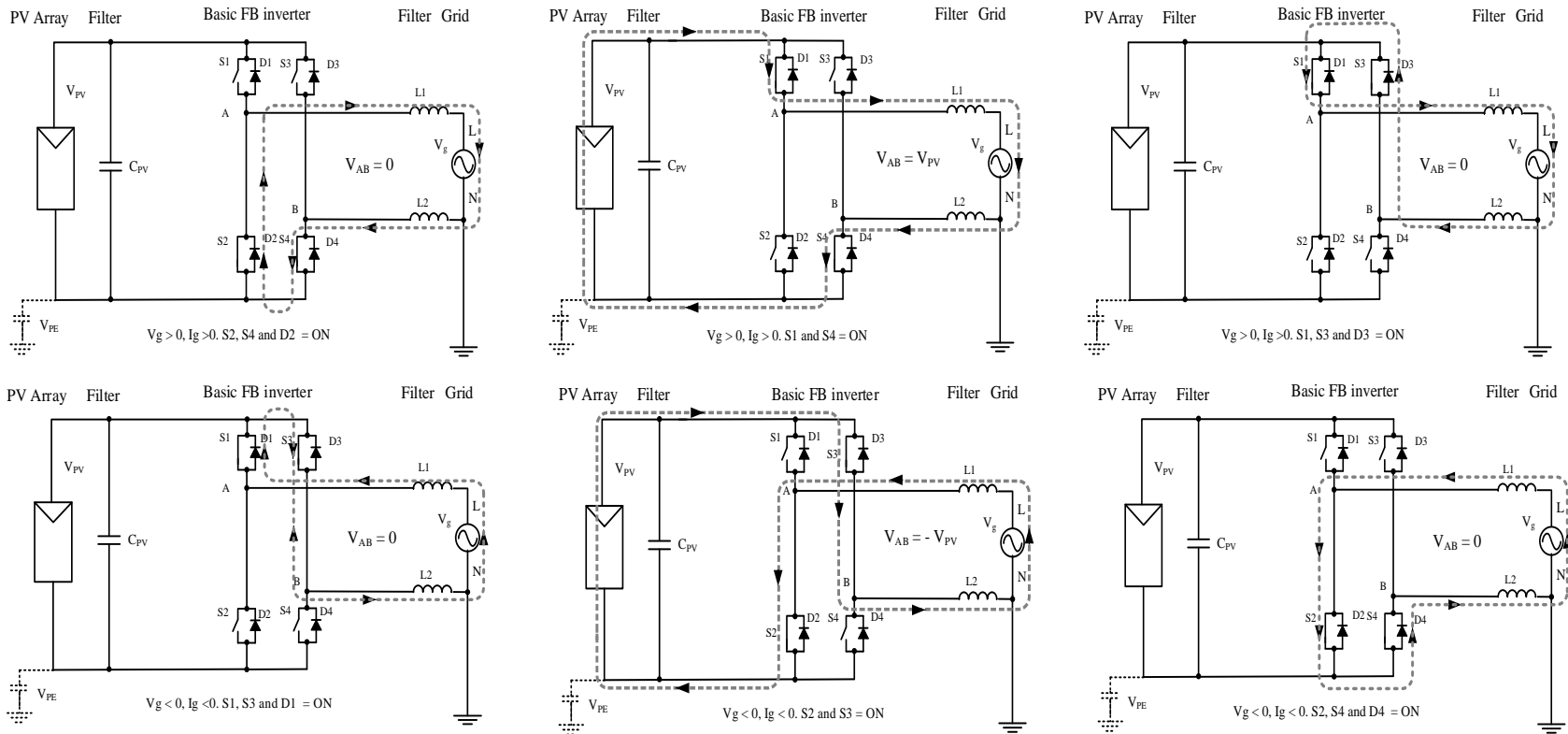


- Leg A and B are switched with high frequency with mirrored sinusoidal reference
- Two 0 output voltage states possible: S1 and S3 = ON and S2 and S4 = ON
- The switching ripple in the current equals 2x switching frequency → lower filtering
- Voltage across filter is unipolar → low core losses
- V_{PE} has switching frequency components → high leakage current and EMI

Common-mode behavior

- DC-AC converter PWM modulation


Bipolar PWM

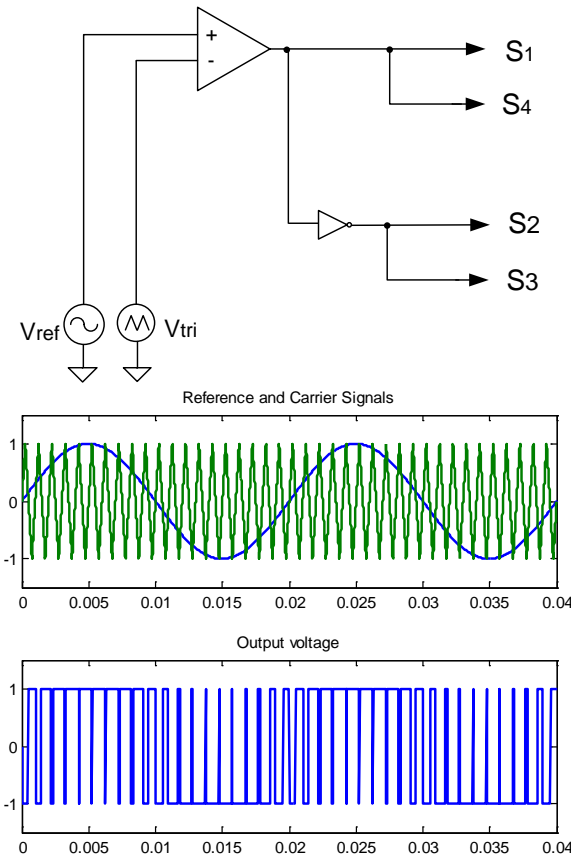S1 + S4 and S2 + S3 are switched complementary at high frequency



Unipolar PWM

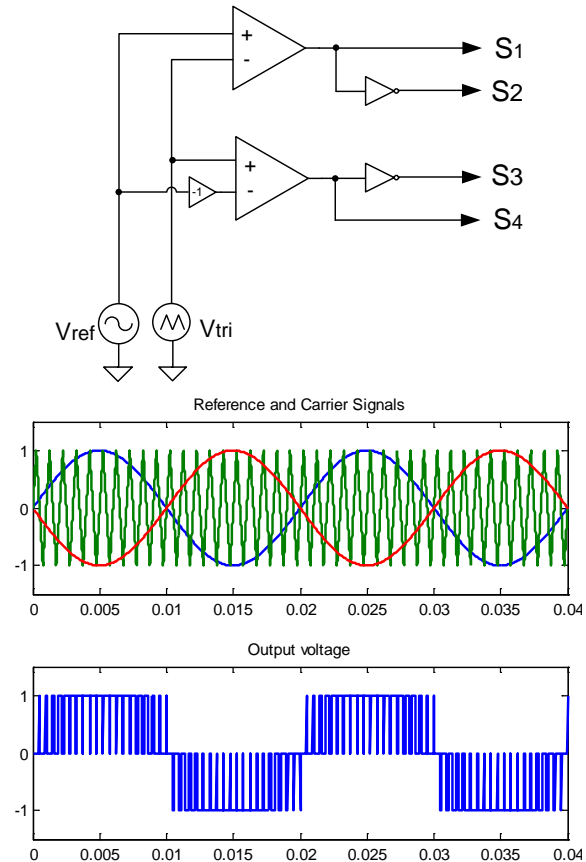Leg A and B are switched with high frequency with mirrored sinusoidal ref.




Common-mode behavior


- DC-AC converter:

$V_{DC}=500V$, $L_{fi}=L_{fg}=1mH$; $R_{ls}=0.05$; $C_f=4.7\mu F$

Bipolar PWM


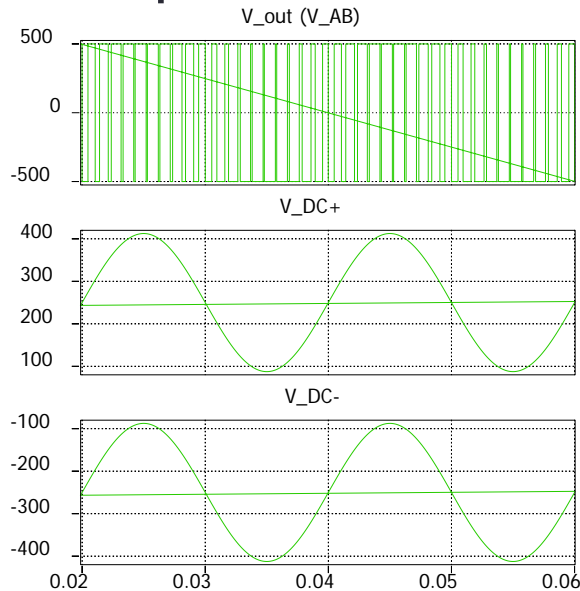


Unipolar PWM

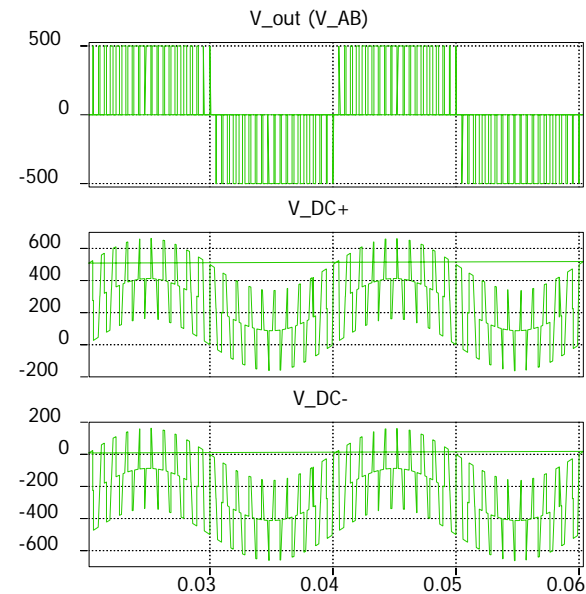

Leakage current in applications

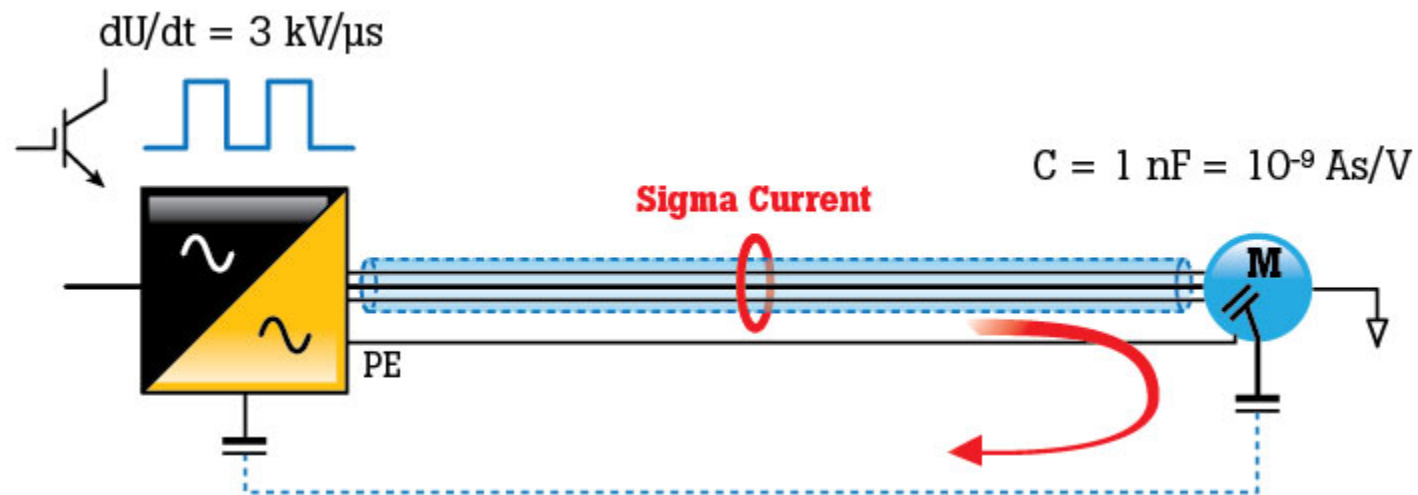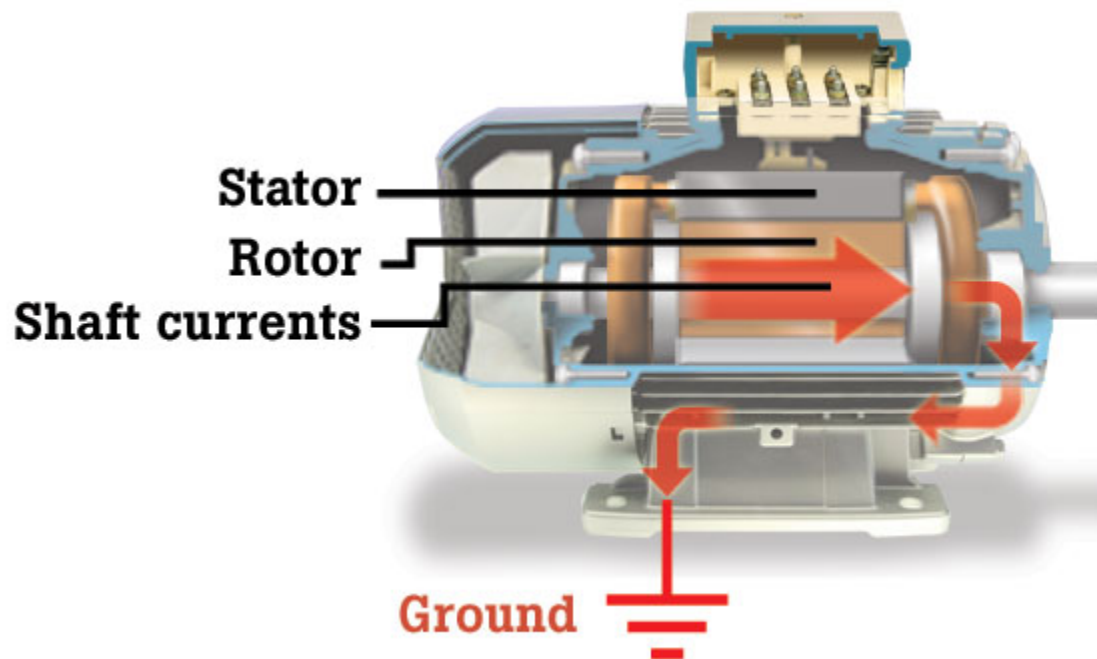- Bearing currents in motor drives (AC)
- Ground currents in PV (AC)
- Potential induced degradation in PV (DC)



Wear protection for future electric motors

Future cars will need higher voltage as current models. New, electrically conductive lubricants will avoid wear in electrical motors and alternators.




BOSCH

Invented for life

ball bearing


lubricating film

electrical discharge

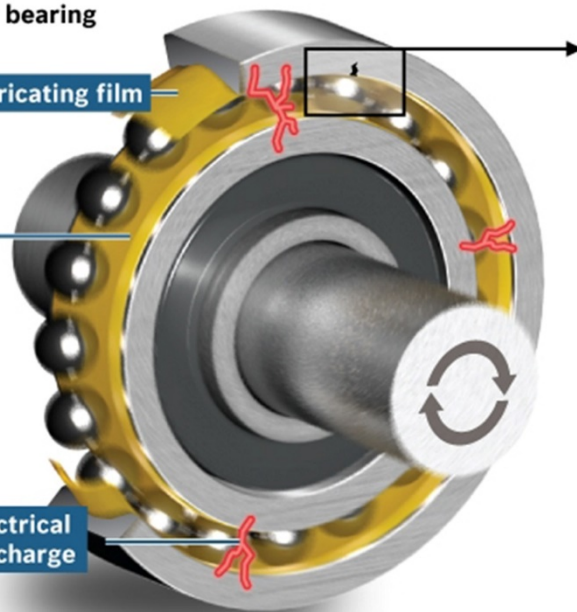


non conductive lubricant film

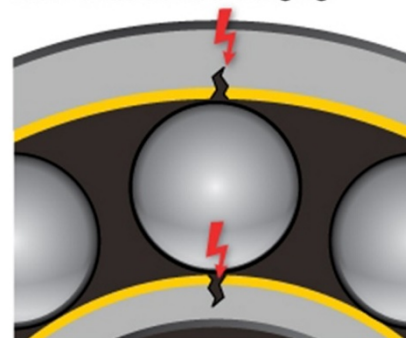↓ damage at the surfaces resulting from electrical discharging



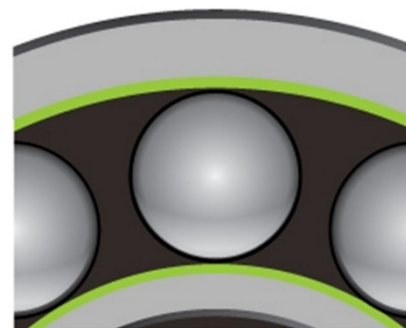conductive lubricant film
no electrical discharging → reduced wear




voltage level in vehicle electrical systems

today



in future

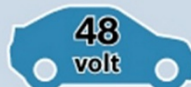

Bearing current


- Blackened lubricant shows the effects of electrical currents produced by variable frequency drives, which can create hot spots within the bearing.



Common-mode voltage (AC)


Parasitic capacitance of the PV array

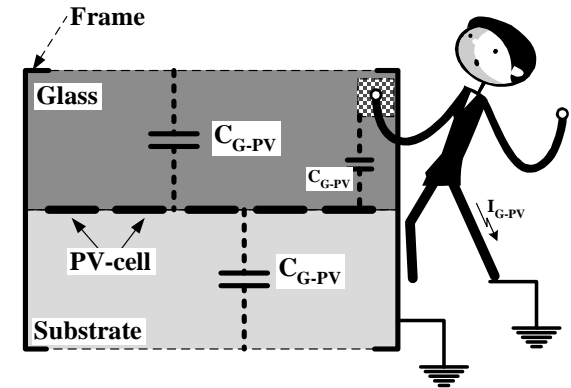
- PV array has large surface
- Parasitic capacitance formed between grounded frame and PV cells
- Its value depends on the:
 - Surface of the PV array and grounded frame
 - Distance of PV cell to the module
 - Atmospheric conditions and dust which can increase the electrical conductivity of the panel's surface



Leakage current

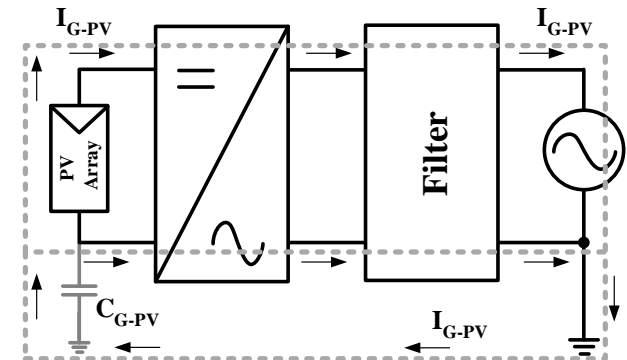
- Charging and discharging this capacitance leads to ground leakage currents (unsafe for human interaction; damage PV panels)
- Amplitude of leakage current depends on
 - Value of parasitic capacitance
 - Amplitude and frequency of imposed voltage
- RCM (Residual Current Monitoring) unit for monitoring leakage ground currents



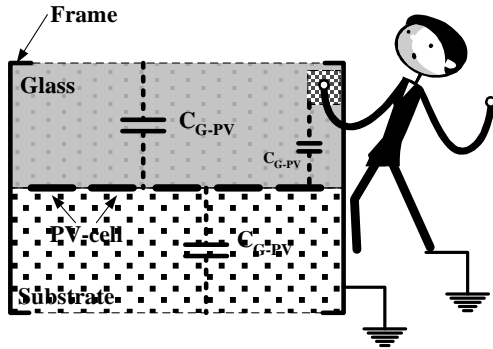


	Soleil FVG 36-125	Kyocera KS10	BPSolar MSX120
Surface of PV panel	204 x 352mm ²	1197 x 535mm ²	1108 x 991mm ²
Power at MPP (STC)	80W	10W	120W
$C_{G-PV}(1 \text{ panel})$	130pF	57pF	21pF
$C_{G-PV}(1 \text{ panel}) \text{ wet}$	1,38nF @ 10kHz	2,39nF @ 10kHz	3nF @ 10kHz
$C_{G-PV}(2 \text{ panels})$	247pF	101pF	not available
$C_{G-PV}(1 \text{ panel} + \text{ palm})$	140pF	150pF	200pF
$C_{G-PV}(1 \text{ panel} + \text{ palm}) \text{ wet}$	185pF @ 10kHz	230pF @ 10kHz	200pF @ 10kHz
$C_{G-PV}(1 \text{ panel} + \text{ copper plate})$	160pF	140pF	150pF
$C_{G-PV}(1 \text{ panel} + \text{ copper plate}) \text{ wet}$	210pF @ 10kHz	212pF @ 10kHz	257pF @ 10kHz


V_{AB} , V_{PE} and I_{PE} for FB-UP

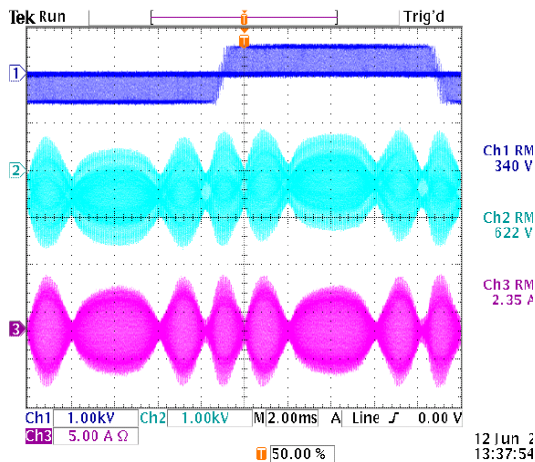

Spectrum of voltage to ground V_{Cp}

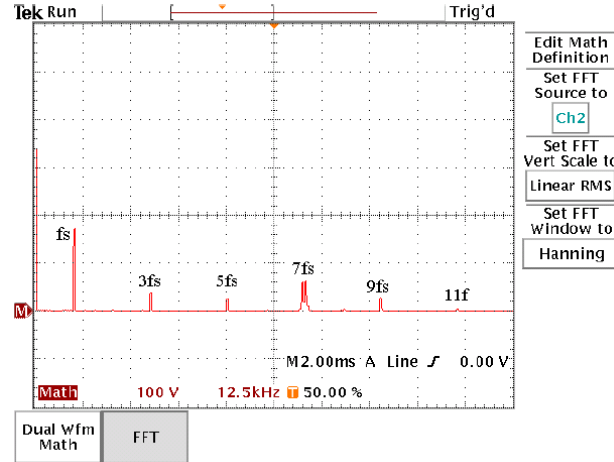

Spectrum of leakage current: I_{Cp}

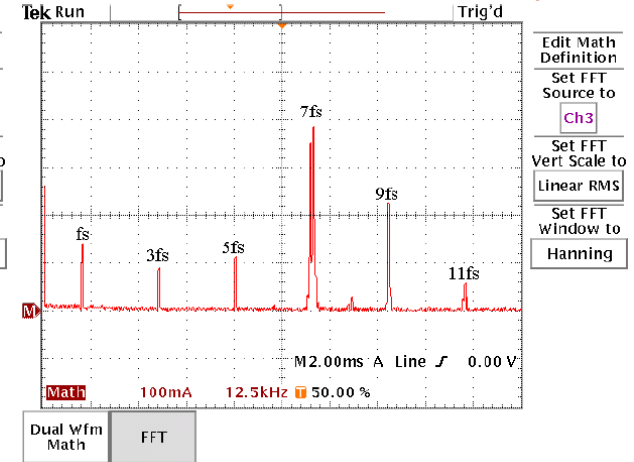

Based on I_{Cp} and V_{Cp} and different frequencies the leakage capacitance was calculated at: $C_p = 13.6 \text{ nF}$ (7.06 nF/kWp). C_p is useful in high-frequency analysis and in damping resonances

Common-mode voltage (DC)

Thin-Film modules

- TCO corrosion: the electrochemical corrosion of thin film PV modules using transparent conductive oxides (TCO) as front contacts on the front cover glass
- In case of PV cells manufactured using the superstrate technology, the TCO used as the negative pole directly contacts the glass
- The negative bias voltage, especially for thin-film modules, can cause TCO corrosion via sodium diffusion through the glass together with the presence of water molecules in the TCO/glass interface. This deterioration is permanent.



Ref: R. Gonzalez, Inverter Topology Issues for Grounded PV Modules


Common-mode voltage (DC)

Backside contact modules

- Metallization of the positive and negative contacts is done on the backside of the cell (cell efficiency > 20%)
- Polarization effect: leakage current flowing through the EVA (ethylene vinyl acetate) film and the upper glass will result in the accumulation of charge carriers on the cell surface, which cannot be released, thereby effecting the performance of the cell
- If the cell experiences positive potential respect to the ground, then these negative charges cannot be released
- If the cell experiences a negative potential respect to ground, the effect can be reversed and the cell returns to its original state

This bias voltage depends on the DC-DC converter topology
For ex:

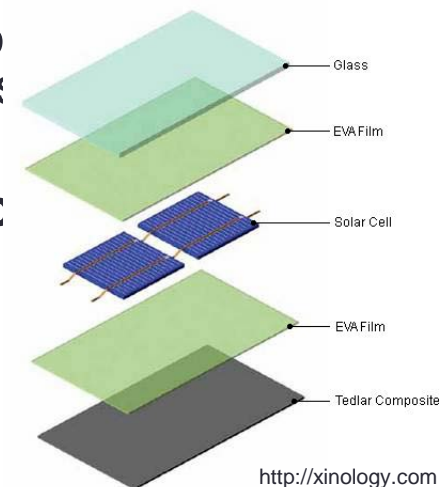- **Boost (boost inductor position)**
- **Buck-boost**
- **Push-Pull**



Agenda

- Differential-mode voltage and current
- Common-mode voltage and current
- PWM of switch-mode converters
- DC-DC converters
- DC-AC converters
- Exercise