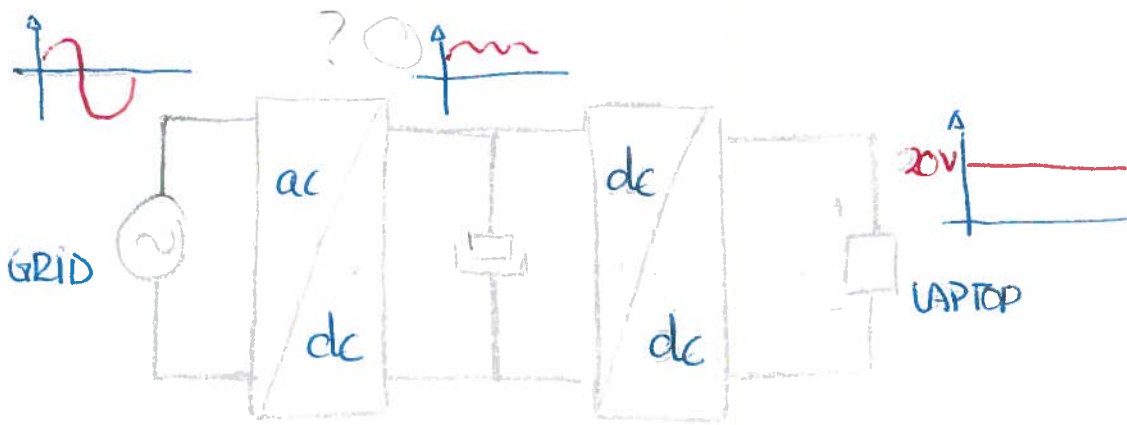



THE IDEAL RECTIFIER



THE IDEAL RECTIFIER:


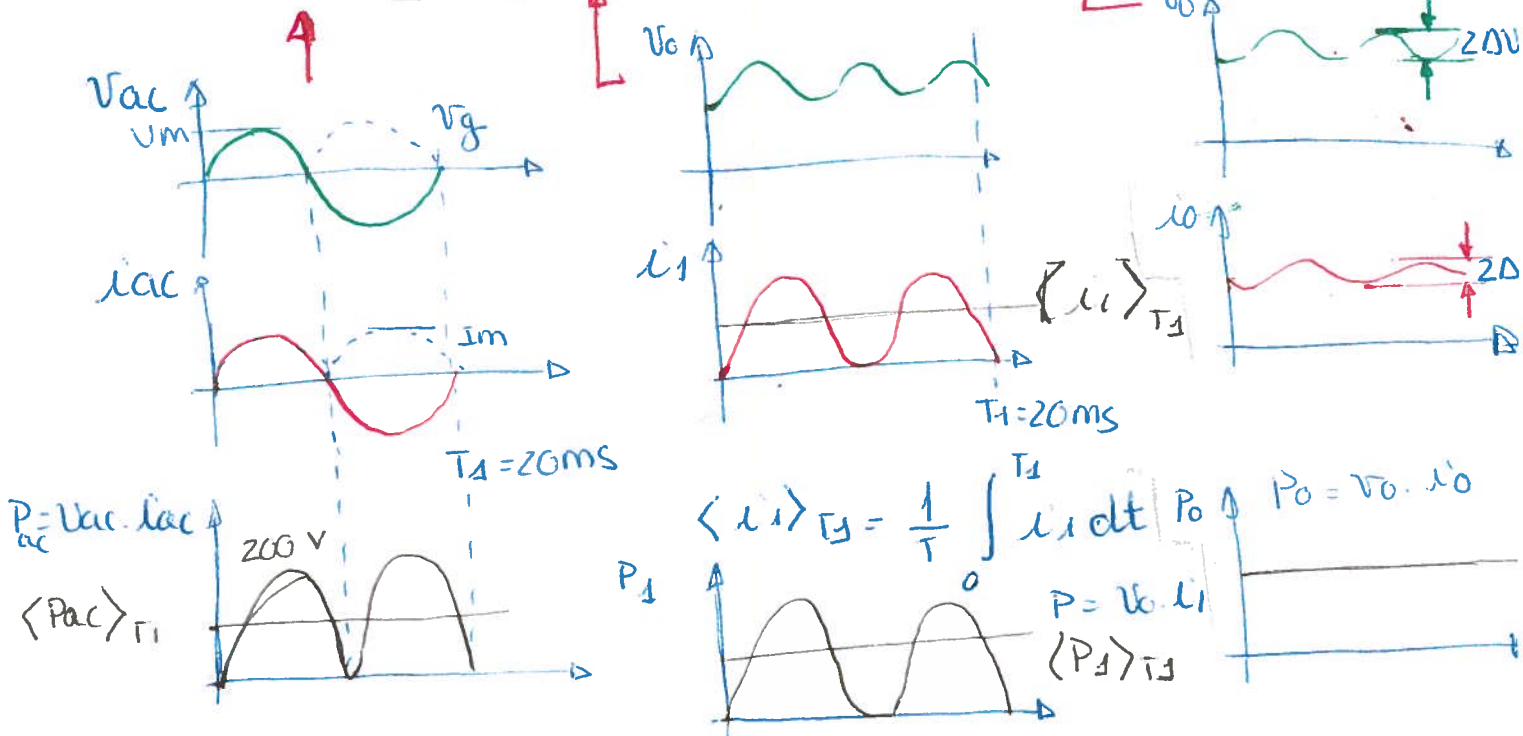
$$R_e = \frac{V_{ac}}{i_{ac}} = \frac{V_{ac}}{I_{ac}}$$



IDEAL RECTIFIER \Rightarrow

$$\langle P_{ac} \rangle_{T_1} = \langle P_1 \rangle_{T_1}$$




$$P_{ac} = P_1 = P_o$$

$$\langle P_{ac} \rangle_{T_1} = \langle P_1 \rangle_{T_1} = \langle P_o \rangle_{T_1}$$

→ For a 3-phase rectifier (remembering that the phases are de-phased 120°), when you "sum" each phase, you also get a DC power

→ Single phase is just for low power app.

PFC - BOOST

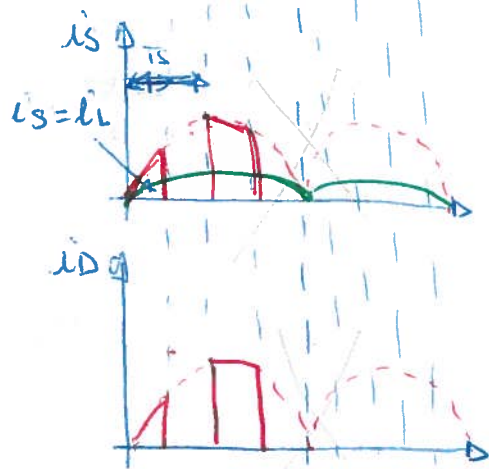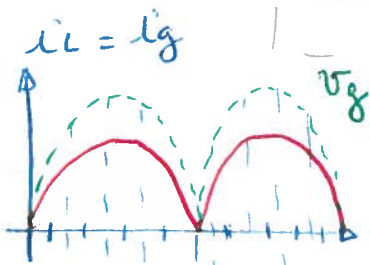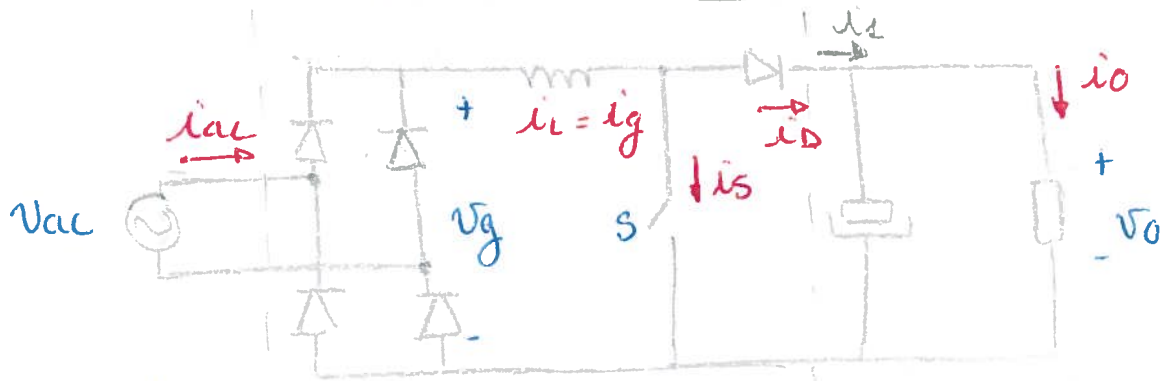

$$\begin{aligned} \langle i_s \rangle_{T_s} &= \frac{1}{T_s} \int_0^{T_s} i_s dt \\ &= \frac{1}{T_s} \int_0^{T_s} \langle i_L \rangle_{T_s} dt + \frac{1}{T_s} \int_{dT_s}^{T_s} 0 dt \end{aligned}$$

$$\langle i_s \rangle_{T_s} = \langle i_L \rangle_{T_s} \cdot d$$

COMPLEMENTARIO DE

$$\langle i_D \rangle_{T_s}$$

Ex:

$$f_s = 50 \text{ Hz} \rightarrow T_s = 20000 \mu\text{s}$$

$$f_s = 30 \text{ KHz} \rightarrow T_s = 33 \mu\text{s}$$

$$\langle i_D \rangle_{T_s} = \frac{1}{T_s} \int_0^{dT_s} 0 \cdot dt + \frac{1}{T_s} \int_{dT_s}^{T_s} \langle i_L \rangle_{T_s} dt$$

$$\langle i_D \rangle_{T_s} = \langle i_L \rangle_{T_s} (1-d) = i_1$$

↳ COMPLEMENTARIO DE i_s

$$\langle i_L \rangle_T = |I_m \sin \omega t|$$

$$1-d = \frac{\langle v_g \rangle_{TS}}{\langle v_g \rangle_{TS}}$$

$$\langle i_D \rangle_{TS} = |I_m \sin \omega t| \frac{|V_m \sin \omega t|}{\langle v_o \rangle_{TS}}$$

$$\langle i_D \rangle_{TS} = \frac{I_m \cdot V_m \cdot \sin^2 \omega t}{\langle v_o \rangle_{TS}} = \frac{I_m \cdot V_m}{\langle v_o \rangle_{TS}} \cdot \frac{1}{2} (1 - \cos 2\omega t)$$

$$\langle i_D \rangle_{TS} = \frac{I_m \cdot V_m}{\langle v_o \rangle_{TS}} \cdot \frac{1}{2} \Rightarrow \boxed{\langle i_D \rangle_{TS} \cdot \langle v_o \rangle_{TS} = \frac{I_m \cdot V_m}{2}}$$

$$P_a = I_{ac-rms} \cdot V_{ac-rms} = \frac{I_m}{\sqrt{2}} \cdot \frac{V_m}{\sqrt{2}}$$


$$R_e = \frac{V_{ac-rms}}{I_{ac-rms}} = \frac{V_m}{I_m} \Rightarrow I_m = \frac{V_m}{R_e}$$

→ WHAT IS THE DUTY CYCLE (IDEAL RECTIFIER)

$$d = 1 - \frac{\langle v_g \rangle_{TS}}{\langle v_o \rangle_{TS}} \approx \frac{1 - |V_m \sin \omega t|}{V_o}$$


$$V_o \rightarrow V_o < V_m \Rightarrow d < 0$$

↓
IMPOSSIBLE

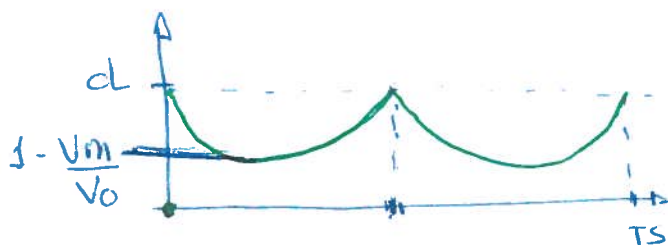

$$1 - \frac{V_m}{V_o} < d < 1$$

OPERATION MODES

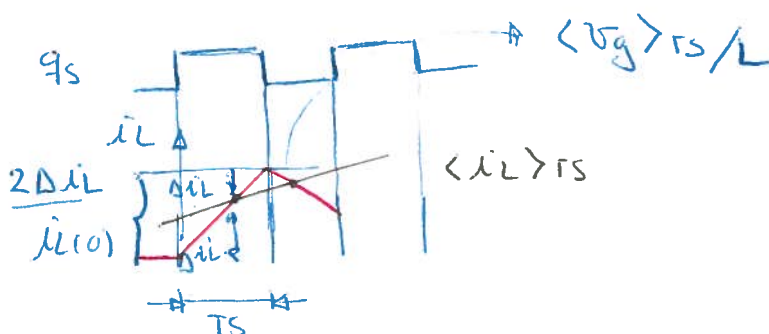

$$2 \cdot \Delta i_L = \frac{\langle v_g \rangle_{TS}}{L} \cdot d T_S$$

$$\boxed{\Delta i_L < \langle i_L \rangle_{TS}}$$

CONTINUOUS CONDUCTION MODE
(CCM)

$$\frac{\langle V_g \rangle_{Ts}}{2L} \cdot dT_s < \frac{\langle V_g \rangle_{Ts}}{R_e} \Rightarrow \boxed{d < \frac{2L}{R_e \cdot T_s}} \quad \underline{\underline{\text{CCM}}}$$

If we want to have the rectifier working in CCM, this relations NEED to be respected.


BUCK - BOOST



$$\langle V_o \rangle_{Ts} = -V_g \cdot \frac{d}{1-d}$$

EXERCISES: CURRENT PROGRAMMED CONTROL

LECTURE

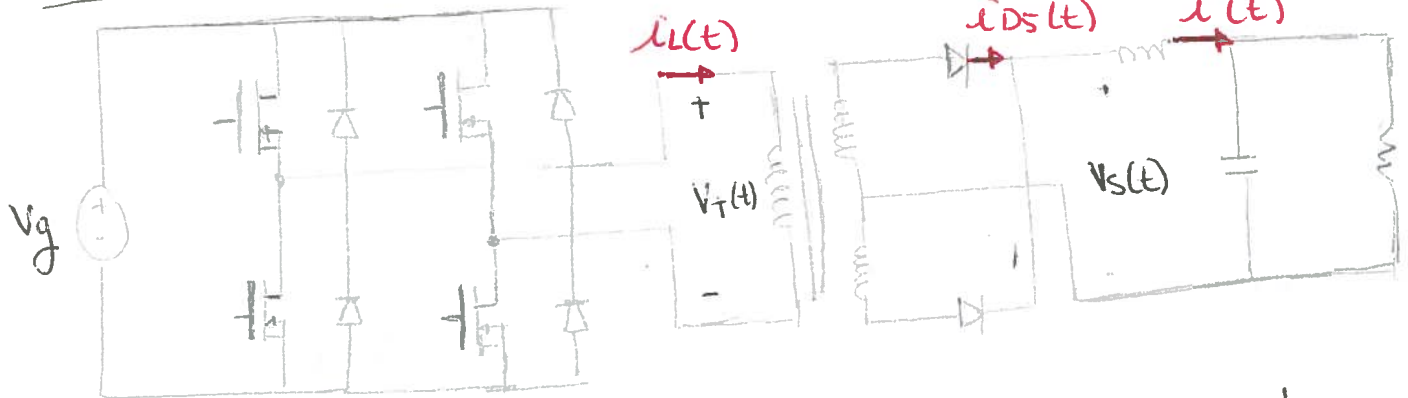

$$V_g = 320 \text{ V}$$

$$P = 1000 \text{ W}$$

$$V_o = 42 \text{ V}$$

$$D = 0.7$$

$$T_s = 10 \mu\text{s}$$


$$L = 50 \mu\text{H}$$

$$C = 100 \mu\text{F}$$


Current controller whose waveforms are referred to the secondary side of the transformer.

- a) Sketch the waveforms $V_s(t)$ and $i'(t)$ for T_s .
Calculate m_1 and m_2 .

$$i'(t) = i_L(t)$$

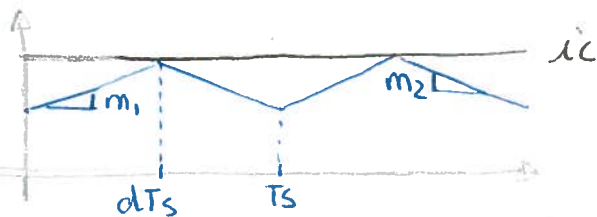

$V_s(t)$ (INPUT TO THE BUCK CONVERTER)

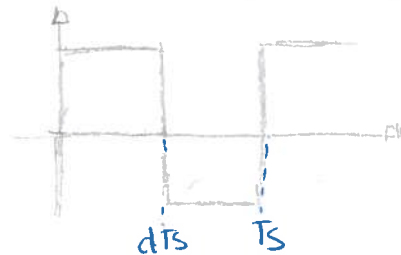

BUCK CONVERTER

$$V_o = V_s \cdot D \rightarrow V_s = \frac{V_o}{D} = \frac{42}{0.7} = 60 \text{ V}$$

$$m_1 (\text{BUCK}) = \frac{V_s - V_o}{L} = \frac{60 - 42 \text{ [V]}}{50 \cdot 10^{-6} \text{ [H]}} = 0.36 \text{ A}/\mu\text{s}$$

$$m_2 (\text{BUCK}) = -\frac{V_o}{L} = -\frac{42}{50 \cdot 10^{-6}} = -0.84 \text{ A}/\mu\text{s}$$

- b) What is the minimum artificial ramp slope m_a , that will stabilize the controller at the given operating point?
Express your result in terms of m_2 and D .

$$d = \frac{m_2 - m_a}{m_1 + m_a} = 1 \rightarrow m_2 - m_a = m_1 + m_a$$

$$2m_a = m_2 - m_1$$

$$m_a = \frac{m_2 - m_1 \cdot \frac{D}{1-D}}{2} \leftarrow \frac{m_2}{m_1} = \frac{D}{1-D} \leftarrow m_a = \frac{m_2 - m_1}{2}$$

c) Calculate the value of m_a and R


$$m_2 = 0.84 \text{ A}/\mu\text{s}$$

$$m_a = 0.84 \cdot \frac{1 - D/D}{2} = 0.84 \cdot \frac{(1 - 0.3/0.3)}{2} = 0.24 \text{ A}/\mu\text{s}$$

$$P = V \cdot I \rightarrow I = P/V = 1000/42 = 23.80 \text{ A}$$

$$V = R \cdot I \rightarrow R = \frac{V}{I} = \frac{42}{23.8} = 1.764 \Omega$$

EXAM JANUARY 2011

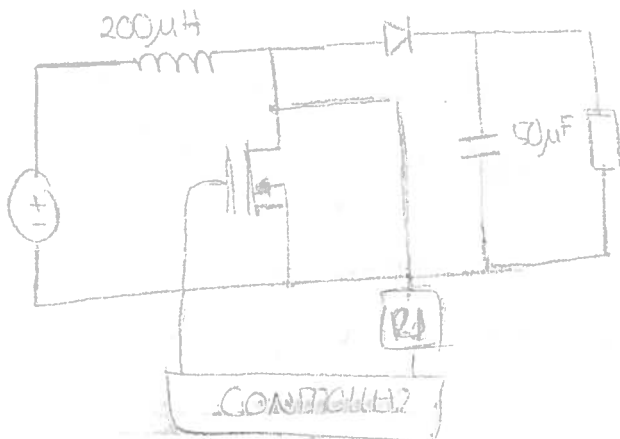

$$T_s = 10 \mu\text{s}$$

$$R = 20 \Omega$$


$$V_g = 20 \text{ V}$$

$$V = 100 \text{ V}$$

$$R_L = 1 \Omega$$

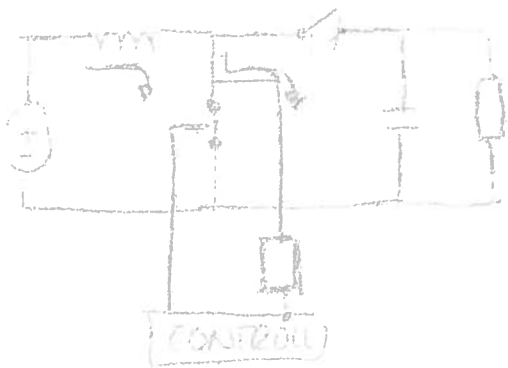a) Calculate the average current of the switch.

- Current in the switch \rightarrow just in switch
- SWITCH ON current: $0.4 + 0.4 \text{ A}$



The current in the switch will be the same that in the inductance.

$$i_L = i_L(0) + m_1 \cdot d \cdot T_s$$

$$\text{BOOST CONVERTER: } m_1 = \frac{V_g}{L}, m_2 = \frac{V_g - V}{L}$$

$$m_1 = \frac{20}{200 \cdot 10^{-6}} = 0.1 \text{ A}/\mu\text{s}$$

$$m_2 = \frac{20 - 100}{200 \cdot 10^{-6}} = -0.4 \text{ A}/\mu\text{s}$$

STEADY STATE

$$\frac{m_2}{m_1} = \frac{D}{1-D} = \frac{D}{1-D}$$

$$\frac{0.4}{0.1} = (1-D) = D$$

STEADY STATE $\rightarrow D = d = 0.8$

$$i_L = i_L(0) + 0.1 \frac{\text{A}}{\mu\text{s}} \cdot 0.8 \cdot 10 \mu\text{s}$$

$$i_L = i_L(0) + 0.8$$

$$4 - 4D = 0 \rightarrow 5D = 4 \rightarrow \frac{D}{5} = \frac{4}{5} = 0.8$$

b) Add a stabilizing ramp and calculate the minimum slope m_a that will give stability.

$$\alpha = \frac{m_2 - m_a}{m_1 + m_a} \rightarrow |L(s)| \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$

STABILIZING : $\alpha = 1$

signos!?


$$\frac{m_2 - m_a}{m_1 + m_a} = 1 \Rightarrow m_2 - m_a = m_1 + m_a \rightarrow 2m_a = m_2 - m_1$$

$$m_a = \frac{m_2 - m_1}{2} = \frac{-0.4 - 0.1}{2} = \frac{-0.5}{2} = \underline{\underline{-0.25}}$$

EXERCISE: PULSE WIDTH MODULATED RECTIFIERS

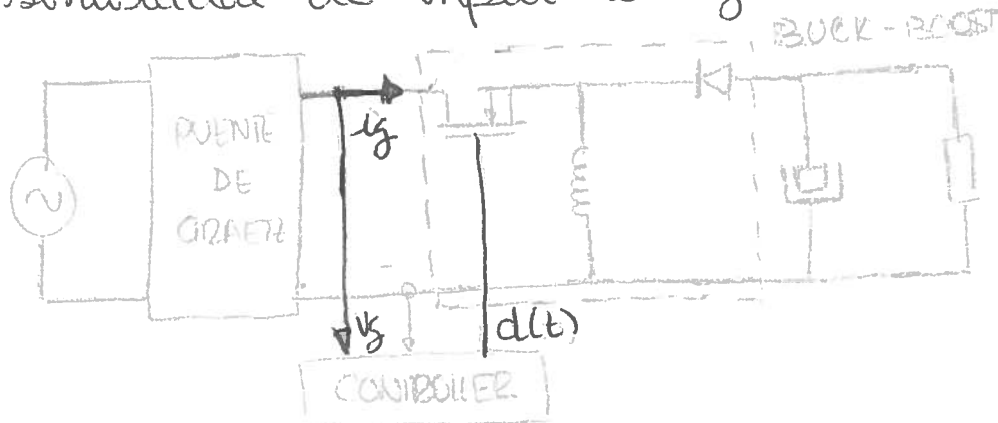18.1

The BUCK of figure 18.5 (p.642) is replaced by a BUCK-BOOST. The inductor energy storage has negligible influence on the low frequency components of the converter waveforms. The average frequency components of the converter waveforms. The average dc output voltage is V and the load power is P_{load} . The dc output voltage is V and the sinusoidal ac input voltage has a peak ^{amplitude} V_M .



$$d = \frac{V_0}{V_0 - V_g}$$

a) Determine expressions for the duty cycle variation $d(t)$ and the inductor current $i(t)$ assuming that the converter is operating in CCM.

$$V_0 = V_{ac} \cdot \frac{\delta}{1-\delta}$$


$$\delta = \frac{L}{T}$$

• DEDUCE THE EQUATIONS FOR A BUCK-BOOST


SON : $0 \leq t \leq DT$



SOFF : $DT \leq t \leq T$

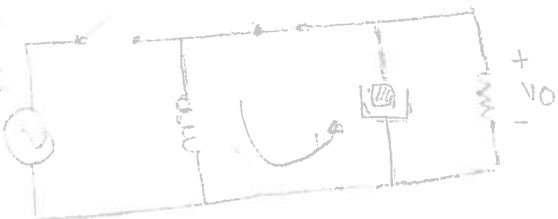

STUDYING THE INDUCTANCE

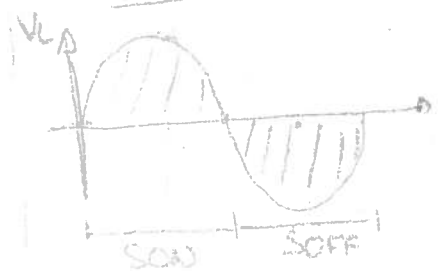

STEADY STATE : $i_L = 0$

$$i_L(t_{ON}) = V_{ac} \cdot dt$$

$$i_L(t_{OFF}) = -V_0 \cdot (1-dt)$$

$$i_L(t)_{ON} = i_L(t)_{OFF}$$

$$V_{ac} \cdot dt = -V_0 \cdot (1-dt)$$

$$V_{ac} \cdot dt + V_0 \cdot (1-dt) = 0$$

$$dt(V_{ac} - V_0) + V_0 = 0$$

$$d(t) = \frac{V_0}{V_{ac} - V_0} = \frac{-V_0}{V_0 - V_{ac}}$$

Knowing : $V_{ac} = V_M \cdot \sin(\omega t)$

$$d(t) = \frac{V_0}{V_0 - V_M \sin(\omega t)} = \frac{1}{1 - \frac{V_M}{V_0} \sin(\omega t)}$$

STEADY STATE EQUATION

FOR NON-STEADY STATE:

$$\langle V_L \rangle_{TS} = \langle V_O \rangle_{TS} + (\langle V_g \rangle_{TS} - \langle V_O \rangle_{TS}) d$$

(CCM) $\rightarrow 0 = \langle V_O \rangle_{TS} + (\langle V_g \rangle_{TS} - \langle V_O \rangle_{TS}) d$

$$d = - \frac{\langle V_O \rangle_{TS}}{\langle V_g \rangle_{TS} - \langle V_O \rangle_{TS}}$$

CURRENT $i(t)$:

$$\langle i_g \rangle_{TS} = d \cdot \langle i_L \rangle_{TS}$$

$$R_e = \frac{\langle V_g \rangle_{TS}}{\langle i_g \rangle_{TS}}$$

$$\langle i_L \rangle_{TS} = \frac{\langle i_g \rangle_{TS}}{d}$$

$$\langle i_L \rangle_{TS} = \frac{\langle V_g \rangle_{TS}}{R_e \cdot d}$$

$$\langle i_L \rangle_{TS} = \frac{\hat{V}_{ac} |\sin \omega t|}{R_e} \cdot \frac{1}{\left(1 - \frac{\hat{V}_{ac}}{V_O} |\sin \omega t|\right)^{-1}} \quad ?$$

$$\langle i_L \rangle_{TS} = \hat{V}_{ac} |\sin \omega t| \cdot \left(1 - \frac{\hat{V}_{ac}}{V_O} |\sin \omega t|\right) \cdot \frac{1}{R_e}$$

b) Derive the conditions for operation in the continuous mode. Manipulate your result to show that the converter operates in CCM when R_e is less than $R_{e, \text{crit}}(L, T_s, V_g(t), V)$ and determine $R_{e, \text{crit}}$.

In CCM it is required:

$$\langle i_L \rangle_{TS} > \Delta i_L$$

$$\Delta i_L = \frac{\langle V_g \rangle_{TS} \cdot T_s \cdot d}{2L}, \quad \langle i_L \rangle_{TS} = \frac{\langle V_g \rangle_{TS}}{R_e \cdot d}$$

$$\frac{\langle V_g \rangle_{TS}}{R_e \cdot d} > \frac{\langle V_g \rangle_{TS} \cdot T_s \cdot d}{2L} \Rightarrow \frac{1}{R_e \cdot d} > \frac{d \cdot T_s}{2L}$$

$$R_e < \frac{1}{d^2} \cdot \frac{1}{T_s} \cdot 2L \Rightarrow R_e < \left(\frac{V_O}{V_O - V_g}\right)^2 \cdot \frac{2L}{T_s}$$


BUCK-BOOST EQ:

$$\frac{V_O}{V_g} = \frac{-d}{1-d} \rightarrow \frac{V_O}{V_g} (1-d) = -d \rightarrow \frac{V_O}{V_g} - \frac{V_O}{V_g} \cdot d = -d$$

$$\left(\frac{V_O}{V_g} - 1\right) d = \frac{V_O}{V_g} \rightarrow d = \frac{V_O - V_g}{V_O}$$

EXERCISE 3. EXAM JANUARY 2011

Boost converter

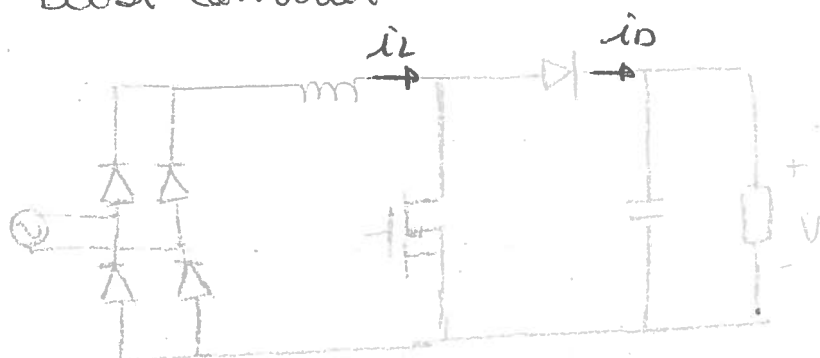

$$V_0 = 390 \text{ V}$$

$$P_0 = 500 \text{ W}$$

$$R_{ms} = 230 \text{ V}$$

$$\eta = 0.95$$

$$f = 50 \text{ Hz}$$

$$f_s = 100 \text{ kHz}$$

a) and b) converter is operating in CCM...

a) For one fundamental period sketch the current of $i_L(t)$



$$I_L = \frac{V_m \cdot |\sin(\omega t)|}{R_e}$$



b) For one switching period sketch $i_D(t)$ assume the average current is 1 A and the duty cycle 25%.



same power
dissipation
is being

c) Calculate the value of the emulated resistance

$$P_{INPUT} = \frac{P_{OUTPUT}}{\eta} = \frac{500}{0.95} = 526.32 \text{ W} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} I_L = \frac{P}{V} = 2.287 \text{ A}$$

$$V_0 = 230 \text{ V}$$

$$R_e = \frac{V_m |\sin(\omega t)|}{I_L} = \frac{230 \cdot \sqrt{2} |\sin(2\pi 50 \cdot 10 \cdot 10^{-6})|}{2.287}$$

c) For what values of R does the converter always operate in CCM? and in DCM?

MINIMUM: R_{CRIT} at $V_g = 0 \rightarrow V_L = 0$

$$R_{CRIT} < \frac{2L}{T_s}$$

MAXIMUM: R_{CRIT} at $V_g = V_{ac}$

$$R_{CRIT} = \left(\frac{V_O - V_{O,c}}{V_{ac}} \right)^2 \cdot \frac{2L}{T_s} \quad ??$$

d) The ac input voltage has rms amplitude in the range 108V - 132V. The maximum load power is 100W, and the minimum load power is 10W. The dc output voltage is 120V. The switching frequency is 75 KHz. What value of L guarantees that the converter always operates in CCM? in DCM?

$$R_{MAX} = \left(\frac{132}{10} \right)^2 = 1742 \Omega$$

$$R_{MIN} = \left(\frac{108}{100} \right)^2 = 117 \Omega$$

$$1 < \frac{2L}{R_{MAX} T_s}$$

$$L > \frac{R_{MAX} T_s}{2}$$

So CCM is obtained for:

$$L > \frac{R_{MAX} T_s}{2}$$

$$L > \frac{1742 \cdot \frac{1}{75 \cdot 10^3}}{2} \rightarrow \boxed{L > 12 \text{ mH}}$$

Whereas in DCM:

$$L < \frac{R_{MIN} T_s}{2} \cdot \left(\frac{V_{ac}}{V_O - V_{ac}} \right)^2$$

$$L < \frac{117 \cdot \frac{1}{75 \cdot 10^3}}{2} \cdot \left(\frac{108}{120 - 108} \right)^2$$

$$\boxed{L < 125 \mu\text{H}}$$