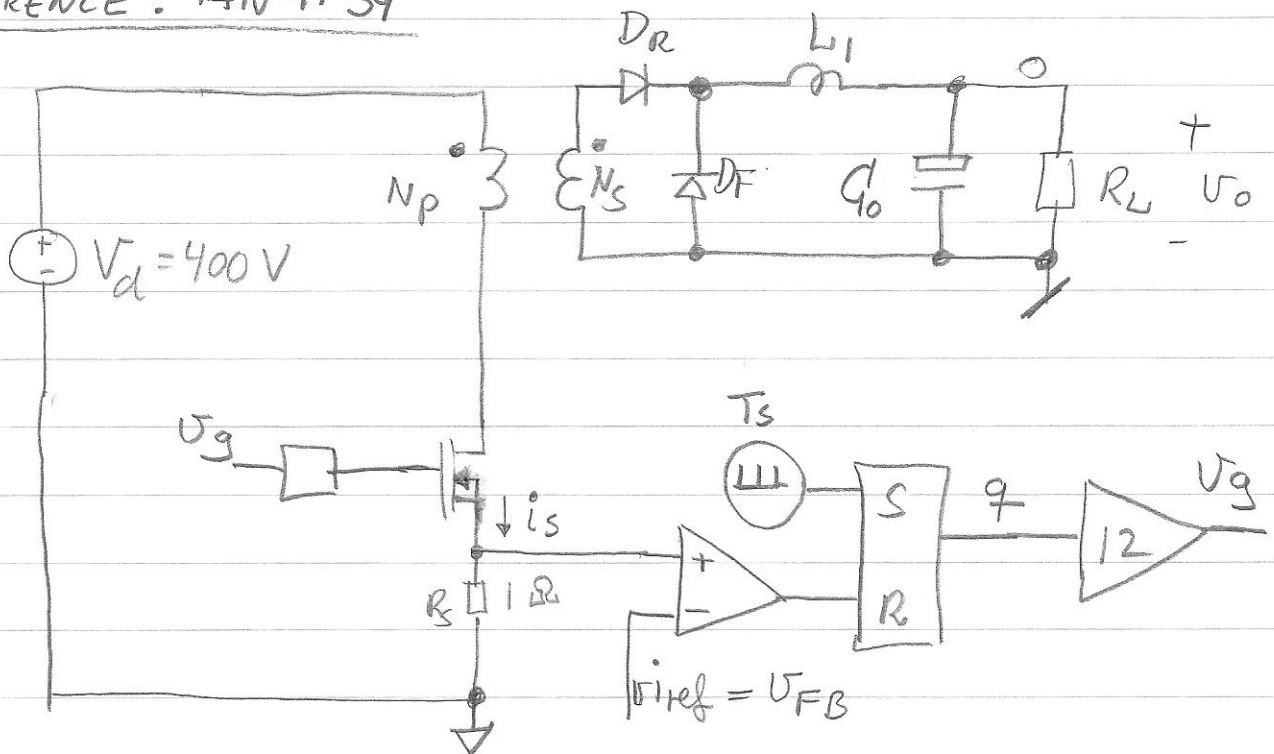


# Problem 3 lecture

REFERENCE: AN4134



Spec:  $V_o = 24V$

$T_s = 20\mu s$


$L_1 = 200\mu H$

$P_o = 70W$

$C_o = 300\mu F$

$N_p/N_s = 5$

$\omega_{cross} = 20000 \text{ rad/s}$

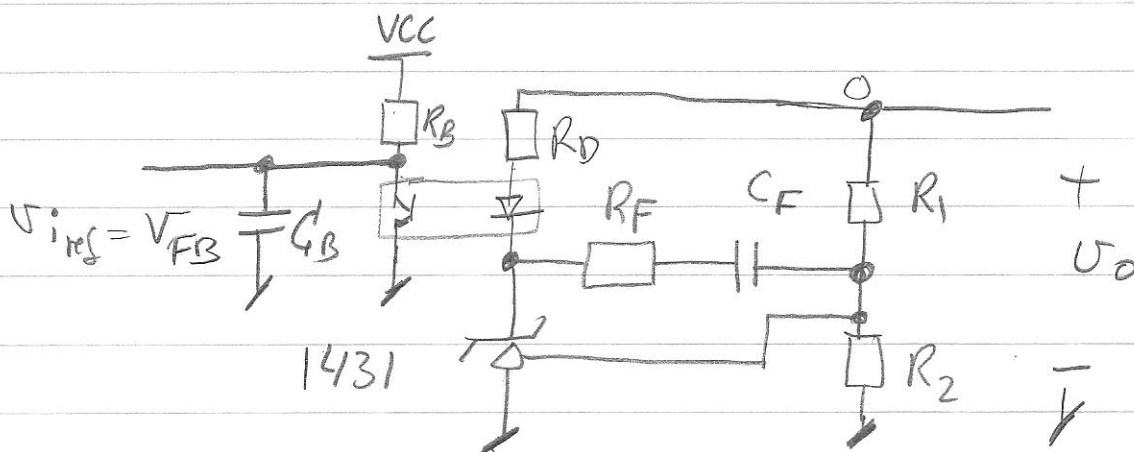

0: Sketch plot of  $G_{vc}$

1: Select value of  $R_1 + R_2$

2: Find desired gain at

$$\omega_{cross} \quad \left( \text{Gain-}\omega_{cross} \sim K_{op} \frac{R_B}{R_D} \right)$$

3: Find  $\omega_{zc} = \omega_{cross} / 3$

Select  $R_F$  and  $C_F$

4: Find  $\omega_{pc} = 3 \omega_{cross}$

Select  $R_D, R_B$  and  $C_B$

5: Simulate in LTSpice

a) Build power circuit

b) Build current controller

c) Build controller


d) Simulate the converter.

Specification:  $C_o = 300\mu\text{F} \rightarrow 330\mu\text{F}$ ,  $L_1=200\mu\text{H}$ ,  $R_L=8.2\ \Omega$ ,  $V_d=400$ ,  $N_P/N_S=5$ ,  $V_o = 24\ \text{V}$

$\omega_{\text{cross}} = 20000\ \text{rad/s}$
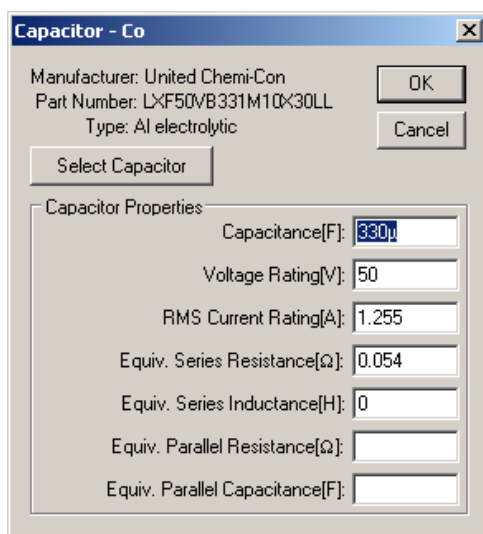
### Answer 0: Sketch plot of $G_{vc}$

Select a capacitor from the list of capacitors the nearest standard capacitance to  $300\mu\text{F}$  is  $330\ \mu\text{F}$ , notice have to look out for RMS current rating is not exceeded.





$R_c = 54\text{m}\Omega$

$R_s$ : Shunt resistor value used to measure the current of the transistor is selected to be:

$R_s = 1\ \Omega$

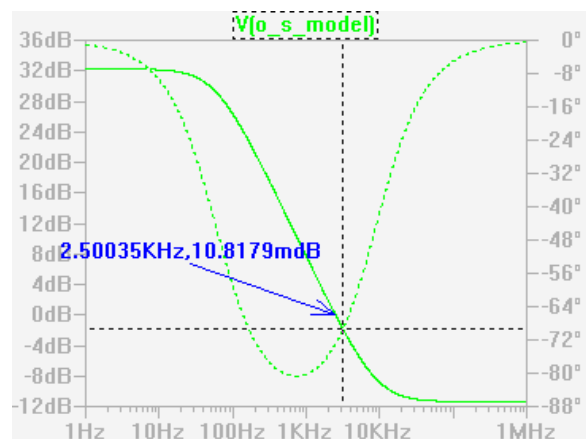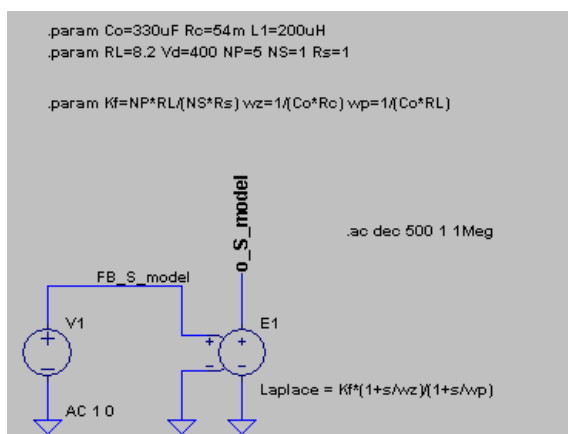Forward converter model implemented in LT spice  $G_{vc} = \tilde{v}_o / \tilde{v}_{FB}$  :



At 1 Hz the gain is 32.2 dB and at 2.5kHz (15707 rad/s) the gain is ~0 dB.

At  $\omega_c = 3.183$  kHz (20000 rad/s) the gain is -1.9 dB and the phase is -70 deg.

### Answer 1: Find R1 and R2

We know that Vref inside the TL431 is 2.5 V and the output voltage is  $V_o = 24$  V. R2 is selected to be **R2=1kOhm** and the current of R2 is then 2.5 mA. From the voltage divider equation R1 is determined:

$$2.5V = 24V \frac{R_2}{R_1 + R_2}$$

R1 is found to be **R1 = 8.6 kOhm**.

### Answer 2: Find desired gain at $\omega_{cross}$

Compensator design type II.

The compensator function is:


$$G_c = \frac{\tilde{v}_{FB}}{\tilde{v}_o} = -\frac{w_i}{s} \frac{1 + s / w_{zc}}{1 + s / w_{pc}}$$

$$w_i = \frac{K_{op} R_B}{R_D R_1 C_F}$$

$$w_{zc} = \frac{1}{(R_1 + R_F) C_F}$$

$$w_{pc} = \frac{1}{R_B C_B}$$

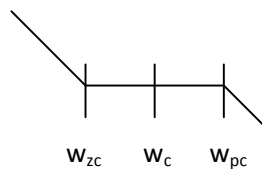The gain of  $G_c$  is sketched in the below plot and location of  $w_{zc}$ ,  $w_c$ ,  $w_{pc}$  is indicated:



Here  $w_c$  is located at the center so  $w_c = \sqrt{w_{zc} w_{pc}}$  and from specifications  $w_c = 20000$  rad/s and from forward converter transfer function the gain at  $w_c = 20000$  rad/s calculated to be -1.9 dB. The gain of the compensator must then be  $G_c(w_c) = 1.9$  dB to obtain an open loop gain  $G_{op} = 1$  dB at  $w_c = 20000$  rad/s.

Now we need to know what the gain of  $G_c(w)$  at  $w=w_c$  is and therefore  $s = jw_c = j\sqrt{w_{zc} w_{pc}}$  is substituted into the  $G_c$  function.

$$G_c(w_c) = -\frac{w_i}{j\sqrt{w_{zc} w_{pc}}} \frac{1 + j\sqrt{\frac{w_{pc}}{w_{zc}}}}{1 + j\sqrt{\frac{w_{zc}}{w_{pc}}}}$$

$$\|G_c(w_c)\| = \frac{w_i}{\sqrt{w_{zc} w_{pc}}} \frac{\sqrt{1 + \frac{w_{pc}}{w_{zc}}}}{\sqrt{1 + \frac{w_{zc}}{w_{pc}}}}$$

And this is reduced to the result:

$$\|G_c(w_c)\| = \frac{w_i}{w_{zc}}$$

If  $R_F \ll R_1$  then

$$\|G_c(w_c)\| = \frac{w_i}{w_{zc}} = \frac{K_{op} R_B}{R_D}$$

We need to find  $K_{op}$ ,  $R_B$  and  $R_D$ , remember  $\|G_c(w_c)\| = 1.9$  dB  $\|G_c(w_c)\| = 1.244$

**Answer 3: Find  $w_{zc} = w_{cross}/3$  select  $R_F$  and  $C_F$**

Select  $R_F = 100$  Ohm and with  $w_{zc} = w_c/3$  and  $w_{zc} = 1/((R_F + R_1) * C_F)$  then  $C_F = 3/(w_c(R_F + R_1))$  and  $C_F$  is found to be  $C_F = 17$  nF.


**Answer 4: Find  $w_{pc} = 3w_{cross}$  select  $R_D$ ,  $R_B$  and  $C_B$**

We use:  $\|G_c(w_c)\| = \frac{w_i}{w_{zc}} = \frac{K_{op} R_B}{R_D}$

And need to find  $K_{op}$ ,  $R_B$  and  $R_D$ :
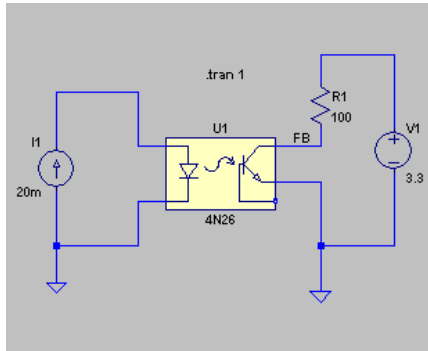
### Finding $K_{op}$

Select opto coupler 4N26 and make a small test circuit in LTspice shown on figure



$$Gain = \frac{i_C}{i_F}$$

$I_c$  = transistor collector current and  $i_F$  is diode current

The test results are:

$i_F$ current ->	1mA	10 mA	20 mA
V1=10V, R1=1k : Gain = $i_C/i_F$	0.8	0.67	0.49
V1=3.3 V, R1=100: Gain= $i_C/i_F$	0.8	0.67	0.56

So for an  $I_F$  in the range of 1mA to 10 mA the Gain is 0.7 and  $K_{op} = 0.7$

**NOTICE:**  $R_1$  is here identical with  $R_B$  so  $R_B$  must be in the range of 100 ohm..... when  $V_1 = 3.3$  V, If  $R_1$  is chosen larger ex. In the kohm range the Gain are much more dependent of  $i_F$ .

### Finding $R_D$

Here is assumed that the TL341 cathode voltage must be higher than 2.5 V and during this condition the current must be minimum 1 mA. So  $V_{Kmin} = 2.5$  V at  $i_F = 1$ mA assuming an opto coupler voltage of 1.1 V so  $V_{opto} = 1.1$  V.

Then  $R_D$  can be calculated

$$R_D \leq (V_o - V_{opto} - V_{K \min}) / i_{F \min}$$

$$R_D \leq (24 - 1.1 - 2.5) / 1mA$$

$R_D < 20 \text{ k}\Omega$ , but since  $R_B$  are selected next and it has to be in the 100 ohm region range to obtain a stabile gain of the opto coupler,  $R_D=200 \text{ ohm}$  – see next paragraph where  $R_B$  is found:

Finding  $R_B$

$$R_B = \frac{\|G_c(w_c)\| R_D}{K_{op}}$$

$$R_B = \frac{1.244 \cdot 200}{0.7}$$


**$R_B = 355 \text{ Ohm}$**

In literature reference 'Designing with the TL431' paragraph 6. is it stated that  $w_{zc}=w_c/3$  and it is selected that  $w_{pc} = 3 \cdot w_c$

Find  $C_B$

Select  $w_{pc} = 3 w_c$  and  $w_{pc} = 1/(C_B R_B)$ . Here  $R_B$  was calculated to  **$R_B=355 \text{ Ohm}$**  with  $w_c = 20000 \text{ rad/s}$   $C_B$  is found to be  **$C_B = 47 \text{ nF}$** .

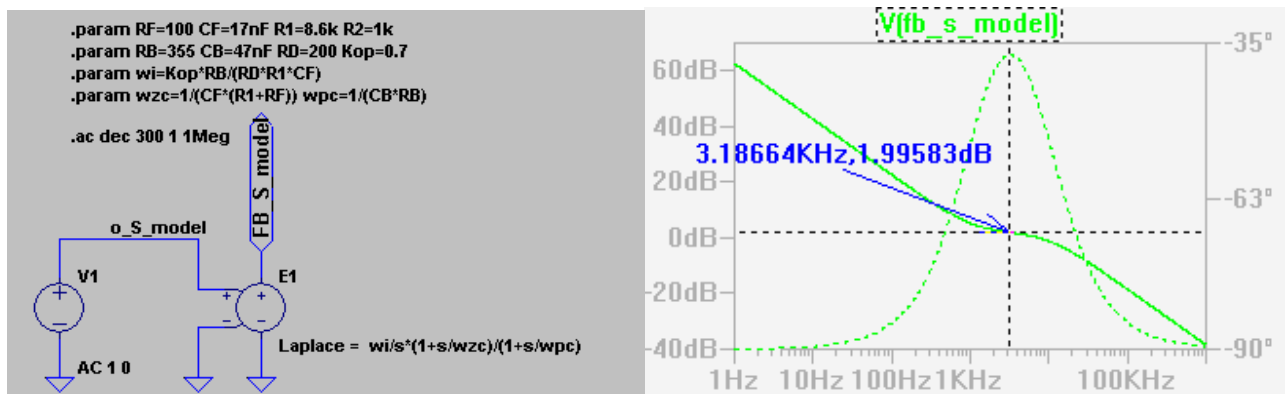The compensator is now implemented in LT spice  $\tilde{v}_{FB} / \tilde{v}_o$  :





The function shows the desired Gain of 2dB at the cross over frequency 3.187 kHz.

## Summary

So all capacitors and resistors and  $K_{op}$  are now found

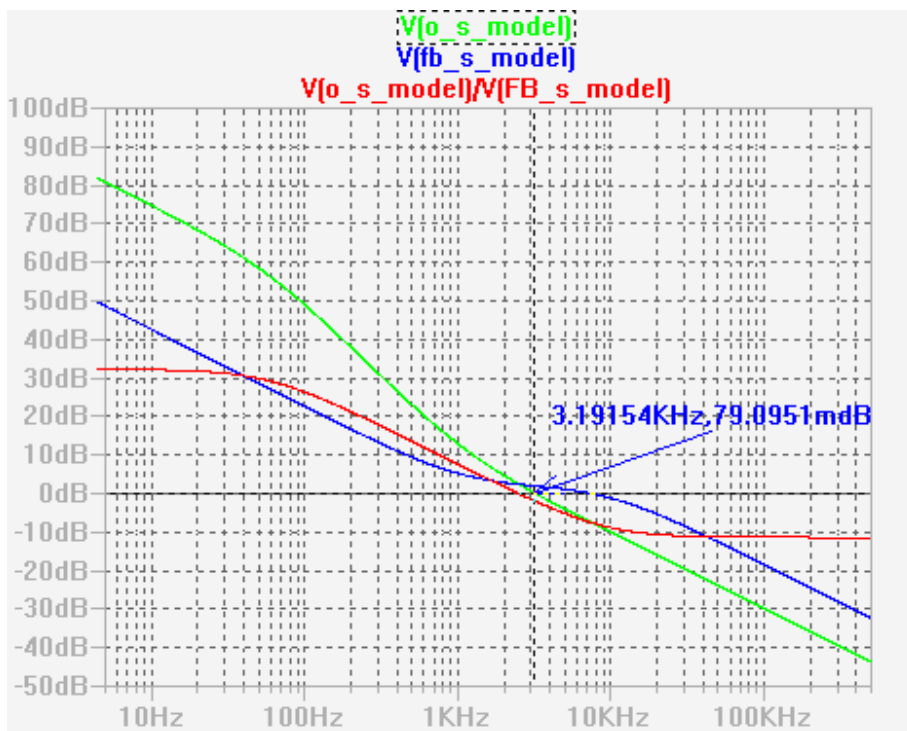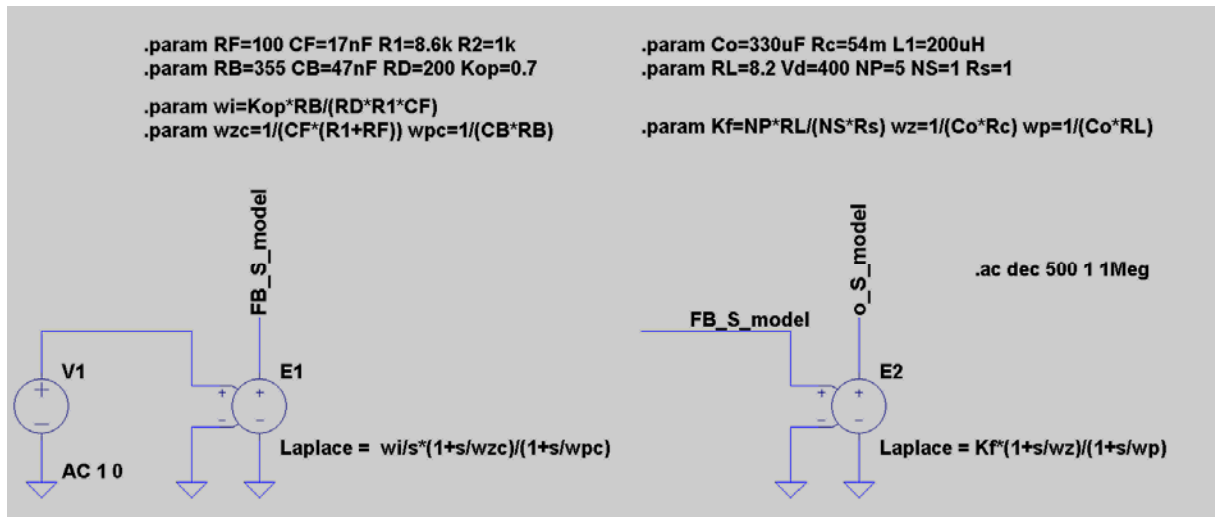**$R_F = 100 \text{ Ohm}$   $C_F = 17 \text{ nF}$   $R_1 = 8.6 \text{ k}\Omega$   $R_2=1\text{k}\Omega$   $R_B = 355 \text{ Ohm}$   $C_B = 47 \text{ nF}$   $R_D= 200 \text{ Ohm}$   $K_{op}=0.7$**

The total open loop  $T_{OL}$  function response is now modeled and calculated.




Green line:  $T_{OL}$ , Red line: Forward converter model, Blue line: Compensator model

It is noticed that the green line showing the response of  $T_{OL}$  have a crossover frequency at 3.1915kHz close to the desired 20000 rad/s.




### Answer 5: Simulate in LTspice


5a) Build Power circuit:

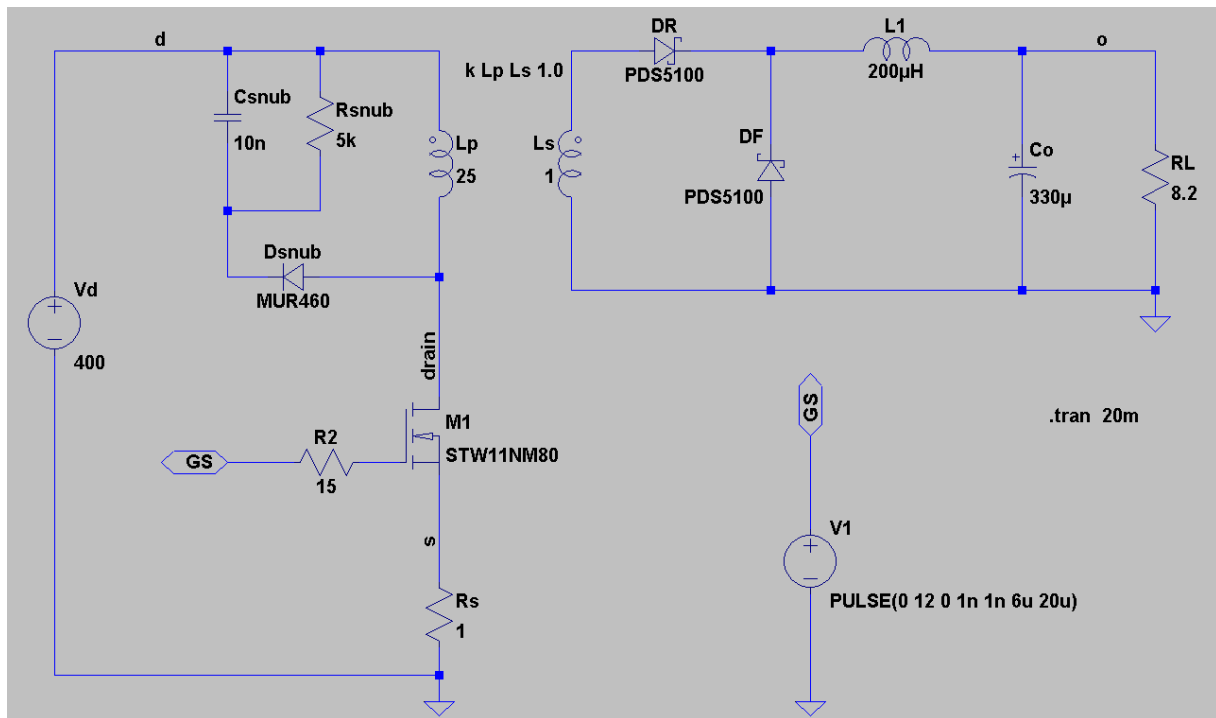


Simulation gives:

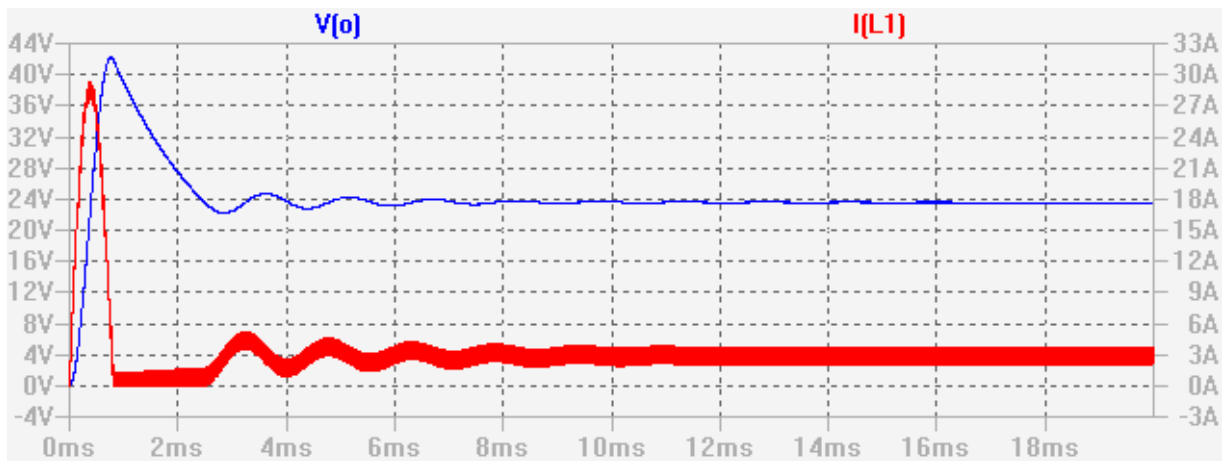


The non controlled behavior of converter is as expected and the  $V(o) \sim 24$  V at a duty cycle of  $D=0.3$ .

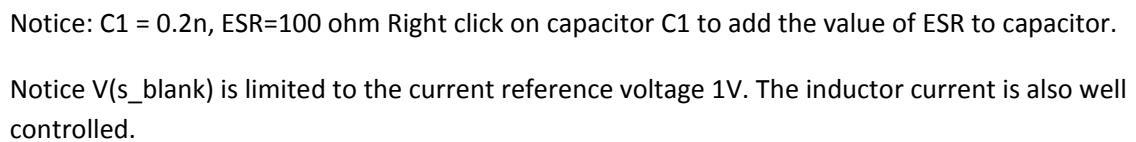[illegible]

5c) Build the controller:

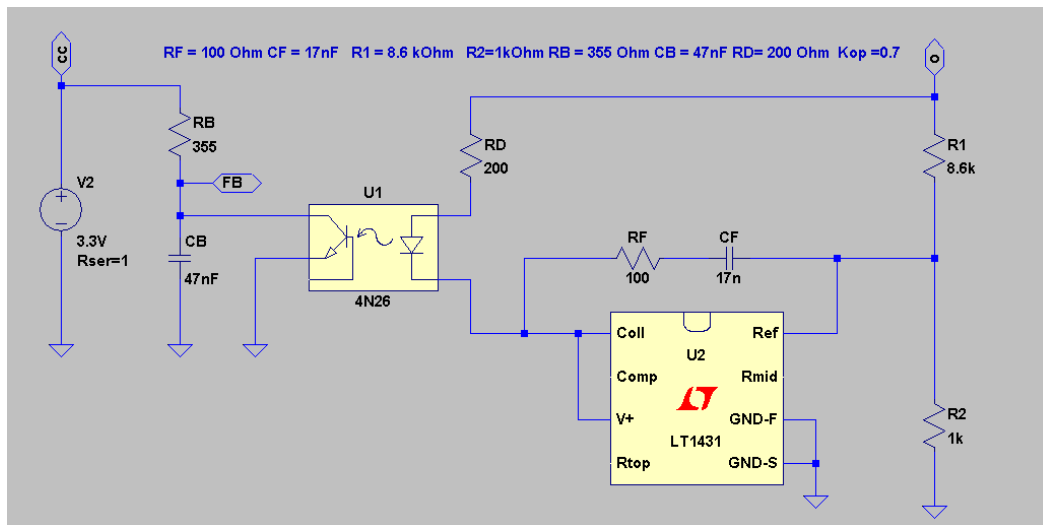

### 5d) Simulate converter

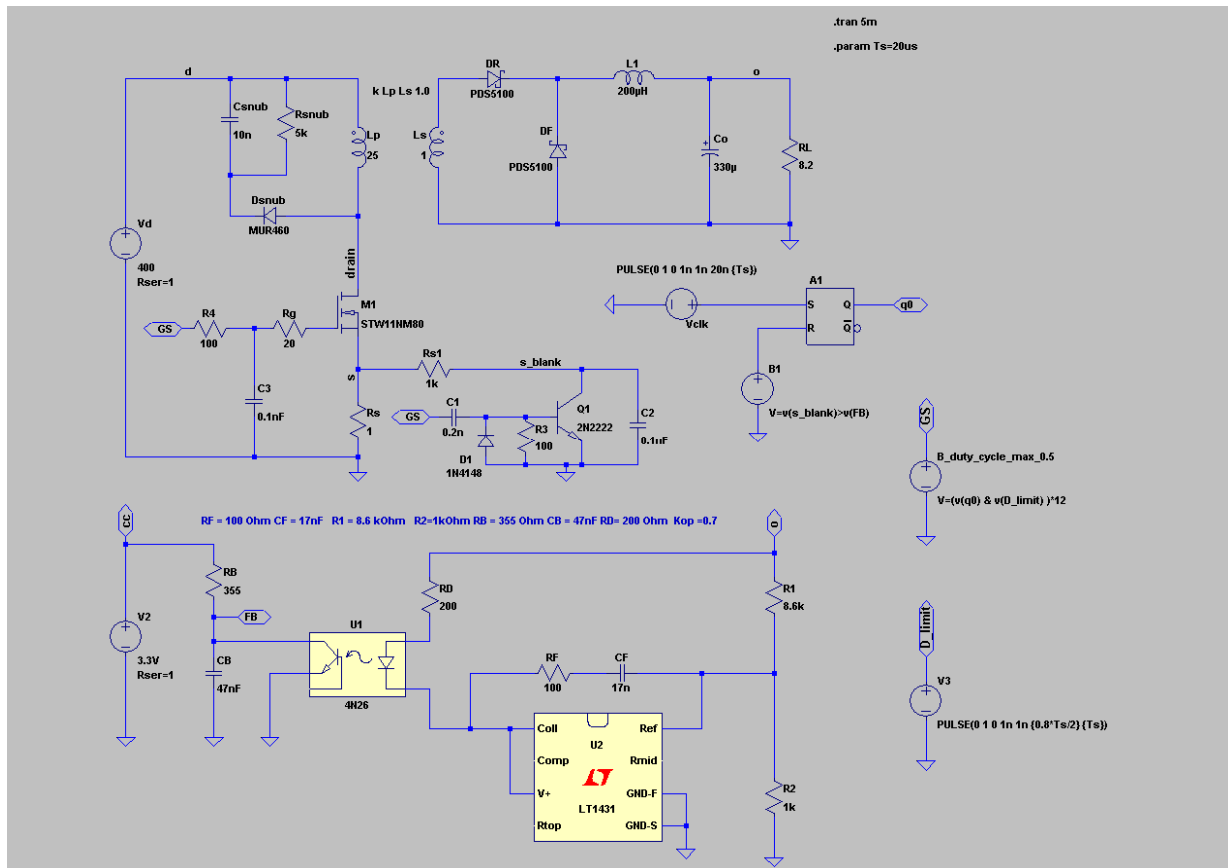

Plots of  $v(o)$  and  $i(L1)$  and  $v(FB)$

