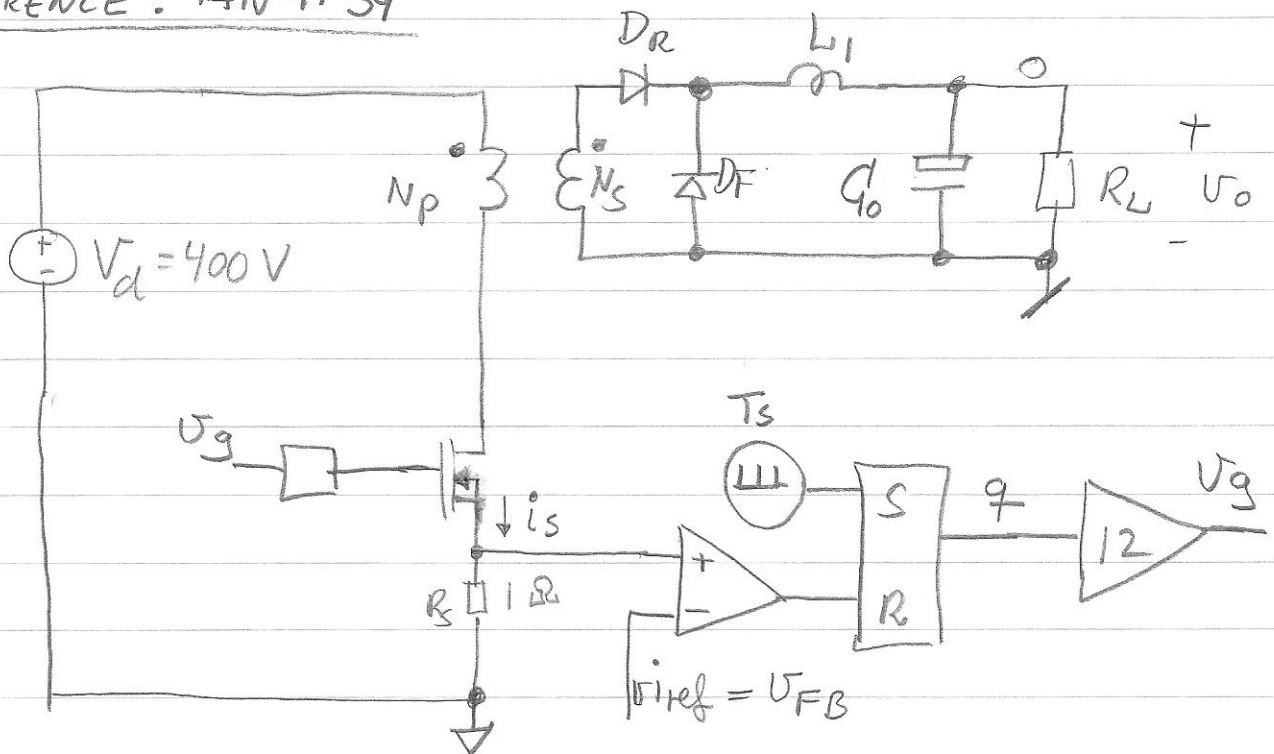


Problem 3 lecture

REFERENCE: AN4134



Spec: $V_o = 24V$

$T_s = 20\mu s$


$L_1 = 200\mu H$

$P_o = 70W$

$C_o = 300\mu F$

$N_P/N_S = 5$

$\omega_{cross} = 20000 \text{ rad/s}$

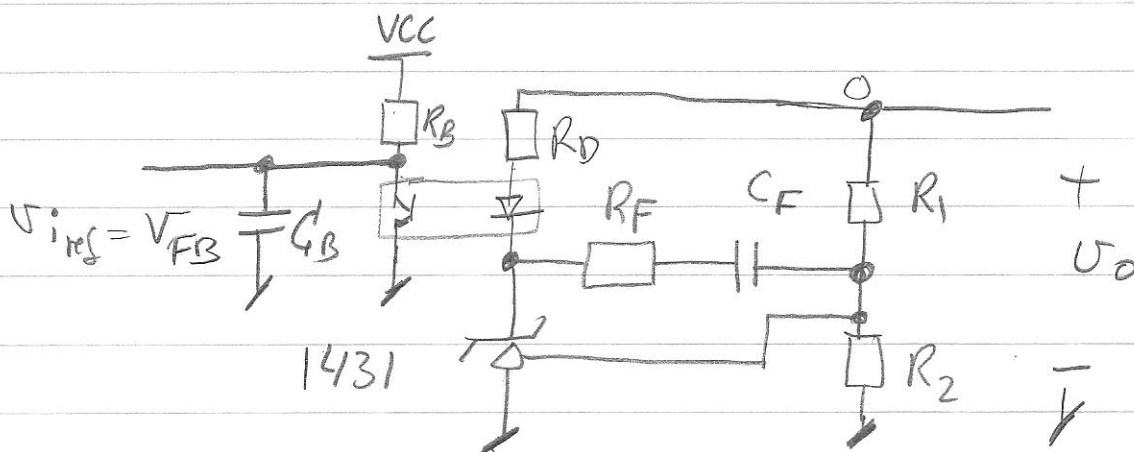

0: Sketch plot of G_{vc}

1: Select value of $R_1 + R_2$

2: Find desired gain at

$$\omega_{cross} \quad \left(\text{Gain-}\omega_{cross} \sim K_{op} \frac{R_B}{R_D} \right)$$

3: Find $\omega_{zc} = \omega_{cross} / 3$

Select R_F and C_F

4: Find $\omega_{pc} = 3 \omega_{cross}$

Select R_D, R_B and C_B

5: Simulate in LTSpice

a) Build power circuit

b) Build current controller

c) Build controller


d) Simulate the converter.

Specification: $C_o = 300\mu\text{F} \rightarrow 330\mu\text{F}$, $L_1=200\mu\text{H}$, $R_L=8.2\ \Omega$, $V_d=400$, $N_P/N_S=5$, $V_o = 24\ \text{V}$

$\omega_{\text{cross}} = 20000\ \text{rad/s}$

Answer 0: Sketch plot of G_{vc}

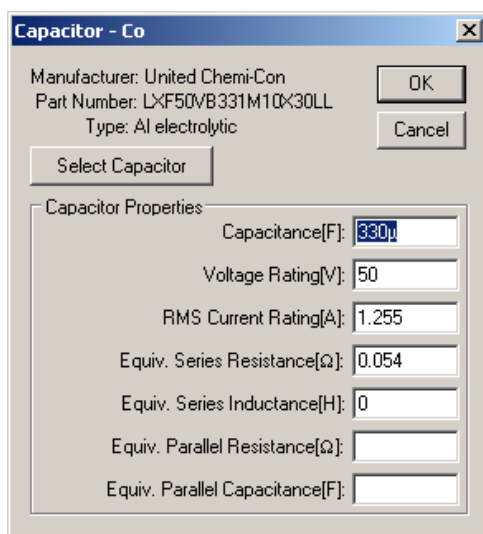Select a capacitor from the list of capacitors the nearest standard capacitance to $300\mu\text{F}$ is $330\ \mu\text{F}$, notice have to look out for RMS current rating is not exceeded.





$R_c = 54\text{m}\Omega$

R_s : Shunt resistor value used to measure the current of the transistor is selected to be:

$R_s = 1\ \Omega$

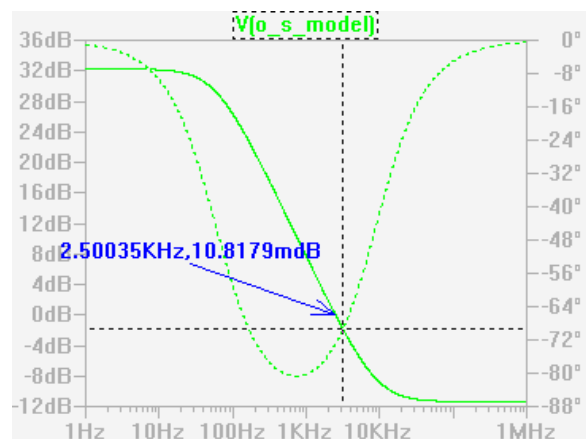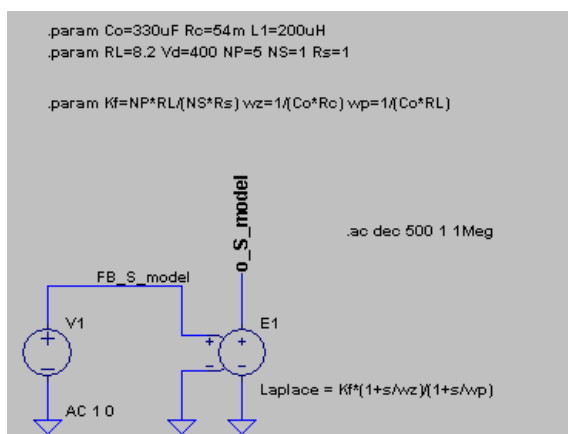Forward converter model implemented in LT spice $G_{vc} = \tilde{v}_o / \tilde{v}_{FB}$:



At 1 Hz the gain is 32.2 dB and at 2.5kHz (15707 rad/s) the gain is ~0 dB.

At $\omega_c = 3.183$ kHz (20000 rad/s) the gain is -1.9 dB and the phase is -70 deg.

Answer 1: Find R1 and R2

We know that Vref inside the TL431 is 2.5 V and the output voltage is $V_o = 24$ V. R2 is selected to be **R2=1kOhm** and the current of R2 is then 2.5 mA. From the voltage divider equation R1 is determined:

$$2.5V = 24V \frac{R_2}{R_1 + R_2}$$

R1 is found to be **R1 = 8.6 kOhm**.

Answer 2: Find desired gain at ω_{cross}

Compensator design type II.

The compensator function is:


$$G_c = \frac{\tilde{v}_{FB}}{\tilde{v}_o} = -\frac{w_i}{s} \frac{1 + s / w_{zc}}{1 + s / w_{pc}}$$

$$w_i = \frac{K_{op} R_B}{R_D R_1 C_F}$$

$$w_{zc} = \frac{1}{(R_1 + R_F) C_F}$$

$$w_{pc} = \frac{1}{R_B C_B}$$

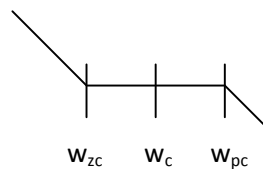The gain of G_c is sketched in the below plot and location of w_{zc} , w_c , w_{pc} is indicated:



Here w_c is located at the center so $w_c = \sqrt{w_{zc} w_{pc}}$ and from specifications $w_c = 20000$ rad/s and from forward converter transfer function the gain at $w_c = 20000$ rad/s calculated to be -1.9 dB. The gain of the compensator must then be $G_c(w_c) = 1.9$ dB to obtain an open loop gain $G_{op} = 1$ dB at $w_c = 20000$ rad/s.

Now we need to know what the gain of $G_c(w)$ at $w=w_c$ is and therefore $s = jw_c = j\sqrt{w_{zc} w_{pc}}$ is substituted into the G_c function.

$$G_c(w_c) = -\frac{w_i}{j\sqrt{w_{zc} w_{pc}}} \frac{1 + j\sqrt{\frac{w_{pc}}{w_{zc}}}}{1 + j\sqrt{\frac{w_{zc}}{w_{pc}}}}$$

$$\|G_c(w_c)\| = \frac{w_i}{\sqrt{w_{zc} w_{pc}}} \frac{\sqrt{1 + \frac{w_{pc}}{w_{zc}}}}{\sqrt{1 + \frac{w_{zc}}{w_{pc}}}}$$

And this is reduced to the result:

$$\|G_c(w_c)\| = \frac{w_i}{w_{zc}}$$

If $R_F \ll R_1$ then

$$\|G_c(w_c)\| = \frac{w_i}{w_{zc}} = \frac{K_{op} R_B}{R_D}$$

We need to find K_{op} , R_B and R_D , remember $\|G_c(w_c)\| = 1.9$ dB $\|G_c(w_c)\| = 1.244$

Answer 3: Find $w_{zc} = w_{cross}/3$ select R_F and C_F

Select $R_F = 100$ Ohm and with $w_{zc} = w_c/3$ and $w_{zc} = 1/((R_F + R_1) * C_F)$ then $C_F = 3/(w_c(R_F + R_1))$ and C_F is found to be $C_F = 17$ nF.


Answer 4: Find $w_{pc} = 3w_{cross}$ select R_D , R_B and C_B

We use: $\|G_c(w_c)\| = \frac{w_i}{w_{zc}} = \frac{K_{op} R_B}{R_D}$

And need to find K_{op} , R_B and R_D :

Finding K_{op}

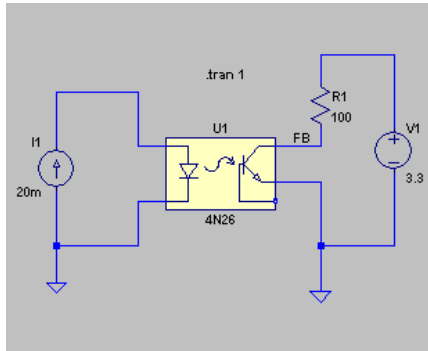Select opto coupler 4N26 and make a small test circuit in LTspice shown on figure



$$Gain = \frac{i_C}{i_F}$$

I_c = transistor collector current and i_F is diode current

The test results are:

i_F current ->	1mA	10 mA	20 mA
V1=10V, R1=1k : Gain = i_C/i_F	0.8	0.67	0.49
V1=3.3 V, R1=100: Gain= i_C/i_F	0.8	0.67	0.56

So for an I_F in the range of 1mA to 10 mA the Gain is 0.7 and $K_{op} = 0.7$

NOTICE: R1 is here identical with R_B so R_B must be in the range of 100 ohm..... when V1 = 3.3 V, If R1 is chosen larger ex. In the kohm range the Gain are much more dependent of i_F .

Finding R_D

Here is assumed that the TL341 cathode voltage must be higher than 2.5 V and during this condition the current must be minimum 1 mA. So $V_{Kmin} = 2.5$ V at $i_F = 1$ mA assuming an opto coupler voltage of 1.1 V so $V_{opto} = 1.1$ V.

Then R_D can be calculated

$$R_D \leq (V_o - V_{opto} - V_{K \min}) / i_{F \min}$$

$$R_D \leq (24 - 1.1 - 2.5) / 1mA$$

$R_D < 20 \text{ k}\Omega$, but since R_B are selected next and it has to be in the 100 ohm region range to obtain a stable gain of the opto coupler, $R_D = 200 \text{ ohm}$ – see next paragraph where R_B is found:

Finding R_B

$$R_B = \frac{\|G_c(w_c)\| R_D}{K_{op}}$$

$$R_B = \frac{1.244 \cdot 200}{0.7}$$


$R_B = 355 \text{ Ohm}$

In literature reference 'Designing with the TL431' paragraph 6. is it stated that $w_{zc} = w_c / 3$ and it is selected that $w_{pc} = 3 \cdot w_c$

Find C_B

Select $w_{pc} = 3 w_c$ and $w_{pc} = 1 / (C_B R_B)$. Here R_B was calculated to **$R_B = 355 \text{ Ohm}$** with $w_c = 20000 \text{ rad/s}$ C_B is found to be **$C_B = 47 \text{ nF}$** .

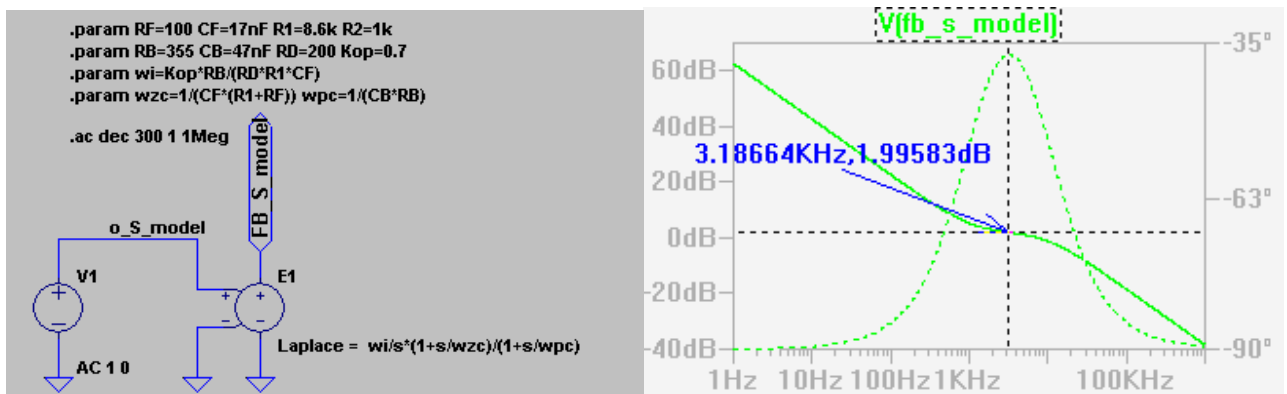The compensator is now implemented in LT spice $\tilde{v}_{FB} / \tilde{v}_o$:





The function shows the desired Gain of 2dB at the cross over frequency 3.187 kHz.

Summary

So all capacitors and resistors and K_{op} are now found

$R_F = 100 \text{ Ohm}$ $C_F = 17 \text{ nF}$ $R_1 = 8.6 \text{ k}\Omega$ $R_2 = 1 \text{ k}\Omega$ $R_B = 355 \text{ Ohm}$ $C_B = 47 \text{ nF}$ $R_D = 200 \text{ Ohm}$ $K_{op} = 0.7$

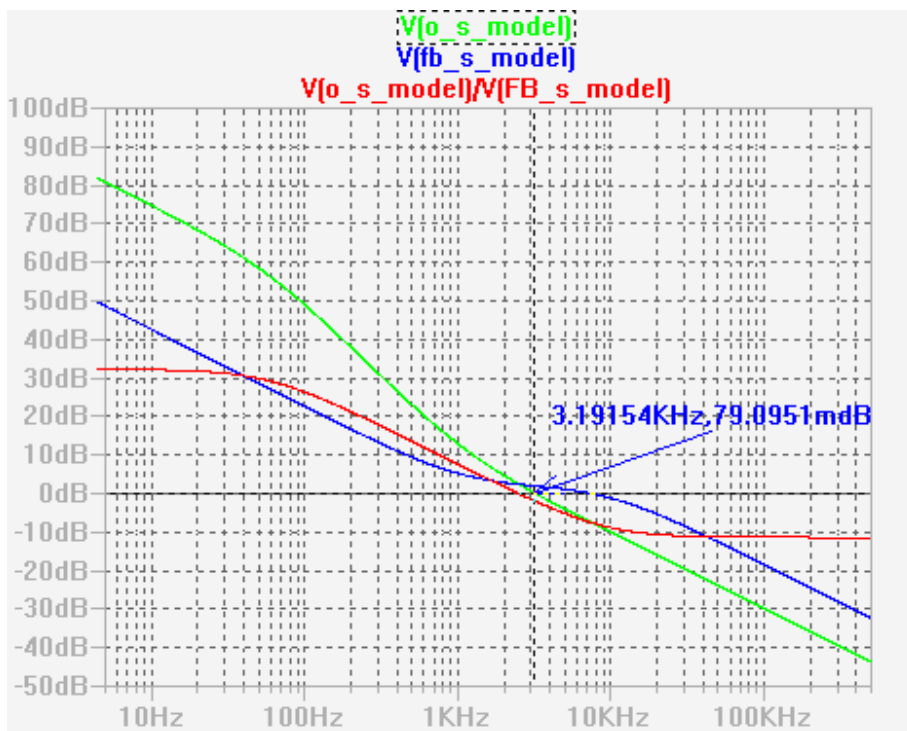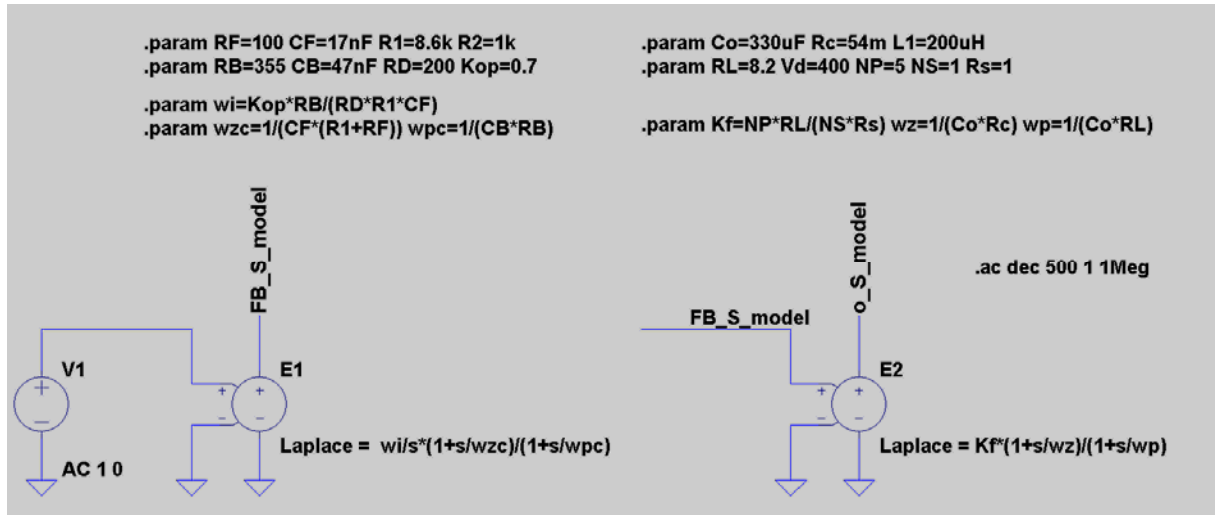The total open loop T_{OL} function response is now modeled and calculated.




Green line: T_{OL} , Red line: Forward converter model, Blue line: Compensator model


It is noticed that the green line showing the response of T_{OL} have a crossover frequency at 3.1915kHz close to the desired 20000 rad/s.

Answer 5: Simulate in LTspice

5a) Build Power circuit:


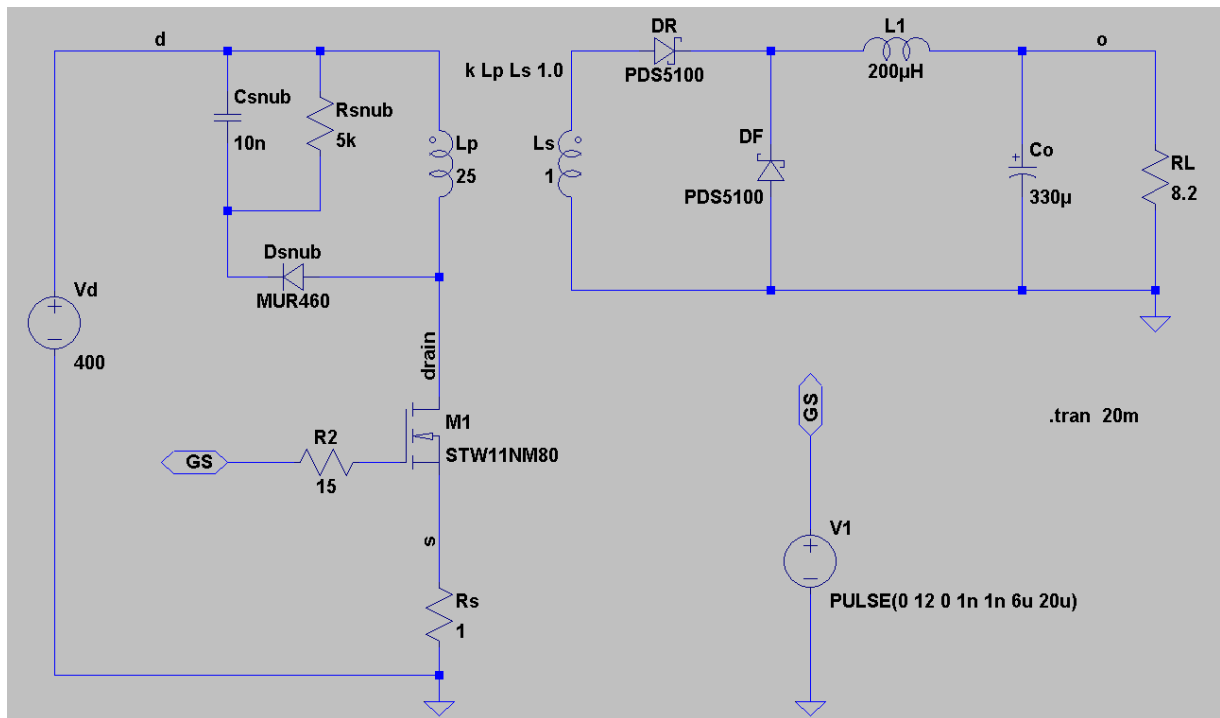


Simulation gives:

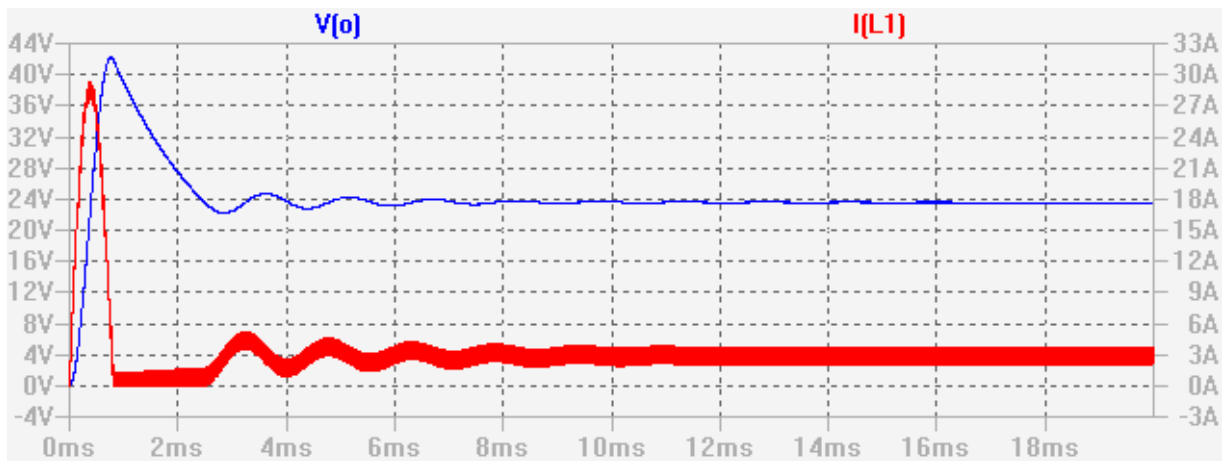

The non controlled behavior of converter is as expected and the $V(o) \sim 24\ V$ at a duty cycle of $D=0.3$.


5b) Build current controller:

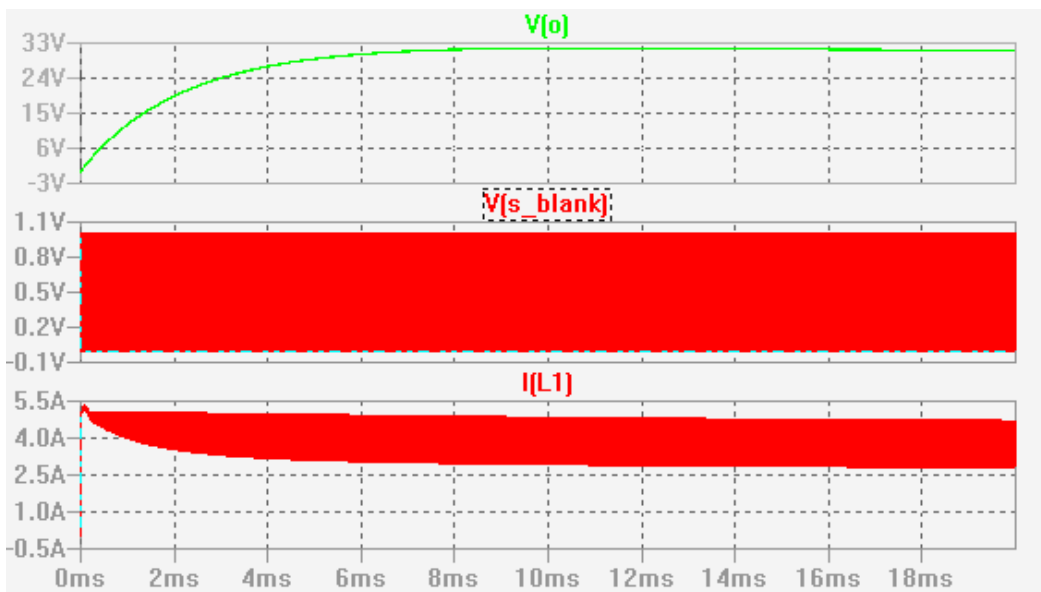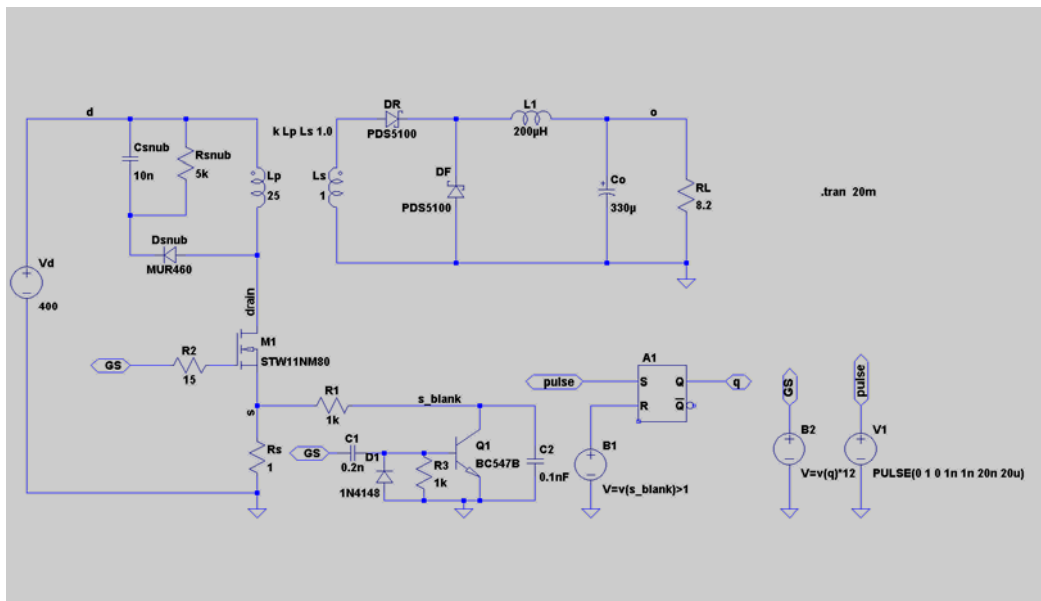


Notice: $C1 = 0.2n$, $ESR = 100 \text{ ohm}$ Right click on capacitor C1 to add the value of ESR to capacitor.

Notice $V(s_blank)$ is limited to the current reference voltage 1V. The inductor current is also well controlled.

5c) Build the controller:

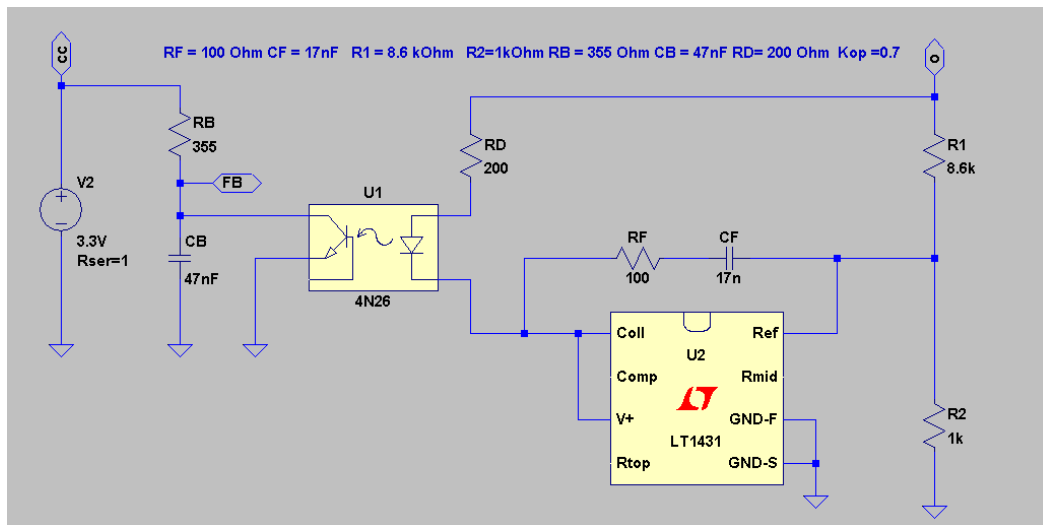

5d) Simulate converter

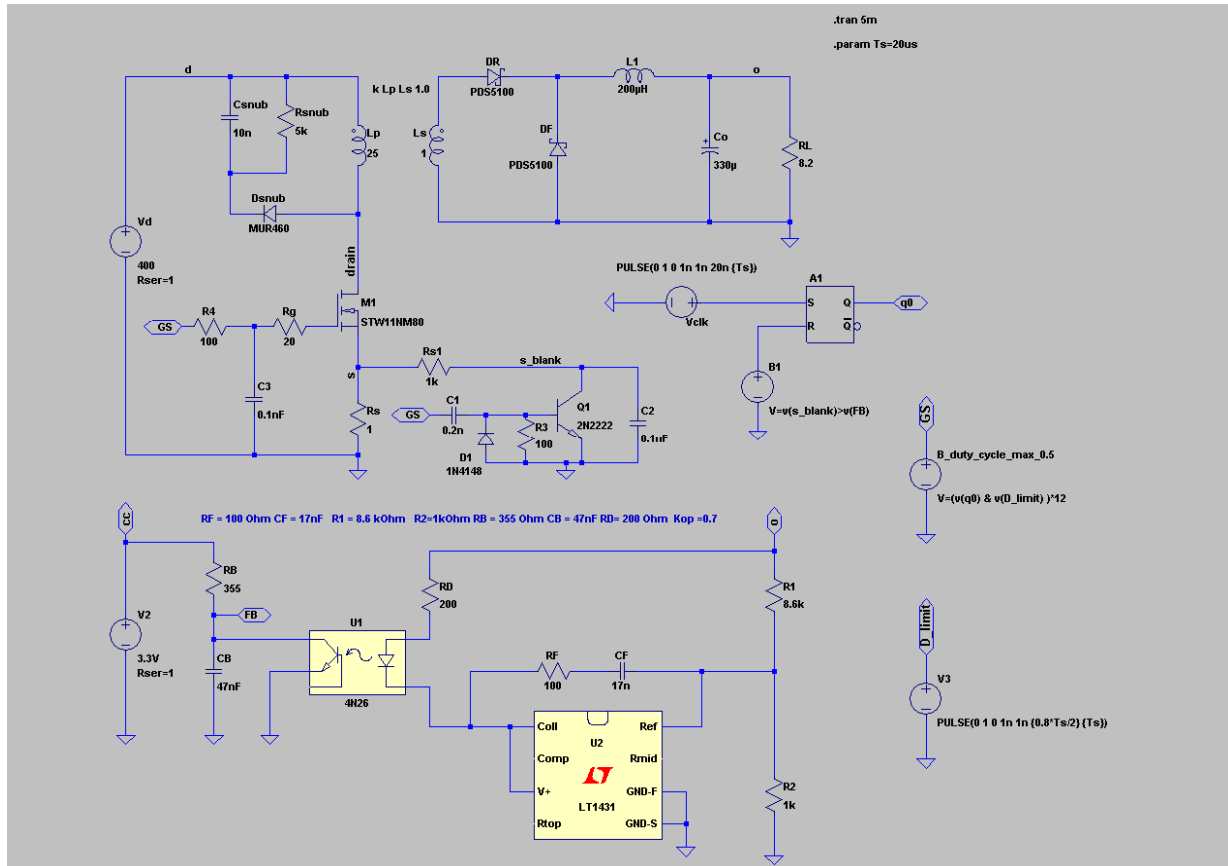

Plots of $v(o)$ and $i(L1)$ and $v(FB)$

