

Adrian

Study number: 2013 70 14	Programme: EPSH/PED/WPS
Evaluation subject: High Voltage Engineering and Design of Switch Mode Converters Friday 27 January at 9:30-13:30	

Please write your study no. on all pages. Do not write your name as your evaluation is anonymous!

Total number of pages, including this page: 10

Please, only write on one side of the papers that you hand in.

NB! Your paper must be easy to read. If this is not the case, your paper may be evaluated as "not passed".

***All usual aids are allowed (notes, books, tables, calculator and PC).
You are not allowed to communicate amongst each other or with the outside world which means that the use of mobile phone, Wi-Fi, internet, email is not allowed.***

You are allowed to take the examination questions with you. But you are NOT allowed to take them with you if you leave the room before the examination has ended.

HV: 44%

Problem 7:

1) it is given by $\eta = \frac{C_1}{C_1 + C_2} = \frac{1}{1 + C_2/C_1}$ Setor b
↓

that the higher value for C_2 the more efficient the generator is.

Therefore we always design it to be much bigger than C_2 .

Otherwise, lower efficiency is obtained. and also C_1 must be big enough to be able to supply the load.

2) $C_1 = 20 \cdot 10^{-9} \text{ F}$ and $C_2 = 2 \cdot 10^{-9} \text{ F}$

A standard switching impulse is

the 250/2500 μs impulse. (T_1/T_2)

From table in book this impulse has

$$\frac{1}{\alpha_1} = 2877 \mu\text{s} \quad \frac{1}{\alpha_2} = 104 \mu\text{s}$$

$$\alpha_1 = 347,584 \frac{1}{\text{s}} \quad \alpha_2 = 9615,4 \frac{1}{\text{s}}$$

$$\text{so } R_1 = \frac{1}{2C_2} \left[\left(\frac{1}{\alpha_1} + \frac{1}{\alpha_2} \right) - \sqrt{\left(\frac{1}{\alpha_1} + \frac{1}{\alpha_2} \right)^2 - \frac{4(C_1 + C_2)}{\alpha_1 \alpha_2 C_1}} \right] = 57,4 \text{ k}\Omega$$

$$R_2 = \frac{1}{2(C_1 + C_2)} \left[\left(\frac{1}{\alpha_1} + \frac{1}{\alpha_2} \right) + \sqrt{\left(\frac{1}{\alpha_1} + \frac{1}{\alpha_2} \right)^2 - \frac{4(C_1 + C_2)}{\alpha_1 \alpha_2 C_1}} \right] = 130,2 \text{ k}\Omega$$

Studienr. 201370141

Problem 1:

$$3) V(t) = \frac{V_0}{k} \left(\frac{1}{\alpha_2 - \alpha_1} \right) (e^{-\alpha_1 t} - e^{-\alpha_2 t})$$


$$V_0 = 50 \text{ kV}$$

10

$$k = R_1 \cdot C_2 = 1,148 \cdot 10^{-4}$$

so:
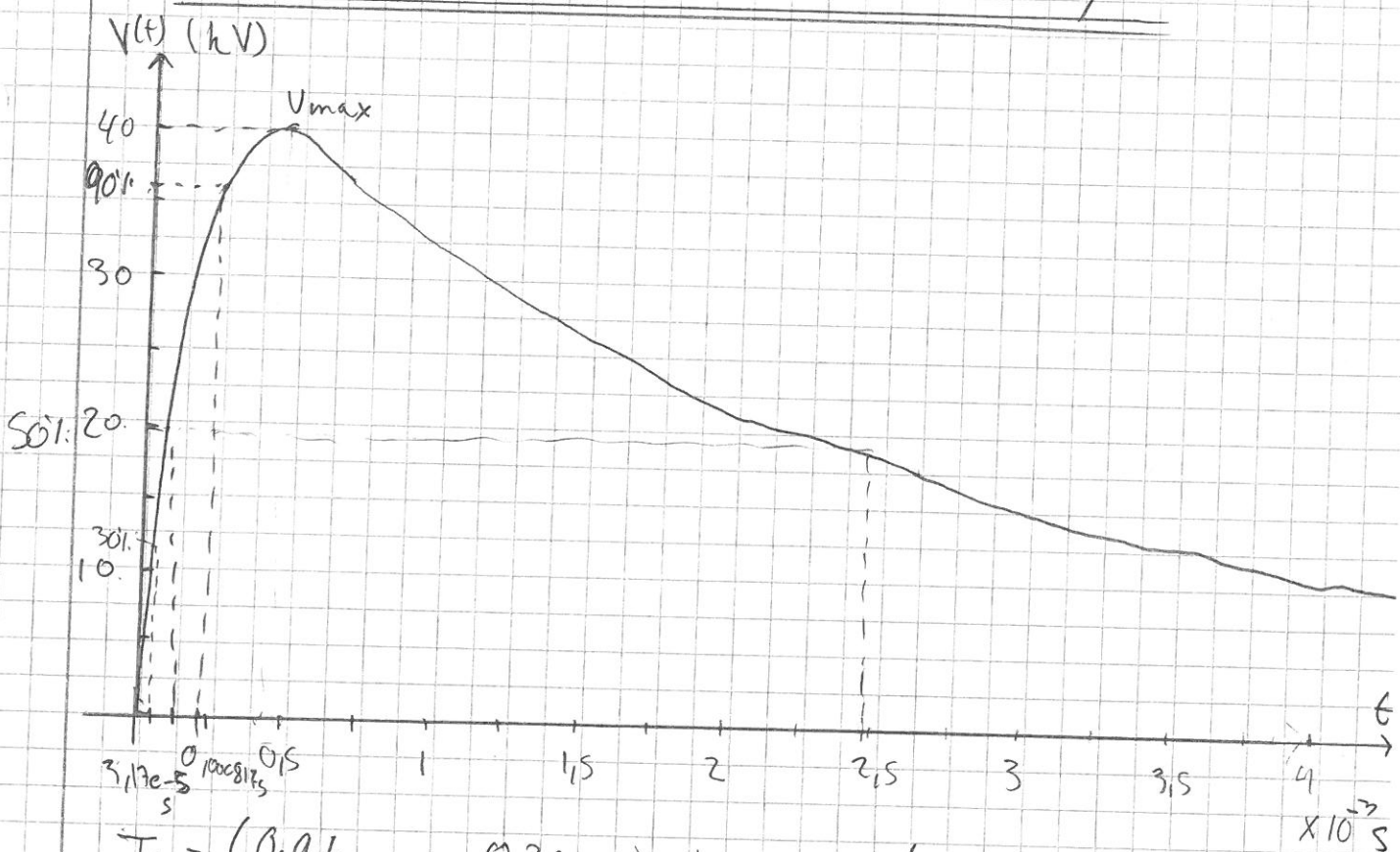
$$V(t) = 46982 \cdot (e^{-347,584t} - e^{-9615,4t})$$



$$T_1 = (0,9 t_{\max} - 0,3 t_{\max}) \cdot 1,67 \quad t_{\max}: \text{when } V(t) = V_{\max}$$

T_2 is the time when at falling it reaches $0,5 \cdot V_{\max}$

$$V_{\max} = 40 \text{ kV}$$

$$0,9 \cdot V_{\max} \Rightarrow t_{0,9} = 0,000184 \text{ s}$$

$$0,3 V_{\max} \Rightarrow t_{0,3} = 3,173 \cdot 10^{-5} \text{ s}$$

$T_1 = 2,5 \cdot 10^{-4} \text{ s}$ which is within $\pm 20\%$ off $250 \mu\text{s}$ so ok!

$T_2 = 2,3 \cdot 10^{-3} \text{ s}$ $\pm 60\%$ of $2500 \mu\text{s}$ so ok!

S. 2 2/10

Student: 20 13 70 14

Exercise 2:

1) Choose DC since insulation under DC, the voltage on the insulation will be dependant on the resistivity. resistivity is opposite of conductivity, so DC current is ok!

$$2) \text{ So } R = \frac{500 \text{ V}}{20 \cdot 10^{-9} \text{ A}} = 25 \cdot 10^{10} \Omega$$

$$\text{and } L = 2 \cdot 10^{-3} \text{ m}, A = 80 \cdot 10^{-3} \text{ m} \cdot 80 \cdot 10^{-3} \text{ m} = 0.0064 \text{ m}^2$$

$$\text{So } \rho = R \cdot \frac{A}{L} = \underline{\underline{8 \cdot 10^{10} \Omega \cdot \text{m}}}$$

3)

$$\epsilon_{oil} = 2$$

$$\epsilon_{dielectr} = 4$$

$$d_{tank} = 10 \cdot 10^{-3} \text{ m}$$

$$d_{diel} = 2 \cdot 10^{-3} \text{ m}$$

$$U = 18 \text{ kV}$$

before inserting dielectric:

$$C_{oil} = \epsilon \cdot \frac{A}{d} = 2 \cdot \frac{1}{10 \cdot 10^{-3} \text{ m}} \cdot A$$

$$Q = C_{oil} \cdot U = 200 \cdot A \cdot 18 \cdot 10^3 \text{ V} = 3600 \text{ kC} \cdot A$$

$$E = \frac{Q}{\epsilon_{oil} \cdot A} = \frac{3600 \cdot 10^3 \text{ C} \cdot A}{2 \cdot A} = \underline{\underline{1800 \frac{\text{kV}}{\text{m}}}} \quad \text{now}$$

after inserting:

$$\begin{array}{c} \text{---} C_{oil} \\ \text{---} C_{diel} \end{array}$$

$$\Rightarrow \frac{V_{oil}}{V_{diel}} = \frac{\epsilon_{diel}}{\epsilon_{oil}} = 2 \Leftrightarrow$$

$$V_{oil} = 2 \cdot V_{diel}$$

$$\text{So: } V_{oil} + V_{diel} = 18 \cdot 10^3 \text{ V}$$

$$\text{|| } 2V_{diel} + V_{diel} = 18 \cdot 10^3 \text{ V} \Leftrightarrow V_{diel} = 6000 \text{ V}$$

Student: 20137014

Exercise 2:

3) $V_{\text{diel}} = 600 \text{ kV}$

$$C_{\text{diel}} = 4 \cdot \frac{1}{2 \cdot 10^{-3}} \text{ A} = 2000 \cdot \text{A}$$

$$E = \frac{Q_{\text{diel}}}{E \cdot A} = 5400 \frac{\text{hV}}{\text{m}}$$

Increase E field, due to the fact that the capacitance increases when dielectric is put in the medium.

4) $C_x = C_N \cdot \frac{R_g}{R_3} = 37,2 \cdot 10^{-12} \text{ F} \cdot \frac{652 \Omega}{242 \Omega} = 1,002 \cdot 10^{-10} \text{ C}$

$$P = \omega \cdot C_x \tan \delta \cdot V^2 \quad (\text{assume power frequency } 50 \text{ Hz})$$
$$= 2\pi 50 \cdot 1,002 \cdot 10^{-10} \text{ C} \cdot 0,006 \cdot (200 \cdot 10^3 \text{ V})^2 = 7,55 \text{ W}$$

Exercise 1) q_0 is the apparent charge but it cannot be equal to the amount of charge locally involved in the PD since it cannot be measured directly.

2) X-axis: complete cycle of the applied voltage.

Y-axis: PD charge magnitude (detected magnitudes)


3) PD's are located at zero crossing of voltage therefore this must be internal PD's (also considering high $V = 30 \text{ kV}$)

Exercise 3

4) Tells us something about the quality of the dielectric.
if internal PD's are present this means small blasters or cavities in the dielectric. \rightarrow very fast current if breakdown \rightarrow degrade the quality of dielectric if happens repeatedly.


Exercise 4

A) When switch is ON:

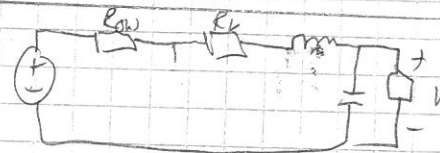

$$V_L(t) = V_g(t) - i_L \cdot (R_{ow} + R_L) - V_o(t)$$

Switch off:

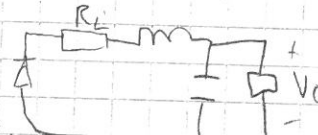

$$V_L = -V_o(t) - V_D \cdot i(t) - R_L \cdot i_L(t) \quad \text{So:}$$

averaging inductor voltage gives (1 Ts):

$$\langle V_L(t) \rangle_{T_s} = [\langle V_g(t) \rangle - \langle i_L(t) \rangle \cdot (R_{ow} + R_L) - \langle V_o(t) \rangle] \cdot D$$

$$- [\langle V_o(t) \rangle + V_D + \langle i_L(t) \rangle \cdot R_L] \cdot (1-D) = 0 \quad \leftarrow \text{voltage-sec - balance (Steady state)}$$

$$\Downarrow D = \frac{V_o + V_D + I_L \cdot R_L}{V_g - I_L(R_{ow} + R_L) + V_o + I_L \cdot R_L} \quad I_L = I_o \quad \text{So:}$$

$$D = \frac{5V + 0,4V + 20A \cdot 0,04\Omega}{12V - 20A \cdot (0,04\Omega + 0,12\Omega) + 0,4V + 20A \cdot 0,04\Omega} = 0,62$$

$$m_1 = \frac{V_{con}}{L} = \frac{V_g - I_o \cdot (R_{ow} + R_L) - V_o}{L} = 3,167 \cdot 10^5$$

$$m_2 = \frac{V_{off}}{L} = \frac{-V_o - V_D - I_o \cdot R_L}{L} = -5,167 \cdot 10^5$$

S.S at 10

20137014

Exercise 4:

B) again on, off - stages!

Q on: $V_L(t) = V_g(t) - I_L(t) (R_{on} + R_L) - V_o(t)$

$I_C(t) = I_L(t) - \frac{V_o(t)}{R_o}$, $I_g(t) = I_L(t)$

Q off: $V_L(t) = -V_o(t) - V_D - I_L(t) \cdot R_L$

$I_C(t) = I_L(t) - \frac{V_o(t)}{R}$, $I_g(t) = 0$

Inductor: linearize and perturbate:

$\langle X(t) \rangle = X + \hat{x}$ i don't write $\hat{x}'(t)$
due to case:

$\frac{D'}{(1-D)-\hat{d}} V_L + \hat{V}_L = (D + \hat{d}) [V_g + \hat{V}_g - (I_L + \hat{I}_L)(R_{on} + R_L) - V_o - \hat{V}_o]$
 $\Rightarrow (D' - \hat{d}) [V_o + \hat{V}_o + V_D + (I_L + \hat{I}_L) R_L]$

AC: $\hat{x} \cdot \hat{y} \rightarrow 0$, $X \rightarrow 0$ so

$\hat{V}_L = D \cdot \hat{V}_g - D \cdot \hat{I}_L (R_{on} + R_L) - D \cdot \hat{V}_o + \hat{d} V_g - \hat{I}_L (R_{on} + R_L) \hat{d}$
 $- \hat{d} V_o - D' \hat{V}_o - D' \hat{I}_L R_L + \hat{d} V_o + V_D \hat{d} + \hat{d} I_L R_L$

I'm not gonna reduce it :)

Capacitor: is equal in both on and off

So: $\langle I_C \rangle = \langle I_L \rangle - \langle \frac{V_o}{R_o} \rangle$

$I_C + \hat{I}_C = I_L + \hat{I}_L - \frac{V_o + \hat{V}_o}{R_o}$

AC: $\hat{I}_C = \hat{I}_L - \frac{\hat{V}_L}{R_o}$

Input current:

$\langle V_g \rangle = \langle I_L \rangle \cdot D \Leftrightarrow I_g + \hat{I}_g = (I_L + \hat{I}_L) \cdot (D + \hat{d})$

\Leftrightarrow AC: $\hat{I}_g = \hat{I}_L D + I_L \hat{d}$

Students: 20/3 70/4

Exercise 4

c) Stable operation is
 $|Z| < 1$ so for

$$M_a = 0,3 M_2$$

$$Z = - \frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}} = - \frac{1 - \frac{0,3 m_2}{m_2}}{\frac{D'}{D} + \frac{0,3 m_2}{m_2}} = - \frac{0,7}{\frac{1}{D} - 0,7}$$

this means that stable operation
is for $D < \frac{5}{7} \approx 0,71$

for $M_a = 0,5 m_2$

$$Z = - \frac{1 - \frac{0,5 m_2}{m_2}}{\frac{D'}{D} + \frac{0,5 m_2}{m_2}} = - \frac{0,5}{\frac{1}{D} - 0,5}$$

meaning that stable operation for
 $D < 1$ (all D)

d) we have, $G_{vc} = \frac{\hat{V}_0(s)}{\hat{I}_{control}}$ so:

$$\hat{I}_c(s) = \hat{I}_L(s) - \frac{V_0(s)}{R} \Leftrightarrow \hat{I}_L(s) = \left(sC + \frac{1}{R} \right) \cdot \hat{V}_0(s)$$


$$\Leftrightarrow \frac{\hat{V}_0(s)}{\hat{I}_L(s)} = \frac{\hat{V}_0(s)}{\hat{I}_{control}} = \frac{1}{sC + \frac{1}{R}} = G_{vc}$$

Student nr: 20137014


Exercise 5)

if i have

V_{Ao}

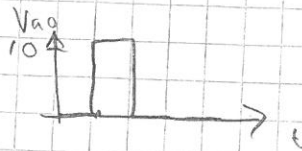


V_{Bo}

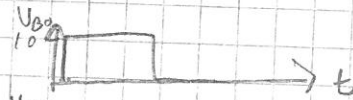

then

Common mode
is:

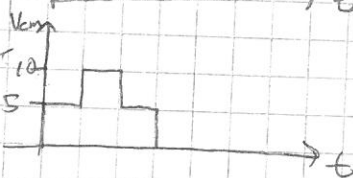

$$V_{cm} = \frac{V_{Ao} + V_{Bo}}{2}$$

- This is not good since it can destroy bearings in motor.
- Depending on the PWM signal it can create high leakage currents which are the bearing currents in the motor. The common mode voltage will give varying frequency component \Rightarrow not good in motor applications \Rightarrow hot spots in bearings.
- So switching actions will cause current pulses at the input of power supply. as see above, the V_{cm} has rectangular waveforms, and for high freq. $\frac{dV}{dt}$ and $\frac{di}{dt}$ is very short \Rightarrow harmonics

Student: 2013 70 14

a) $V_o = D \cdot V_g \cdot n \Leftrightarrow$

$$D = \frac{V_o}{V_g \cdot n} = \frac{12V}{400V \cdot \frac{160}{8}} = \underline{0,6}$$

$$n = \frac{N_s}{N_p}$$

b) $P = V_o \cdot I_o \Leftrightarrow I_o = \frac{70W}{12V} = 5,833A$

$$R_L = \frac{V_o}{I_o} = \frac{12V}{5,833A} = \underline{2,06 \Omega}$$

c) $\Delta I_{o,pa} = I_o \cdot 0,01 = 0,0583A$


$$\Delta I_{o,pp} = 2 \cdot \Delta I_{o,pa} = 0,1166A$$

$$T_{sw} = \frac{1}{100 \cdot 10^3 Hz} = 1 \cdot 10^{-5} s$$

$$L_o = \frac{V_o}{\Delta I_{err}} \cdot (1-D) \cdot T_s = \frac{12}{0,1166A} \cdot (1-0,6) \cdot 1 \cdot 10^{-5} s$$

$$= \underline{4,12 \cdot 10^{-4} H}$$

d) bode is plotted in matlab:

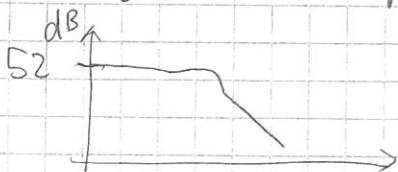

reading $G_{vco} = 52 dB$

again measuring on bode plot in matlab

gives $G_{vd}(1000 \cdot 2\pi \frac{rad}{s}) = 49,1 dB$

$$G_{vd-\omega_c} = 49,1 dB \quad \left. \vphantom{G_{vd-\omega_c}} \right\} G_{vd} = \frac{400}{4,1 \cdot 10^{-8} s^2 + 9,0002 \cdot s + 1}$$

To get ω_c as cross over then gain of

G_{vco} should be $G_{vco} = -49,1 dB$ which is:

$$|G_{vco}| = 10^{\frac{-49,1}{20}} = \underline{0,0035}$$

↑ quite high gain

5.9 at 10

2.5