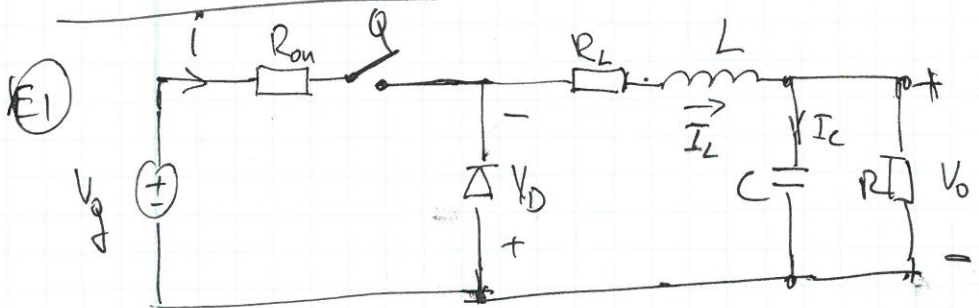


Exercise solution



~~Q~~ $Q_A = 1$ ($0 < t < DT_s$)

$$V_L(t) = V_g(t) - I_L(t)(R_{on} + R_L) - V_o(t)$$

$$I_C(t) = I_L(t) - \frac{V_o(t)}{R}$$

$$I_g(t) = I_L(t) \quad (0 < t < T_s)$$

$$V_L(t) = -V_o(t) - V_D + I_L(t)R_L$$

$$I_C(t) = I_L(t) - \frac{V_o(t)}{R}$$

$$I_g(t) = 0$$

Averaging over one switching period

$$\langle V_L(t) \rangle_{T_s} = [\langle V_g(t) \rangle - \langle I_L(t) \rangle (R_{on} + R_L) - \langle V_o(t) \rangle] \cdot D$$

$$- [\langle V_o(t) \rangle + V_D - \langle I_L(t) \rangle \cdot R_L] \cdot D'$$

$$\langle I_C(t) \rangle_{T_s} = \langle I_L(t) \rangle - \frac{\langle V_o(t) \rangle}{R}$$

$$\langle I_g(t) \rangle_{T_s} = \langle I_L(t) \rangle \cdot D$$

CORRECTION: last term in inductor voltage expression should also be with **minus!**

Accordingly, the inductor volt-second balance equations below need to be updated.

E2

~~$V_L(t)$~~

Inductor voltage perturbation & linearization

$$\begin{aligned}
 V_L + \hat{V}_L &= [V_g + \hat{V}_g - (I_L + \hat{I}_L)(R_{on} + R_L) - V_o - \hat{V}_o] \cdot (D + \hat{d}) - \\
 &= [V_o + \hat{V}_o + V_D - (I_L + \hat{I}_L)R_L] \cdot (D' - \hat{d}) = \\
 &= \cancel{V_g \cdot D} + \hat{V}_g \cdot D - \cancel{I_L \cdot (R_{on} + R_L) \cdot D} - \hat{I}_L \cdot (R_{on} + R_L) \cdot D - \cancel{V_o \cdot D} - \hat{V}_o \cdot D + \\
 &+ \cancel{V_g \cdot \hat{d}} + \hat{V}_g \cdot \hat{d} - \cancel{I_L \cdot (R_{on} + R_L) \cdot \hat{d}} - \hat{I}_L \cdot (R_{on} + R_L) \cdot \hat{d} - \cancel{V_o \cdot \hat{d}} - \hat{V}_o \cdot \hat{d} - \\
 &- \cancel{V_o \cdot D'} - \hat{V}_o \cdot D' - \cancel{V_D \cdot D'} + \cancel{I_L \cdot R_L \cdot D'} + \hat{I}_L \cdot R_L \cdot D' + \\
 &+ \cancel{V_o \cdot \hat{d}} + \hat{V}_o \cdot \hat{d} + \cancel{V_D \cdot \hat{d}} + \cancel{I_L \cdot R_L \cdot \hat{d}} + \hat{I}_L \cdot R_L \cdot \hat{d}
 \end{aligned}$$

DC:

$$0 = V_g \cdot D - I_L \cdot (R_{on} + R_L) \cdot D - \underbrace{V_o \cdot D - V_o \cdot D'}_{V_o} - V_D \cdot D' + I_L \cdot R_L \cdot D'$$

$$0 = V_g \cdot D - I_L \cdot (R_{on} + R_L) \cdot D - V_o - V_D \cdot D' + I_L \cdot R_L \cdot D'$$

$$\underline{V_o = V_g \cdot D - I_L \cdot (R_{on} + R_L) \cdot D - V_D \cdot D' + I_L \cdot R_L \cdot D'}$$

\Downarrow
 D (in steady state $I_L = I_D$)

E3

$$m_1 = \frac{V_g - I_L(R_{on} + R_L) - V_0}{L}$$

$$-m_2 = \frac{-V_0 - V_D + I_L \cdot R_L}{L}$$

b) inductor voltage ac component

$$\begin{aligned} \hat{V}_L = & \hat{V}_g \cdot D - \hat{I}_L \cdot (R_{on} + R_L) D - \hat{V}_0 \cdot d + \hat{V}_g \cdot \hat{d} - \hat{I}_L \cdot (R_L + R_{on}) \hat{d} - \\ & - V_0 \cdot \hat{d} - \hat{V}_0 \cdot D' + \hat{I}_L \cdot R_L \cdot D' + V_0 \cdot \hat{d} + V_D \cdot \hat{d} - \\ & - \hat{I}_L \cdot R_L \cdot \hat{d} \end{aligned}$$

Capacitor current perturbation and linearization

$$I_C + \hat{I}_C = I_L + \hat{I}_L - \frac{V_0 + \hat{V}_0}{R}$$

$$DC: I_C = I_L - \frac{V_0}{R} = 0 \Rightarrow I_L = \frac{V_0}{R}$$

$$AC: \left[\hat{I}_C = \hat{I}_L - \frac{\hat{V}_0}{R} \right]$$

(E4) Input current

$$\cancel{I_g} I_g + \hat{I}_g = (\bar{I}_L + \hat{I}_L)(D + \hat{d})$$

$$\cancel{DC: I_g} I_g + \hat{I}_g = \bar{I}_L \cdot D + \hat{I}_L \cdot D + \bar{I}_L \cdot \hat{d} + \hat{I}_L \cdot \hat{d}$$

$$DC: \{ I_g = \bar{I}_L \cdot D \}$$

$$AC: \{ \hat{I}_g = \hat{I}_L \cdot D + \bar{I}_L \cdot \hat{d} \}$$

$$b) \underline{C_1}: M_a = 0.5 \cdot M_2 \frac{m a}{m_2} \quad \left[R.27 \text{ from Erickson} \right]$$
$$d = - \frac{1 - \frac{m a}{m_2}}{\frac{D'}{D} + \frac{m a}{m_2}}$$

Stability margin: $d = 1$ for stability

~~should be~~ $\underline{d < 1}$ should be $\underline{d < 1}$

(ES)

d.) From capacitor current equation

$$\boxed{\hat{i}_C = \hat{i}_L - \frac{\hat{V}_0}{R}}$$

in Laplace domain:

$$\hat{i}_C(s) = \hat{i}_L(s) - \frac{\hat{V}_0(s)}{R} \quad ; \quad \hat{i}_C(s) = s \cdot C \cdot \hat{V}_0(s)$$

~~the same to:~~

$$s \cdot C \cdot \hat{V}_0(s) = \hat{i}_L(s) - \frac{\hat{V}_0(s)}{R}$$

$$s \cdot C \cdot \hat{V}_0(s) + \frac{\hat{V}_0(s)}{R} = \hat{i}_L(s) \Rightarrow \left(s \cdot C + \frac{1}{R} \right) \hat{V}_0(s) = \hat{i}_L(s)$$

simple approximation: $\hat{i}_L(s) \approx i_{ctrl}(s)$

$$\boxed{G_{vc}(s) = \frac{\hat{V}_0(s)}{\hat{i}_{ctrl}(s)} = \frac{1}{sC + \frac{1}{R}}}$$

control to output transfer function
doesn't depend on loss elements.