

# MEASUREMENTS AND SIGNAL CONDITIONING FOR POWER CONVERTERS

DESIGN OF SWITCH MODE CONVERTERS

DEZSO SERA (DES@ET.AAU.DK)



DEPARTMENT OF ENERGY TECHNOLOGY  
AALBORG UNIVERSITY

# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ GALVANIC ISOLATION
- ❑ PROTECTION
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)





# VOLTAGE MEASUREMENT

## RESISTIVE VOLTAGE DIVIDER

❑ VOLTAGE IS A POTENTIAL DIFFERENCE BETWEEN TWO POINTS

❑ VOLTAGE DIVIDER:

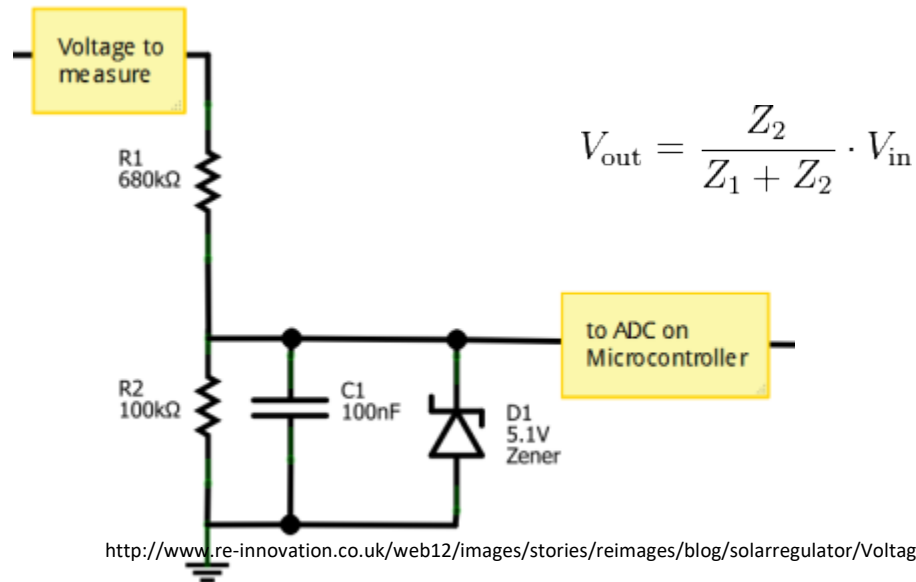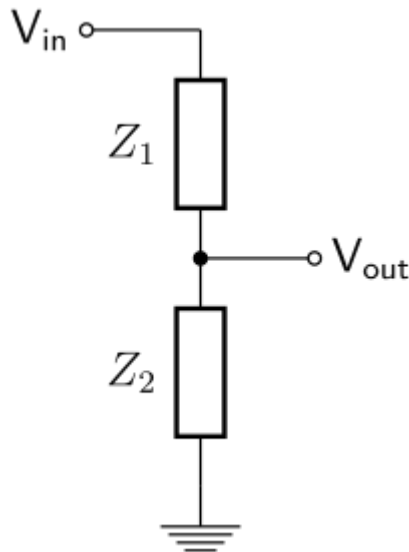

[http://www.re-innovation.co.uk/web12/images/stories/reimages/blog/solarregulator/Voltage\\_divider.png](http://www.re-innovation.co.uk/web12/images/stories/reimages/blog/solarregulator/Voltage_divider.png)

❑ ADVANTAGES:

- Simple
- Cheap
- Both DC and AC

❑ DISADVANTAGES:



- NO GALVANIC ISOLATION
- RESISTOR VALUES CAN CHANGE WITH TEMPERATURE



# VOLTAGE MEASUREMENT

## CAPACITIVE AND INDUCTIVE VOLTAGE DIVIDER

□ FOR AC ONLY

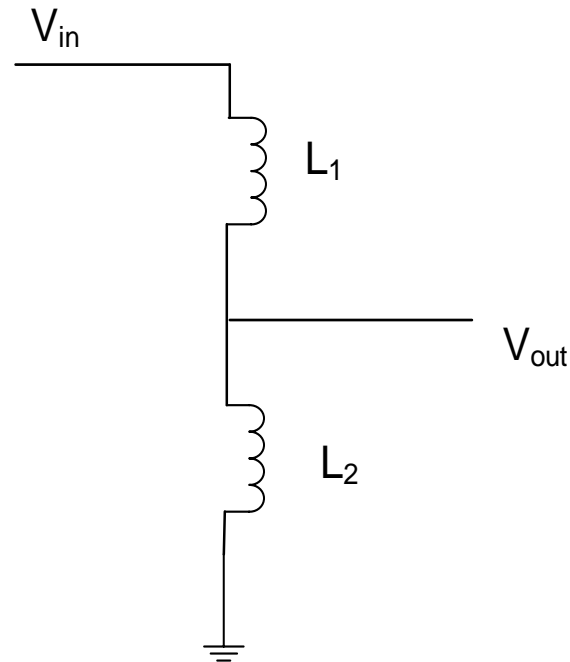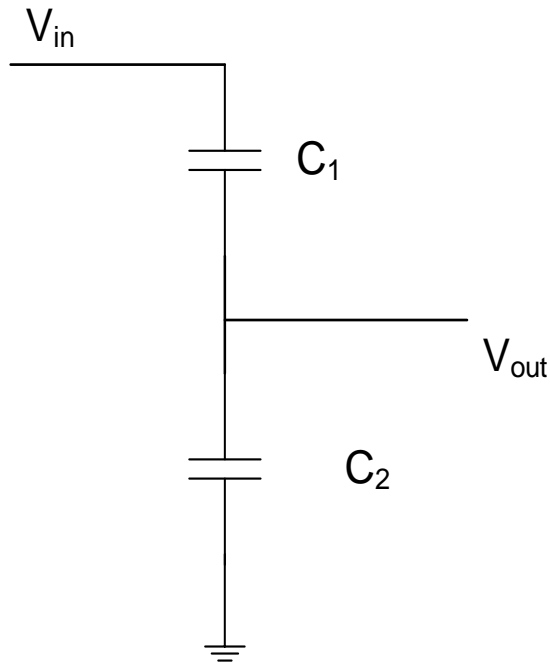

$$\square V_{out} = V_{in} \cdot \frac{C_1}{C_1 + C_2}$$


$$V_{out} = V_{in} \cdot \frac{L_2}{L_1 + L_2}$$



# VOLTAGE MEASUREMENT

## VOLTAGE DIVIDER - RC

### □ LOW-PASS RC FILTER

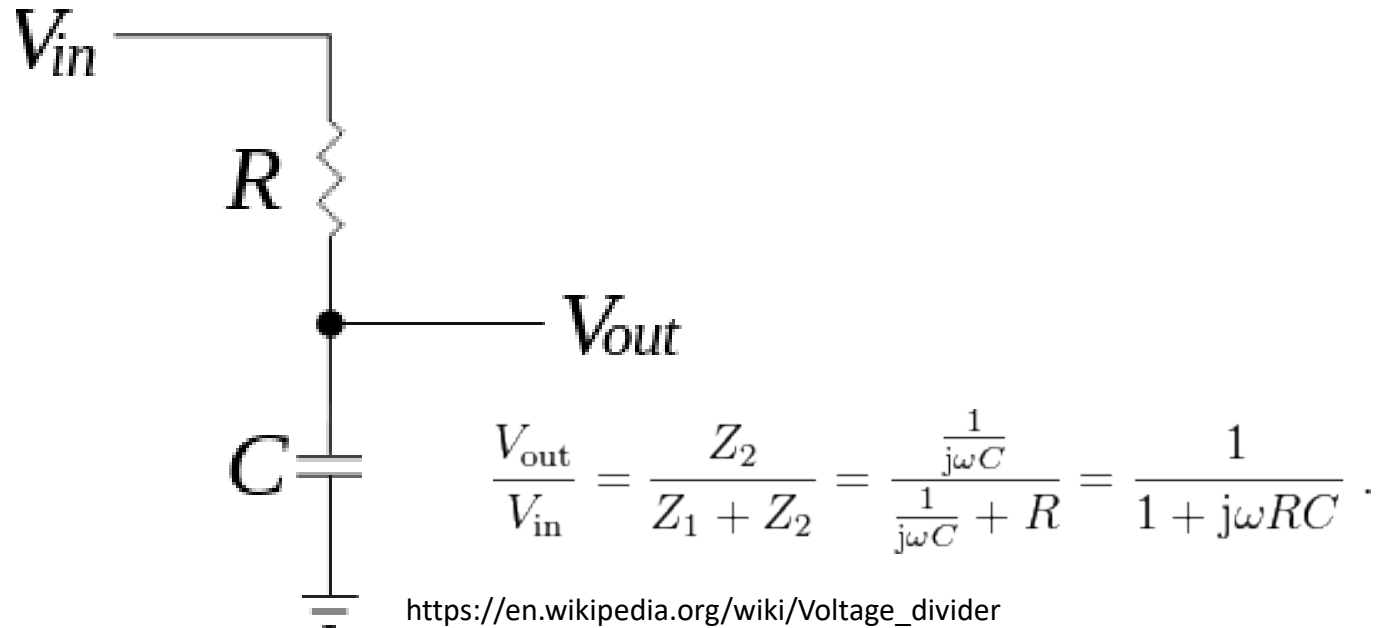


[https://en.wikipedia.org/wiki/Voltage\\_divider](https://en.wikipedia.org/wiki/Voltage_divider)



# VOLTAGE MEASUREMENT

## TRANSFORMER

❑ FOR AC ONLY

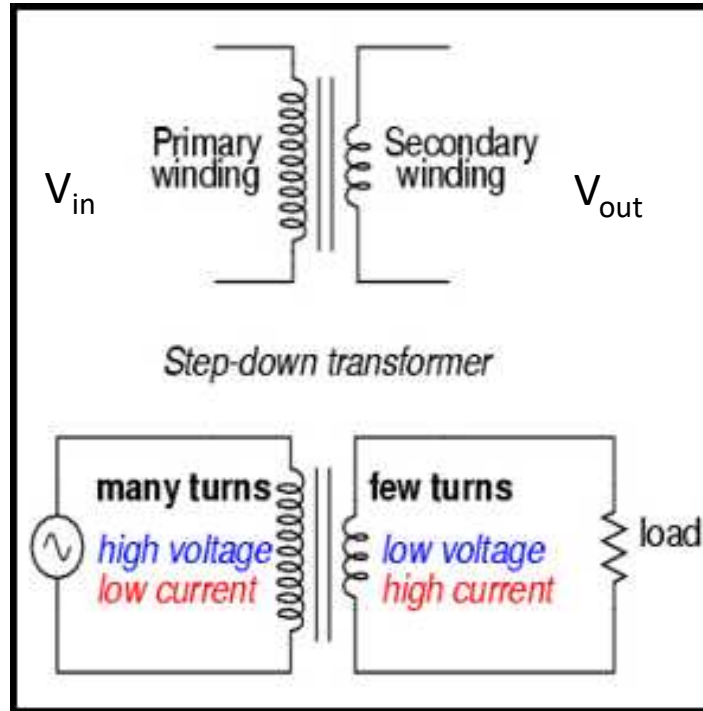

$$V_{out} = V_{in} \cdot \frac{N_2}{N_1}$$

### ❑ ADVANTAGES:

- SIMPLE
- GALVANIC ISOLATION


### ❑ DISADVANTAGES:

- TRANSFORMER NON-LINEARITIES
- LEAKAGE LOSSES
- MORE EXPENSIVE



# VOLTAGE MEASUREMENT

## HALL SENSOR

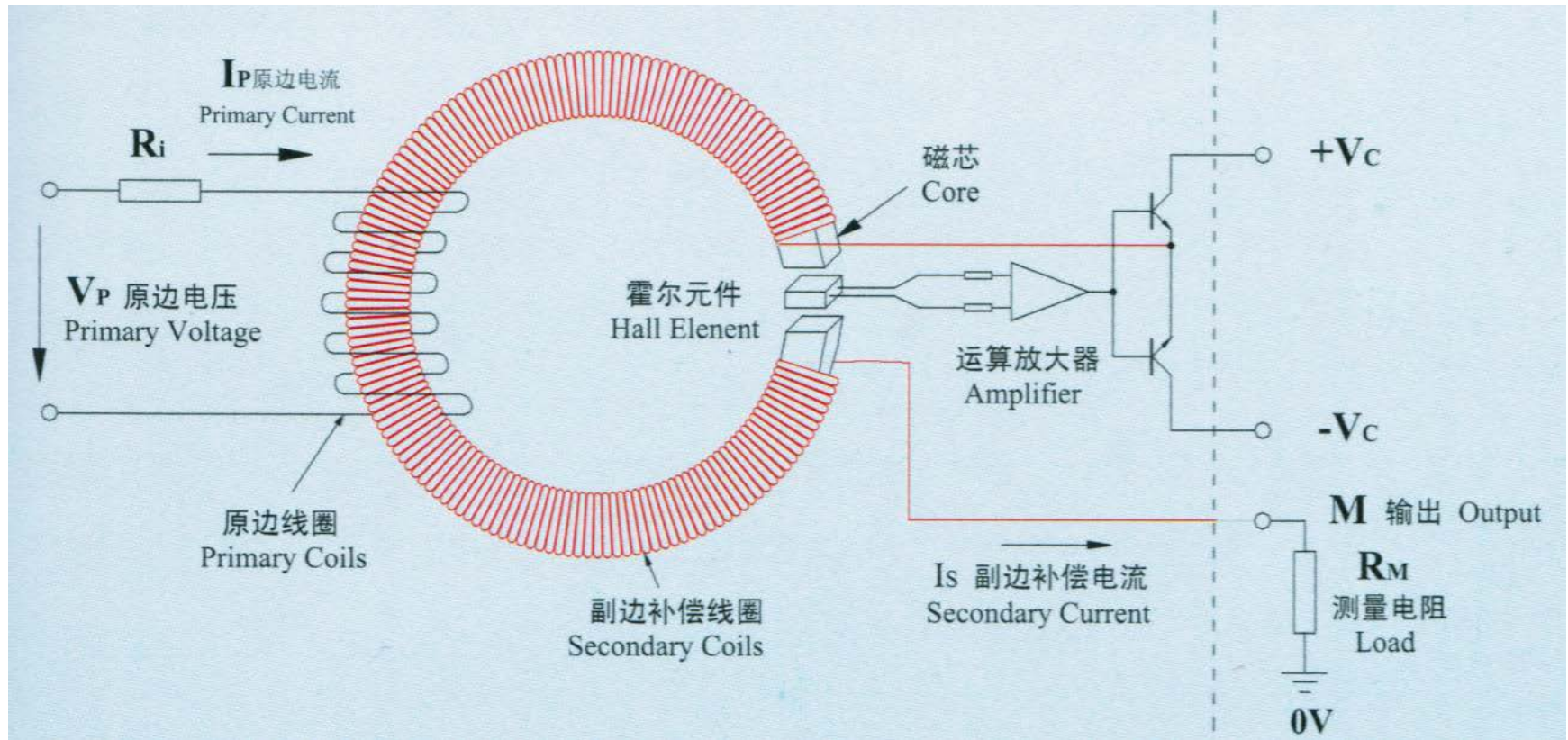

- ❑ SMALL CURRENT THROUGH PRIMARY BY MEASURED VOLTAGE
- ❑ BALANCING FLUX FROM SUPPLY CIRCUIT IN SECONDARY
- ❑ HALL DEVICE USED TO MEASURE FLUX - COMPENSATE



# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ **CURRENT MEASUREMENT METHODS**
- ❑ GALVANIC ISOLATION
- ❑ PROTECTION
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)





# CURRENT MEASUREMENT


## MAIN TYPES

- ❑ TWO MAIN TYPES: DIRECT AND INDIRECT SENSING
- ❑ DIRECT SENSING IS BASED ON OHM'S LAW – SHUNT RESISTOR
  - Low R shunt → voltage drop is normally measured by differential amplifiers
  - Invasive - the sensing circuit is part of the power circuit
  - No galvanic isolation
  - Usually for lower currents ( $<100\text{A}$ )
  - Cost effective
- ❑ INDIRECT SENSING IS BASED ON AMPER'S AND FARADAY'S LAW
  - Non-invasive – measures the field created by electric current
  - Galvanic isolated
  - Typically higher currents
  - Typically more expensive sensors



# CURRENT MEASUREMENT

## SHUNT RESISTOR

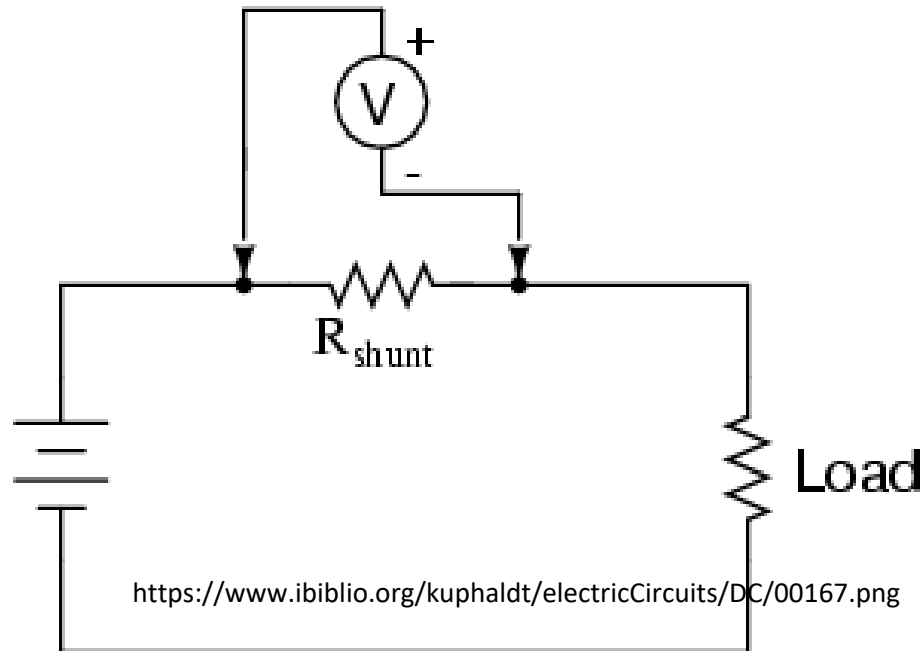

### □ ADVANTAGES:

- Simple
- Linear –  $V_{out} = I \cdot R$
- Low-cost

### □ DISADVANTAGES:


- NO GALVANIC ISOLATION
- LOSSES ON R



# CURRENT MEASUREMENT

## CURRENT TRANSFORMER

❑ AC ONLY

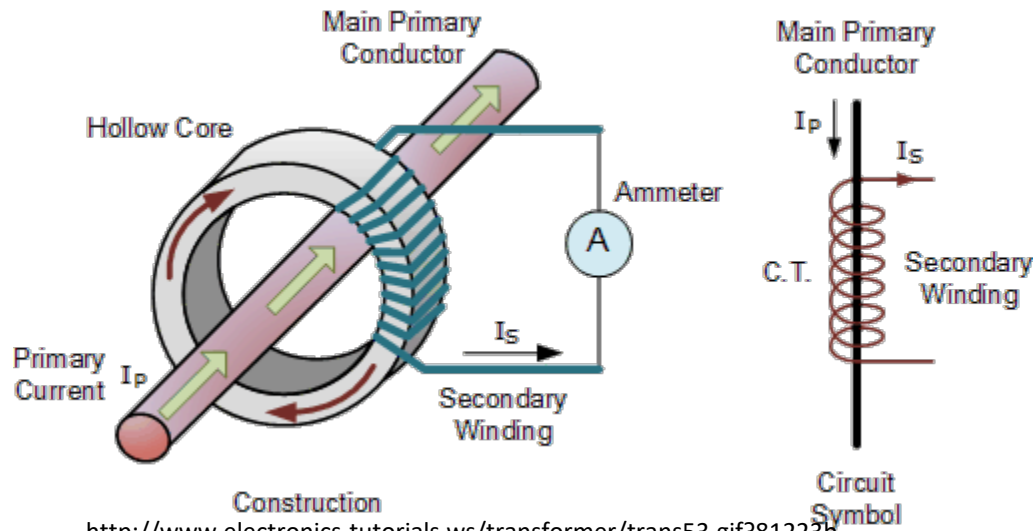

<http://www.electronics-tutorials.ws/transformer/trans53.gif?81223b>

❑ CAN MEASURE VERY HIGH CURRENTS

❑ GALVANIC ISOLATION


❑ SECONDARY SIDE CURRENT CAN BE TRANSFORMED TO V BY E.G. SHUNT



# CURRENT MEASUREMENT
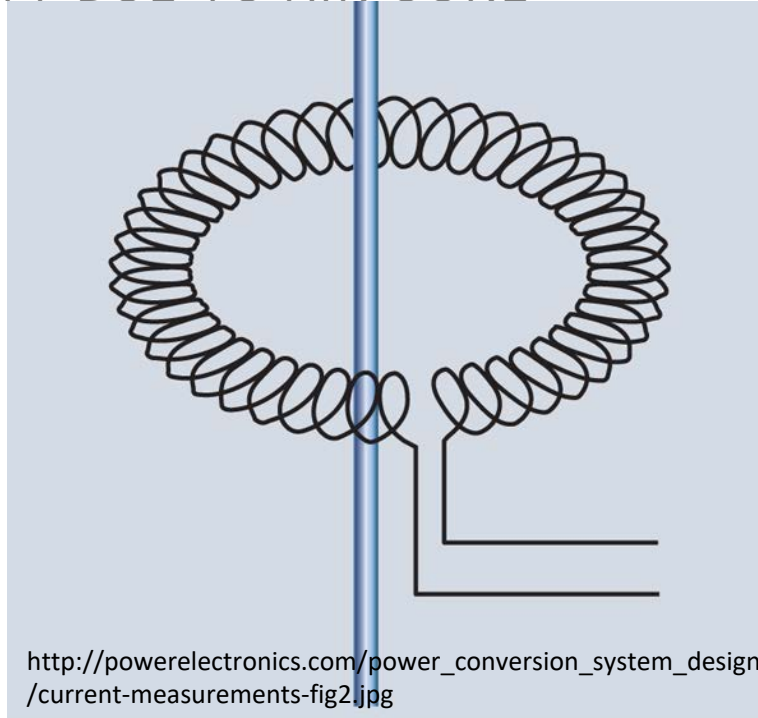
## CURRENT TRANSFORMER – ROGOWSKI COIL

- ❑ SPECIAL DESIGNED WITH AIR CORE – LOWER INDUCTANCE AND FASTER RESPONSE
- ❑ VERY GOOD LINEARITY DUE TO AIR CORE




- ❑ TYPICALLY USED FOR MEASURING IN HIGH BANDWIDTH APPLICATIONS  $>1\text{MHz}$ , OR FAST TRANSIENT CURRENTS




# CURRENT MEASUREMENT

## HALL-EFFECT SENSOR - PRINCIPLE

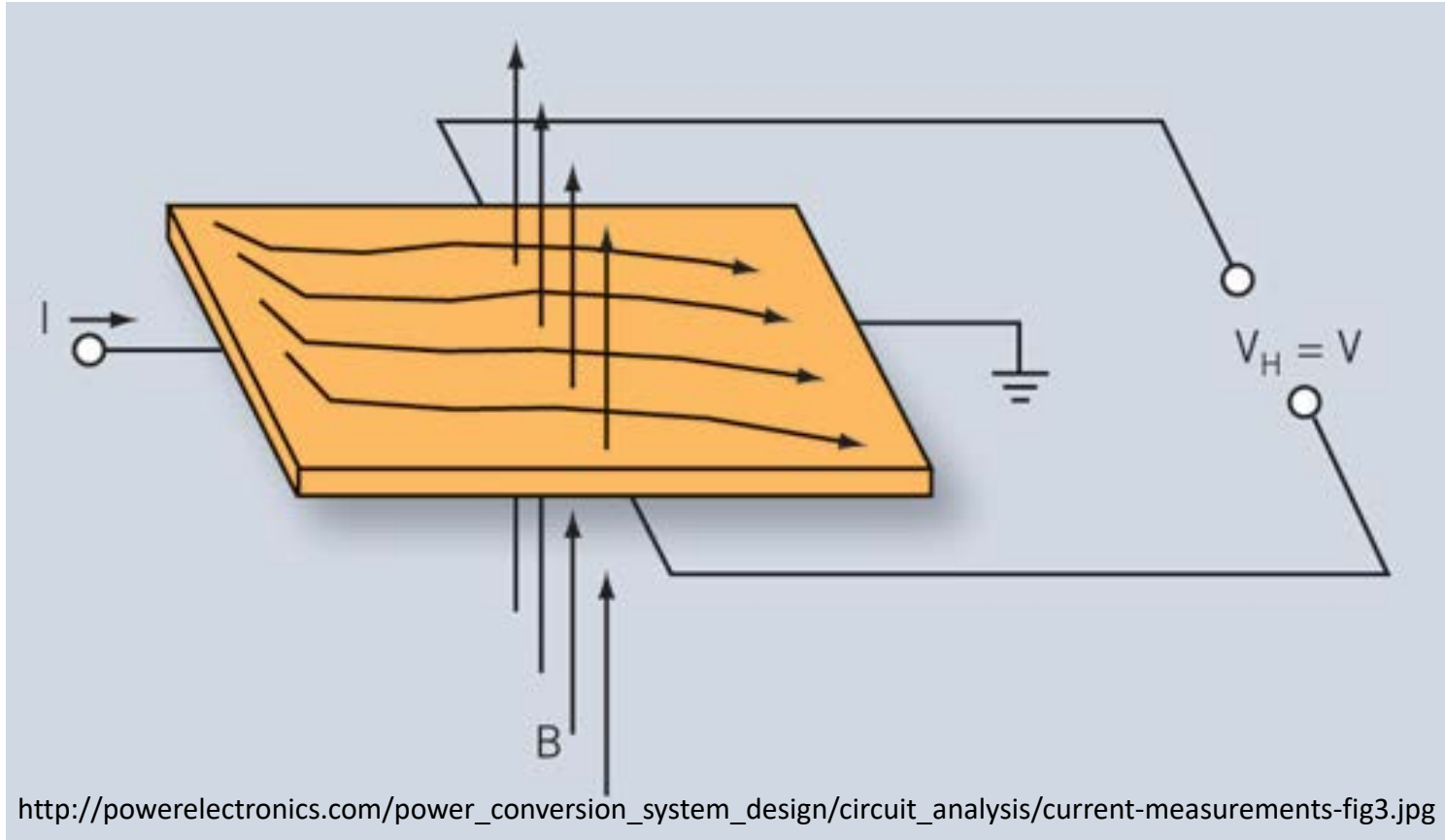

# CURRENT MEASUREMENT


## OPEN-LOOP HALL-EFFECT SENSOR

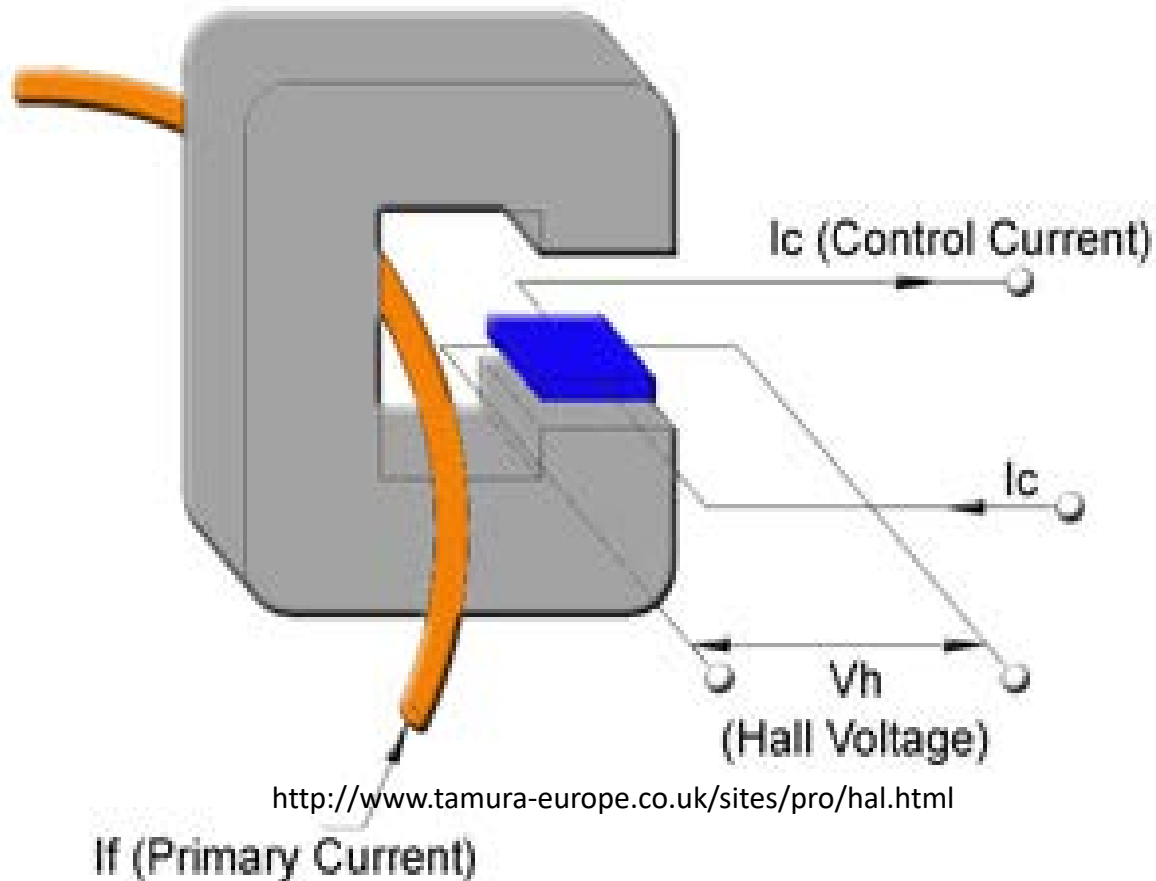

# CURRENT MEASUREMENT

## CLOSED-LOOP HALL-EFFECT SENSOR

❑ ALSO CALLED COMPENSATED, OR ZERO-FLUX

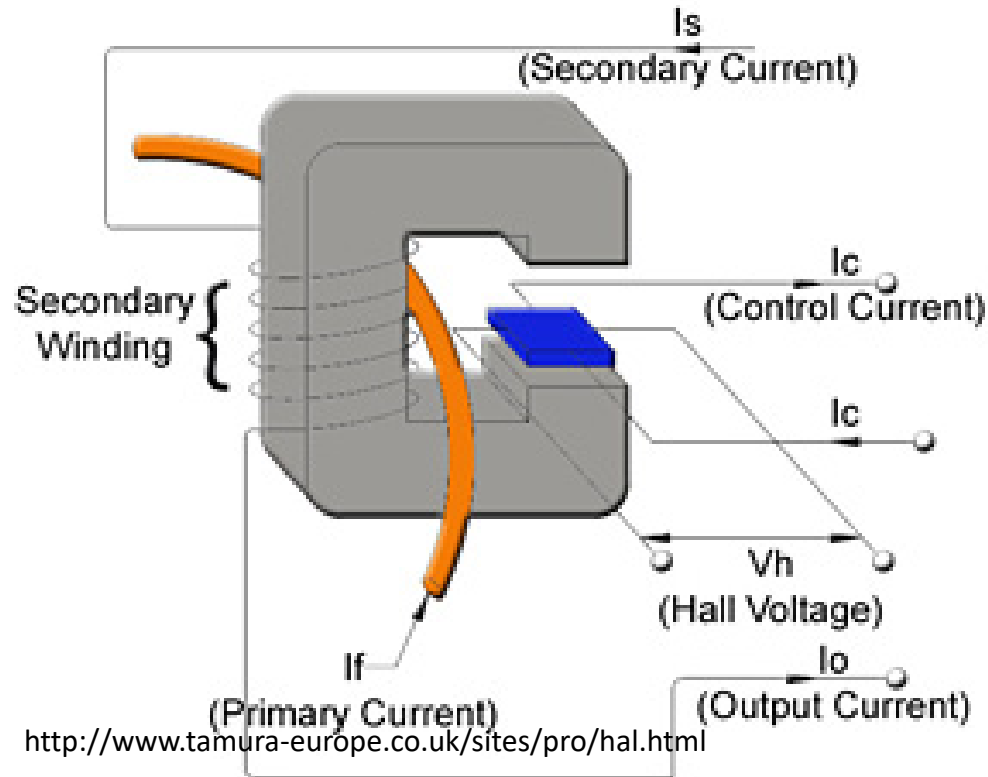

❑ COMPARED TO OPEN-LOOP VERSION:

❑ MORE EXPENSIVE


- Higher accuracy, no nonlinearity of Hall sensor
- Higher noise immunity
- No saturation, No temperature drift



# CURRENT MEASUREMENT

## CLOSED-LOOP HALL-EFFECT SENSOR

### □ IMPLEMENTATION EXAMPLE

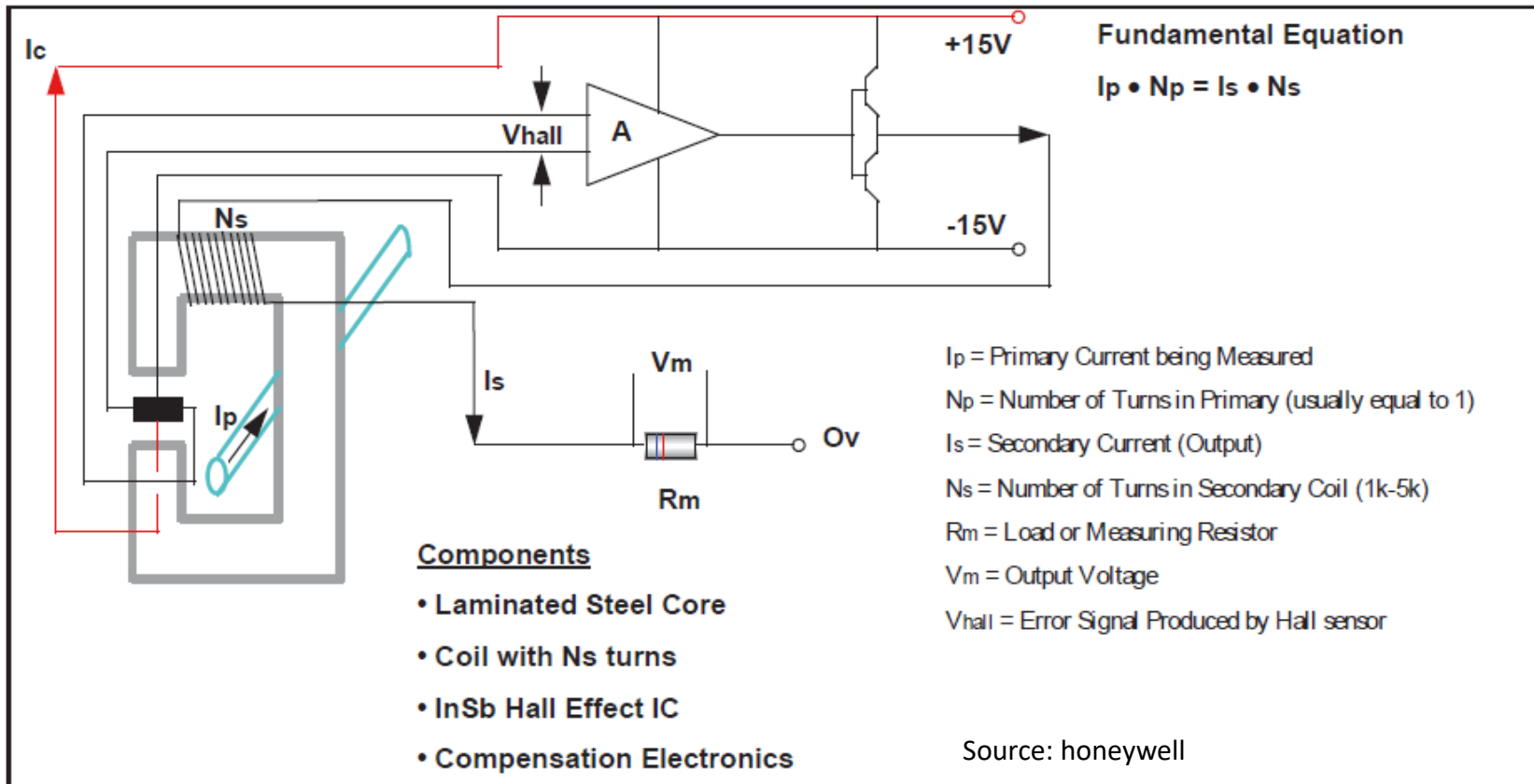





# CURRENT MEASUREMENT

## CLOSED-LOOP HALL-EFFECT SENSOR

### □ CURRENT MEASUREMENT

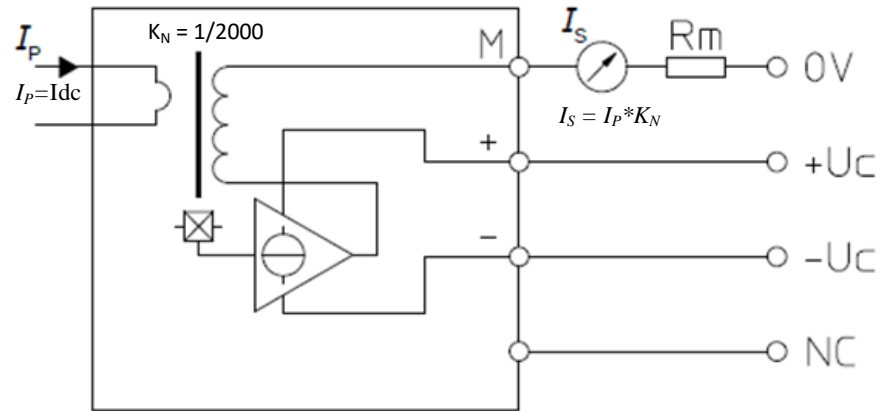

### □ VOLTAGE MEASUREMENT

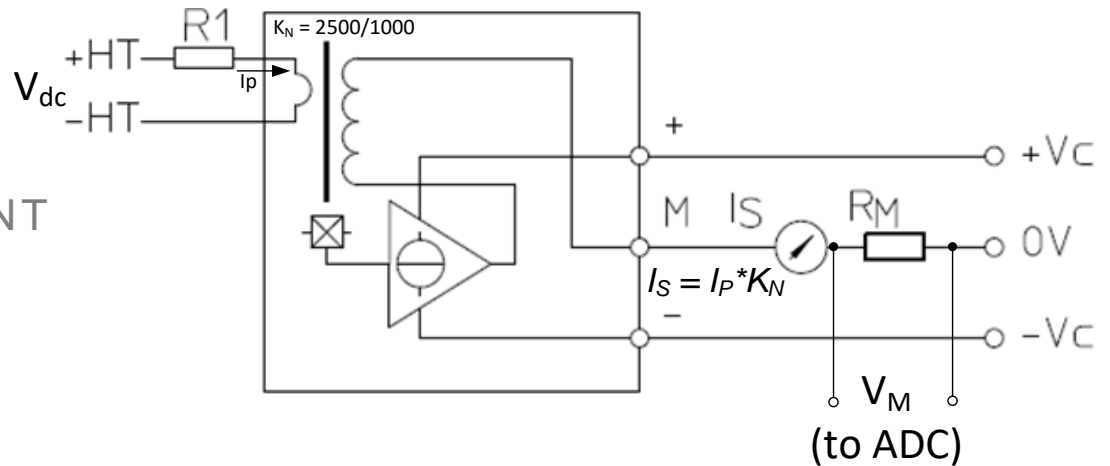

Source: LEM



# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ **GALVANIC ISOLATION**
- ❑ PROTECTION
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)



# **GALVANIC ISOLATION**

**BLOCKS DC CURRENT FLOW BETWEEN THE ISOLATED CIRCUITS**

## **❑ PURPOSE:**

To be able to pass signals between circuits with different ground potentials  
Safety - close ground loop through a person

## **❑ MAIN METHODS/PRINCIPLES:**

Transformer  
Opto-isolator  
Capacitor  
Hall effect

## **❑ CHARACTERISTICS**


Isolation impedance / leakage  
Blocking/isolation voltage  
Bandwidth



# GALVANIC ISOLATION

## OPTICAL ISOLATION - OPTO-COUPLER

### ❑ PRINCIPLE

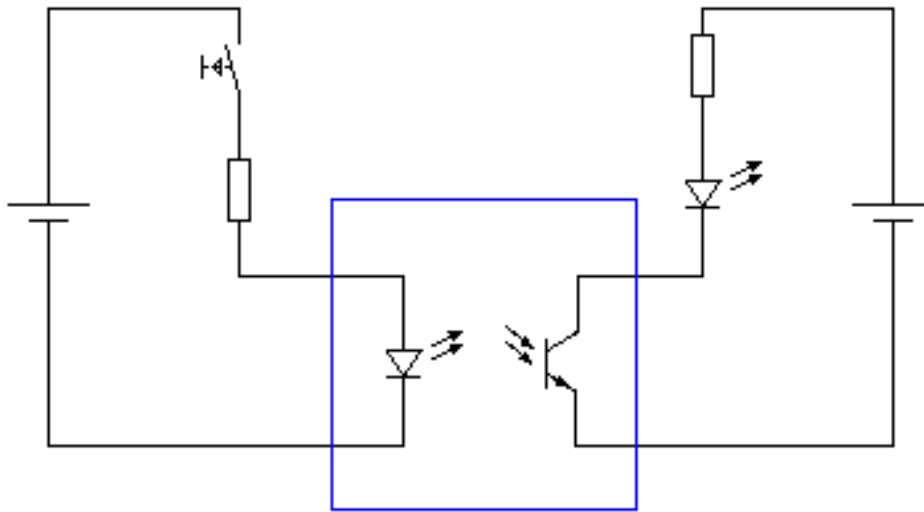

"Optokoppler" by Quark48 at the German language Wikipedia. Licensed under CC BY-SA 3.0 via Commons - <https://commons.wikimedia.org/wiki/File:Optokoppler.gif#/media/File:Optokoppler.gif>

❑ LED IS NON-LINEAR LIGHT SOURCE

❑ IN BASIC FORM IS ON/OFF (DIGITAL)


❑ OPTO-COUPPLERS HAVE GENERALLY GOOD NOISE IMMUNITY



# GALVANIC ISOLATION
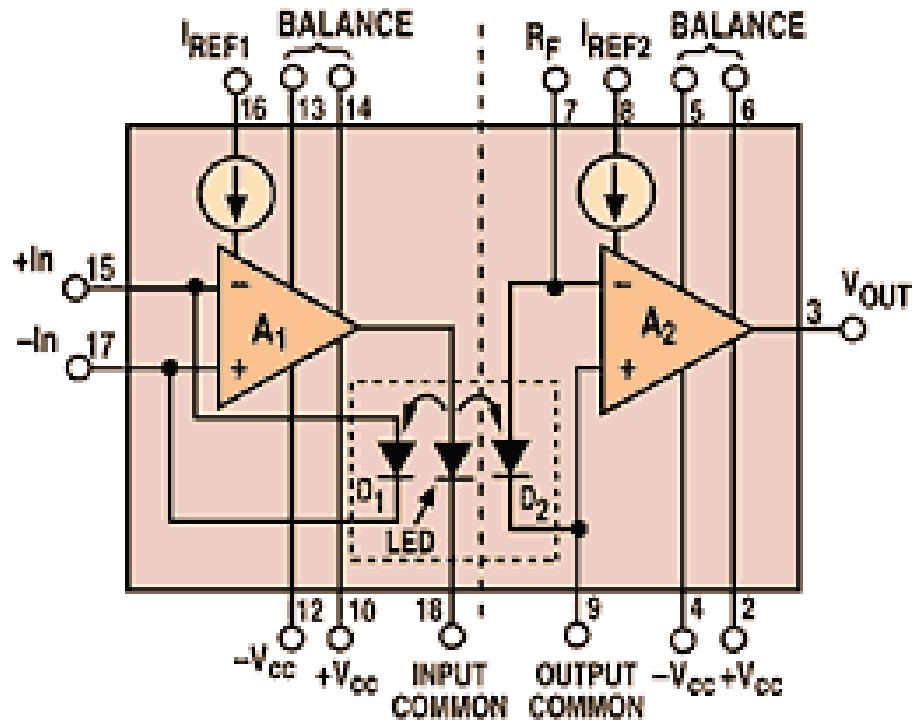
## OPTICAL ISOLATION

❑ IMPLEMENTATIONS – SIGNAL PASSED IN ANALOGUE FORM



[http://archives.sensormag.com/articles/0199/iso0199/iso0199\\_fig4.gif](http://archives.sensormag.com/articles/0199/iso0199/iso0199_fig4.gif)


❑ MATCHED PHOTODIODES



# GALVANIC ISOLATION
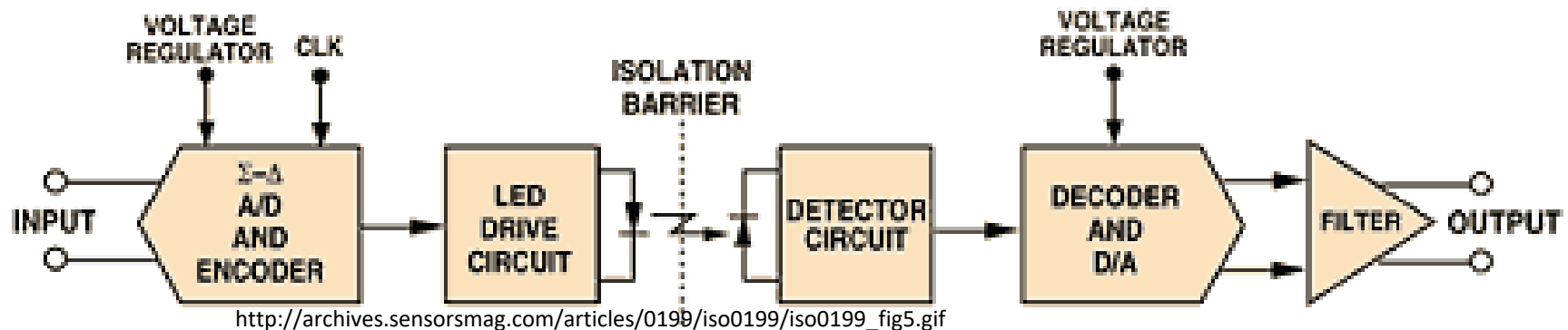
## OPTICAL ISOLATION

❑ IMPLEMENTATIONS – SIGNAL PASSED IN DIGITAL FORM



❑ AVOIDS THE SECOND PHOTO-DIODE BUT ADDS TO THE COMPLEXITY




# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ GALVANIC ISOLATION
- ❑ **PROTECTION**
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)


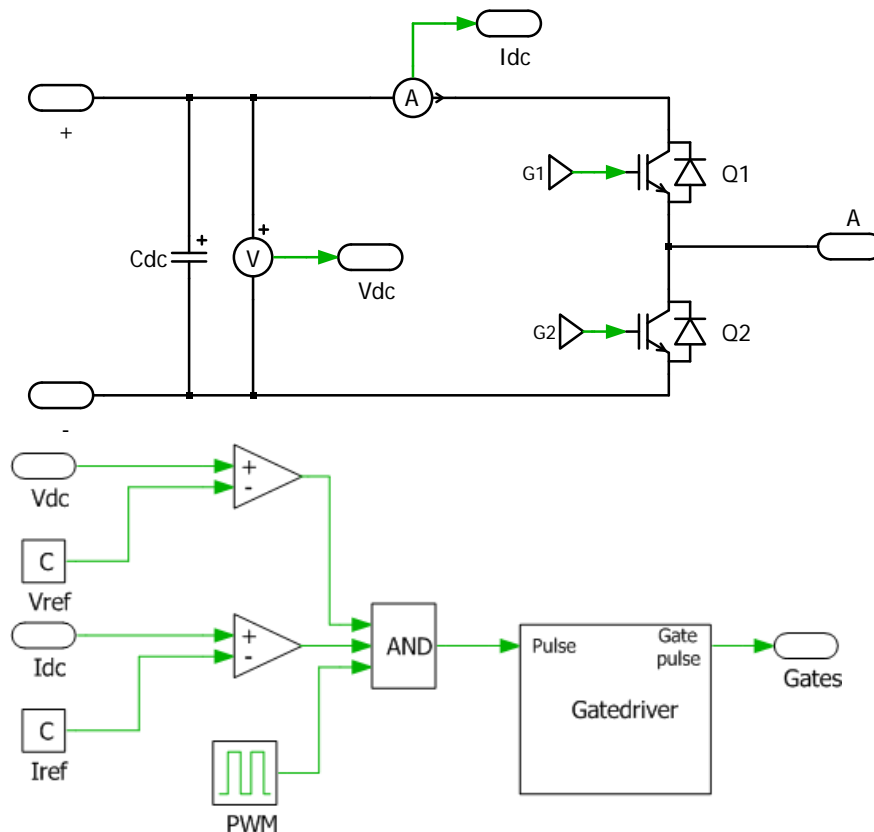
# PROTECTION

- Over voltage protection
- Over current protection
- What if it happens only once?




- What if it happens periodically?





# LATCH AND BUFFER

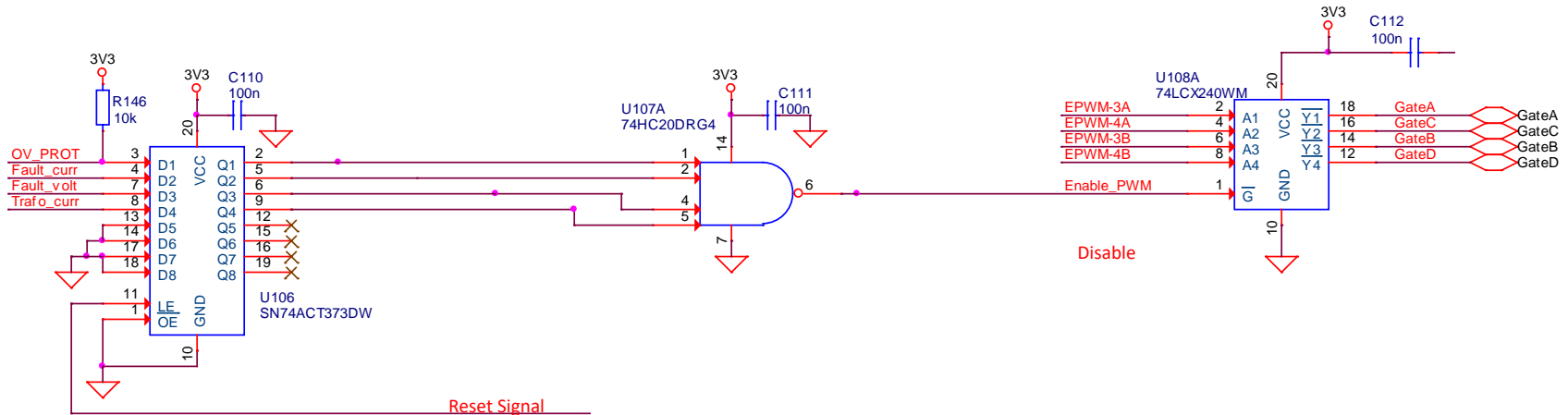

- U106: **Latch** - x fault event makes  $Q_x=1$
- U107: NAND gate output = 1 (default 0)
- U108: **Buffer** – `Disable` = 1 -> gate pulses stopped
- Reset signal needed



# OUTLINE


- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ GALVANIC ISOLATION
- ❑ PROTECTION
- ❑ **ANALOGUE-TO-DIGITAL CONVERSION**
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)



# WHAT IS AN ADC
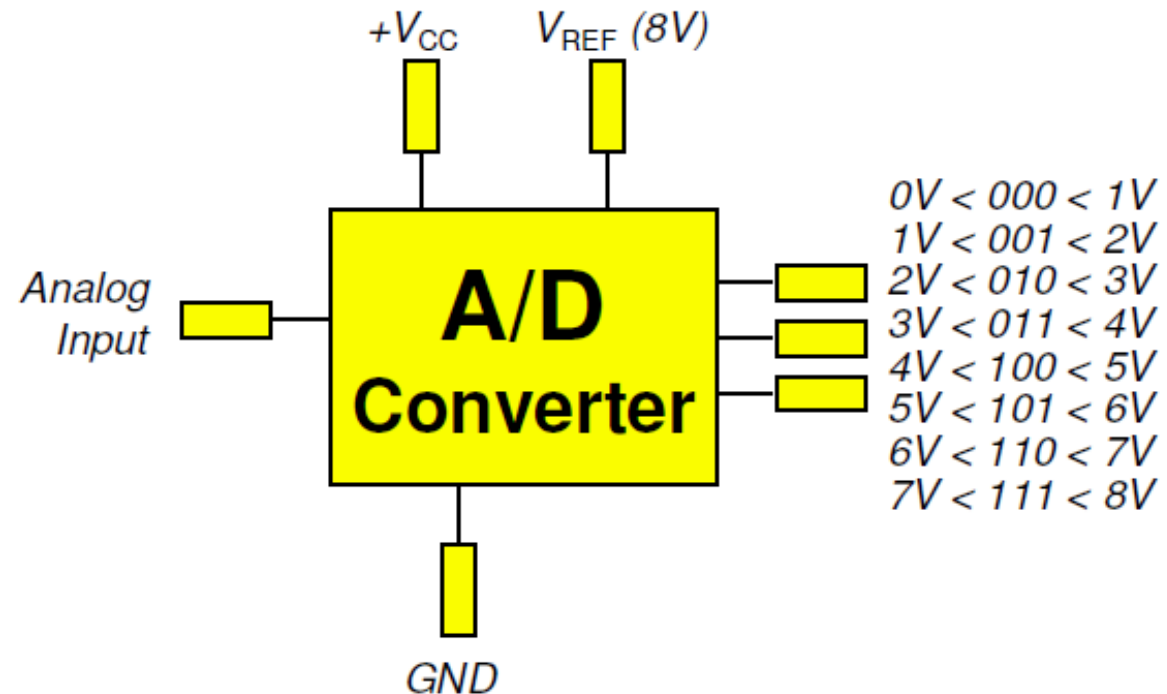
## ANALOGUE-TO-DIGITAL CONVERTER

- ❑ CONVERTS AN ANALOGUE, CONTINUOUS SIGNAL AT ITS INPUT INTO A DIGITAL DISCRETE NUMBER AT ITS OUTPUT
- ❑ FOR A 3-BIT ADC, THERE ARE 8 POSSIBLE OUTPUT CODES.




- ❑ IN THIS EXAMPLE, IF THE INPUT VOLTAGE IS 5.5V AND THE REFERENCE IS 8V, THEN THE OUTPUT WILL BE 101 (6V).




# TRANSFER FUNCTION OF ADC AT DIFFERENT RESOLUTION

3-bit ADC

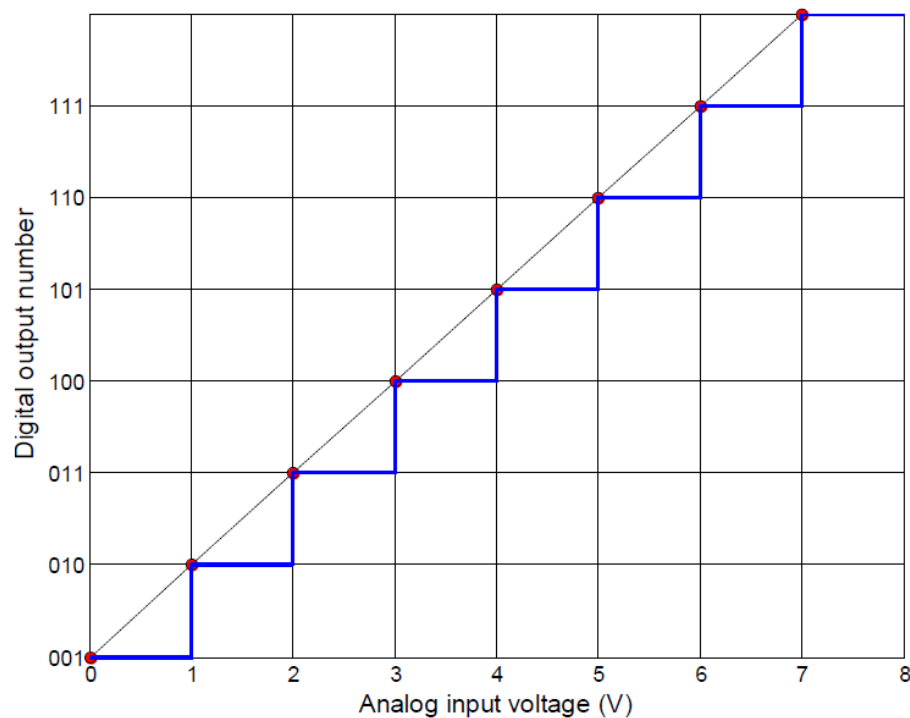

6-bit ADC

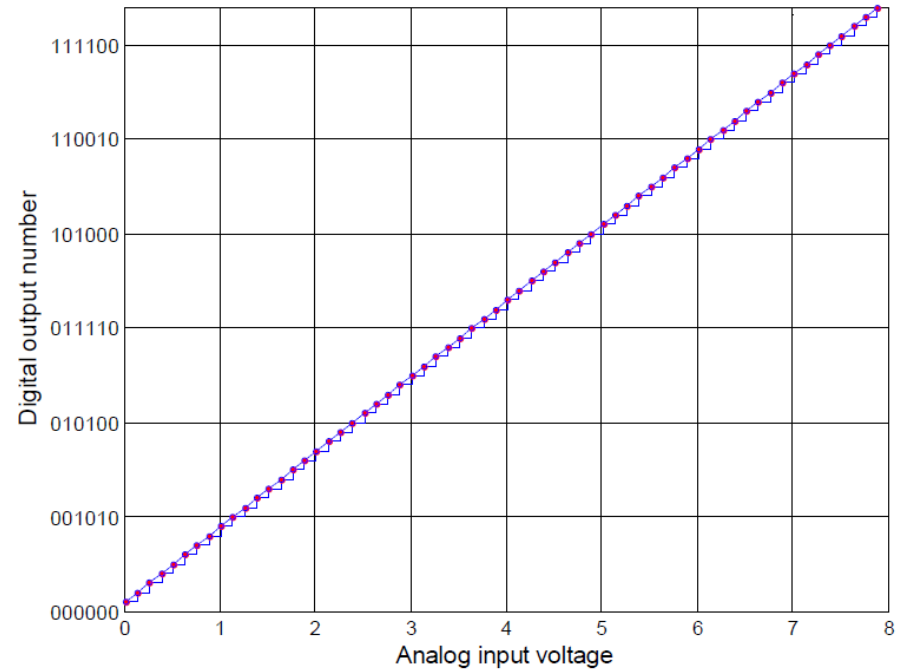


# ADC RESOLUTION

- ❑ RESOLUTION: THE NUMBER OF DISCRETE VALUES IT CAN PRODUCE OVER THE RANGE OF ANALOGUE VALUES
- IT CAN BE GIVEN IN BITS: FOR EXAMPLE, A 12-BIT RESOLUTION ADC CAN PRODUCE  $2^{12} = 4096$  DISCRETE DIGITAL VALUES OF ITS FULL-SCALE ANALOGUE INPUT VOLTAGE
- IT CAN BE GIVEN IN VOLTS: FOR EXAMPLE, WITH A FULL-SCALE INPUT OF 0-3V, WILL HAVE A RESOLUTION OF  $3 / 4096 = 0.00073V$




# TYPICAL A/D CONVERSION SCHEME


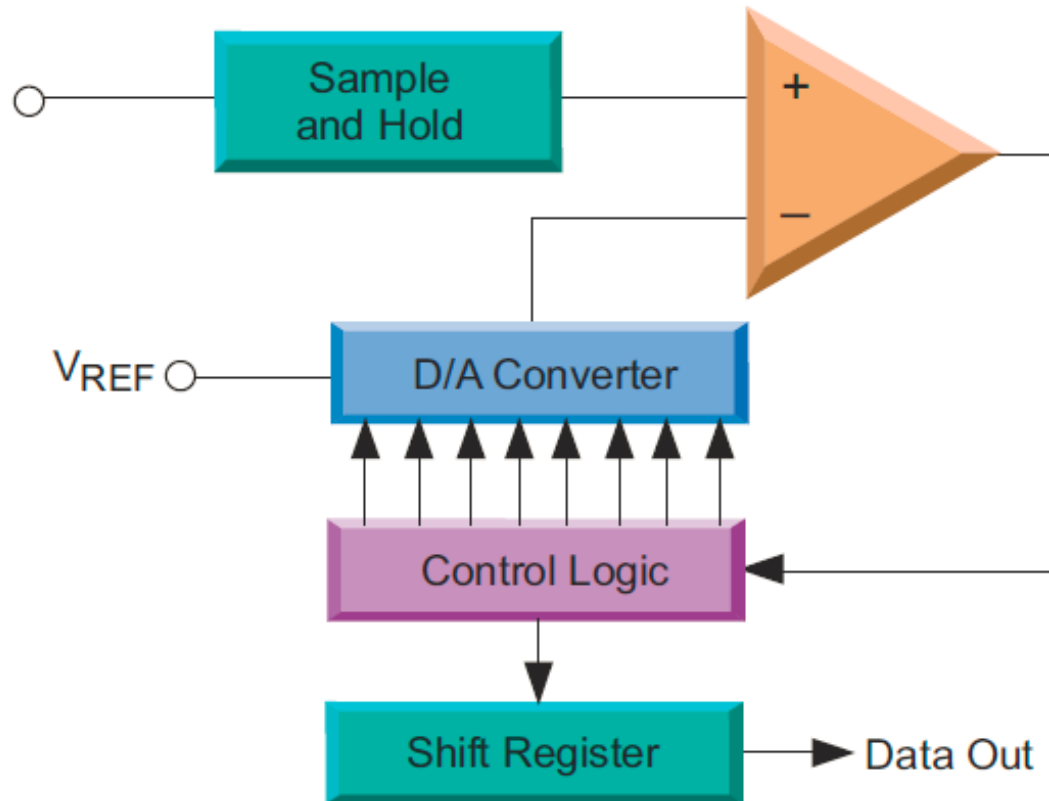

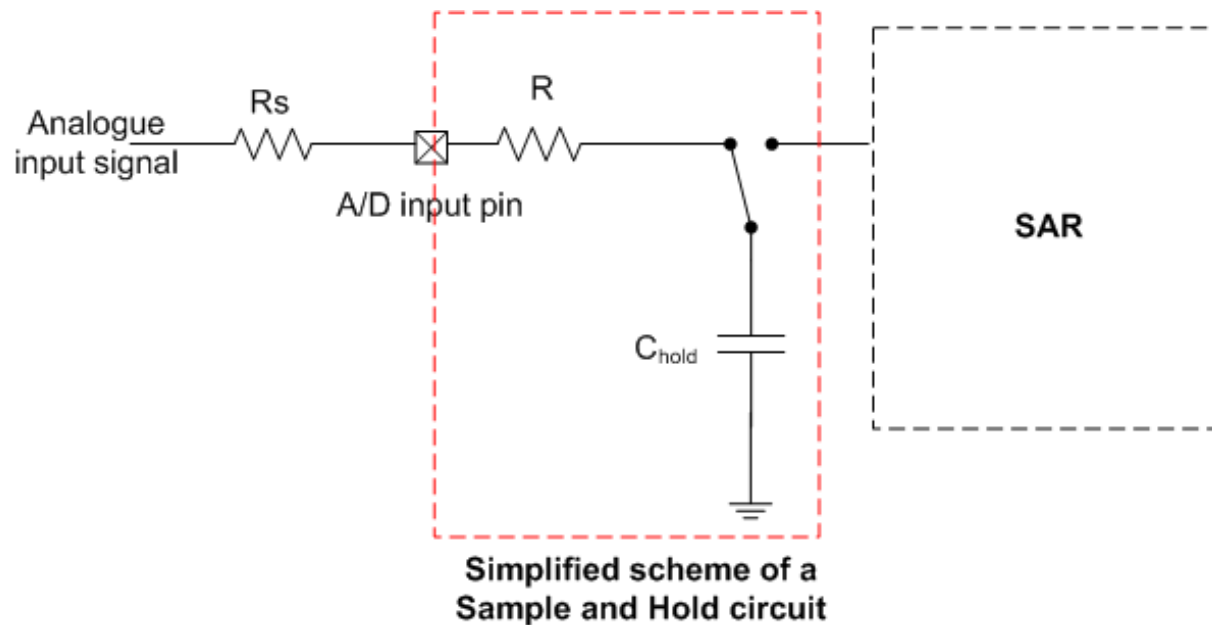
# SAMPLE AND HOLD CIRCUIT

- ❑ THE PURPOSE THE S/H CIRCUIT IS TO KEEP THE VOLTAGE LEVEL CONSTANT DURING THE CONVERSION (MAINLY A CAPACITOR)
- ❑ THE SETTLING TIME (TIME NEEDED TO CHARGE UP THE S/H CAPACITOR) LIMITS THE MAXIMUM INPUT FREQUENCY



# SUCCESSIVE APPROXIMATION

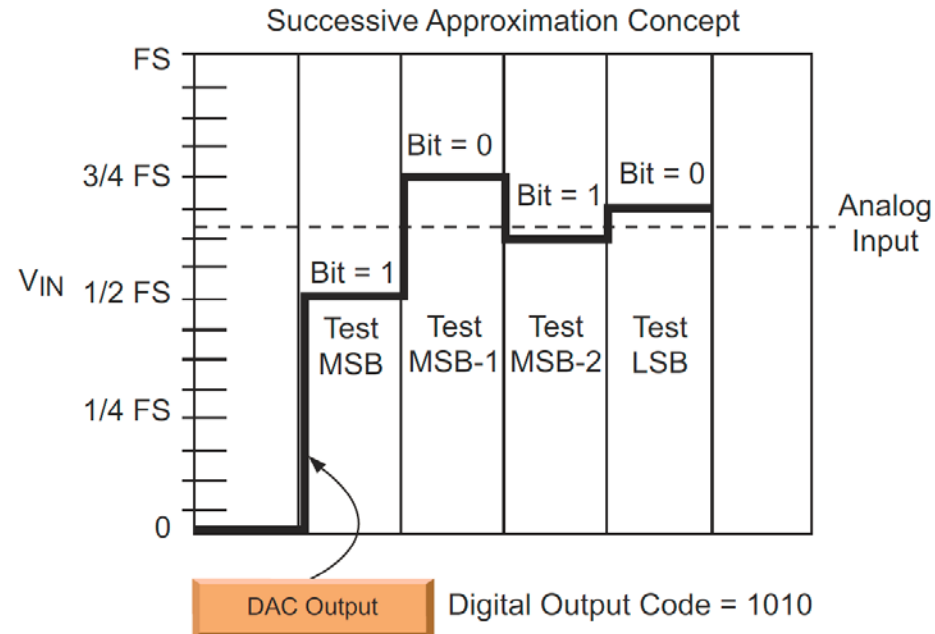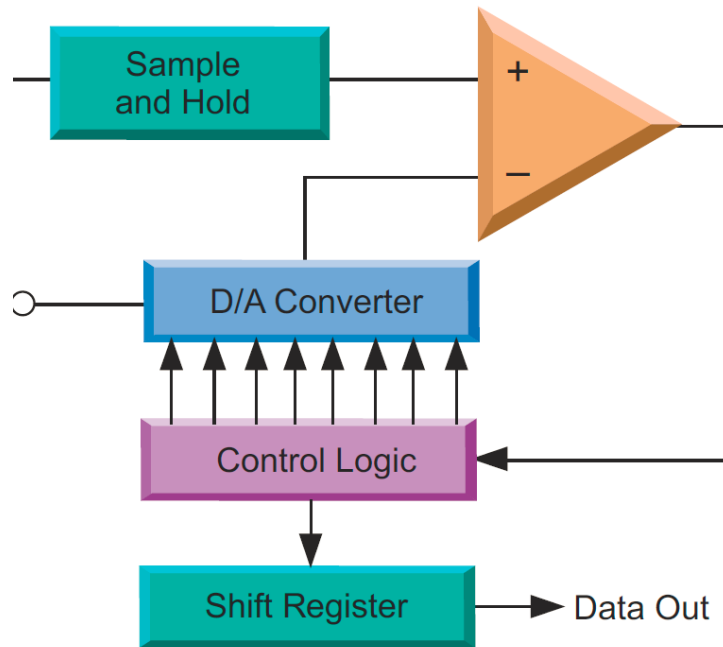

- 1 - MSB of DAC input is set to '1' (half of DAC output range)
- 2 - Test if DAC output is higher than analog input. If higher, MSB = 0, else MSB = 1
- 3 - Repeat 1 and 2 with MSB-1








# SUMMARY OF THE CHARACTERISTICS OF THE ADC

❑ THE FULL CONVERSION TIME IS A TWO STEP PROCESS:

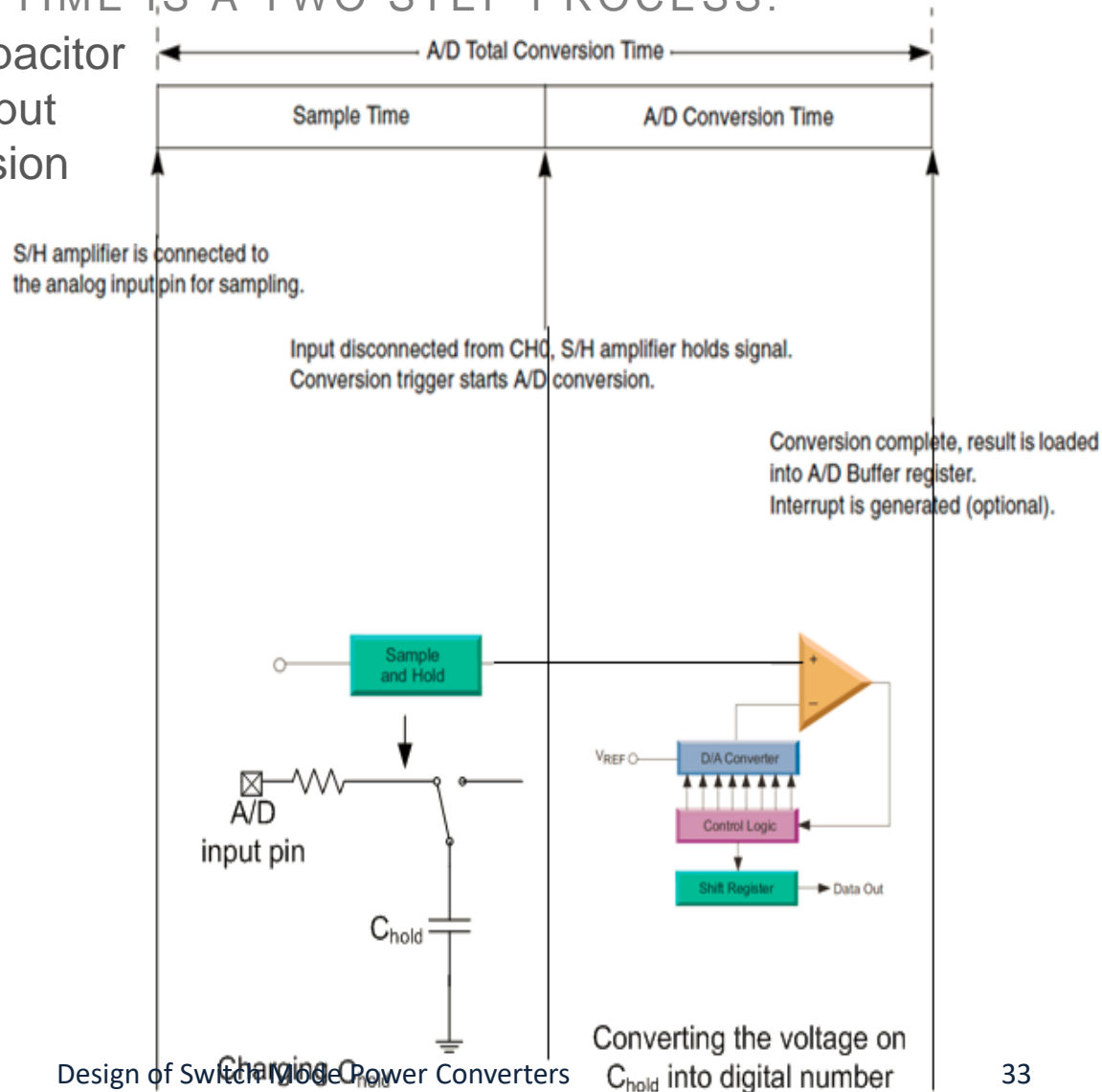1. Charging the sampling capacitor
2. Disconnect C<sub>hold</sub> from input pin and start the A/D conversion



# PERIODIC SAMPLING

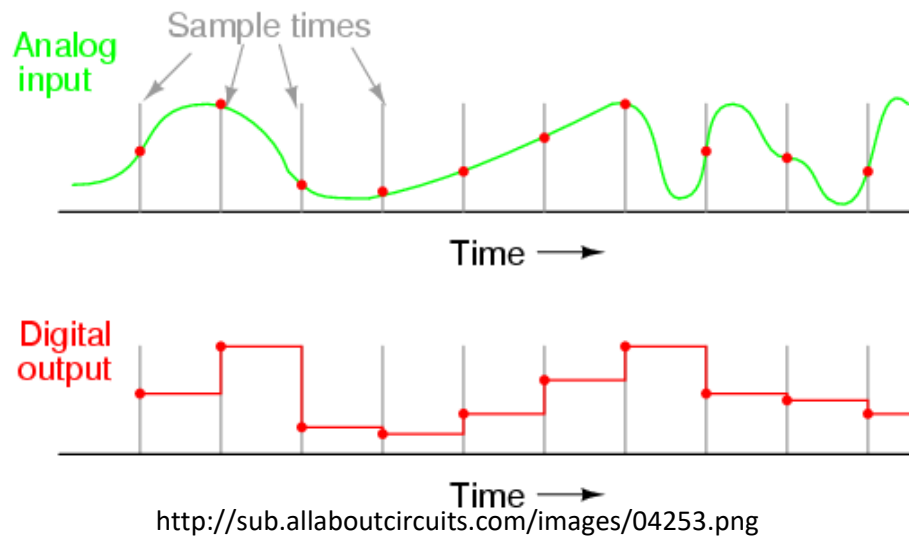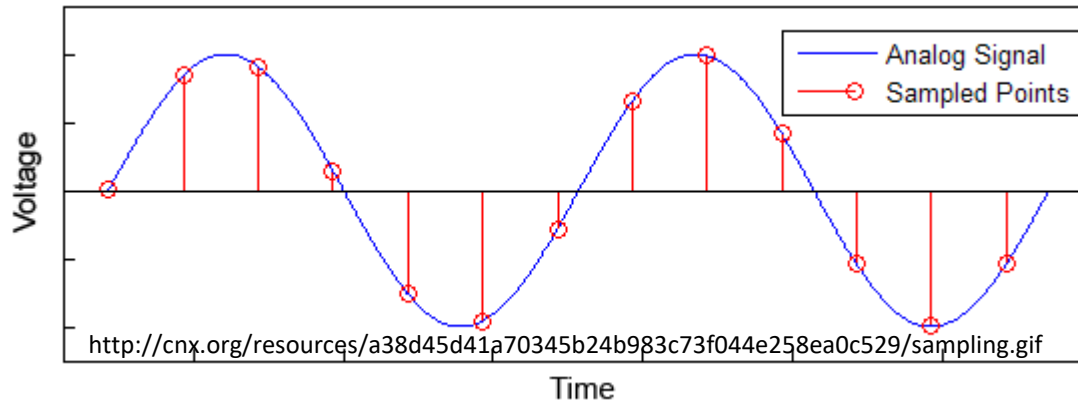

# PERIODIC SAMPLING

## NYQUIST'S RULE



- ❑ SAMPLING OF CONTINUOUS SIGNAL WAVEFORM
- ❑ MEASURED SIGNALS WITH COMPLEX WAVEFORMS CAN BE REPRESENTED BY SUM OF SINUSOIDAL (FOURIER)

IN ORDER TO CORRECTLY REPRESENT THE MEASURED SIGNAL:

$$F_{\text{sampling}} \geq 2 * F_{\text{max}}$$

$F_{\text{max}}$  – THE HIGHEST FREQUENCY COMPONENT IN THE MEASURED SIGNAL

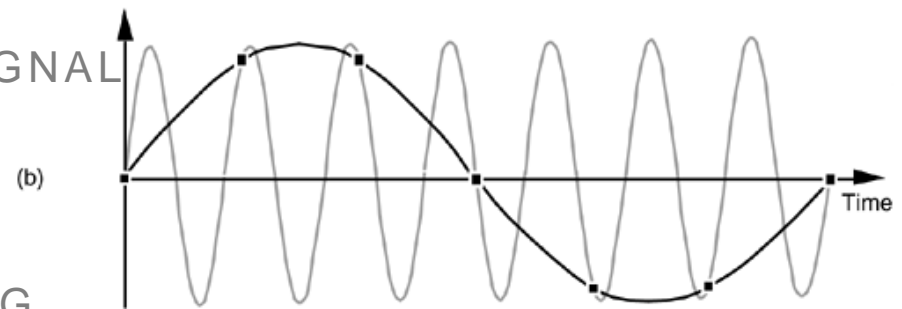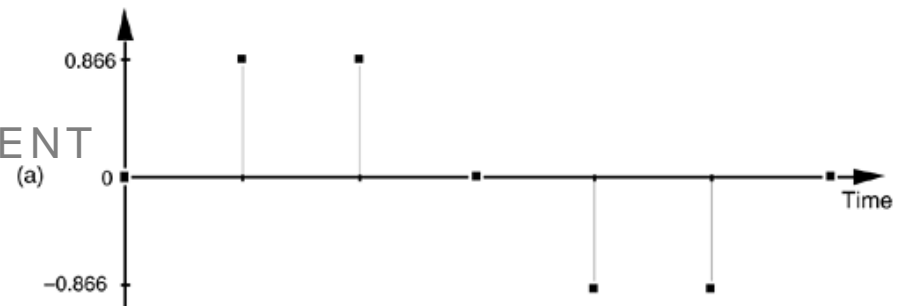IF THERE ARE (UNDESIRABLE) FREQUENCY COMPONENTS WITH  $F > F_{\text{sampling}}$  → ANALOGUE FILTERING PRIOR TO ADC



Understanding Digital Signal Processing, 2nd Edition, Richard G. Lyons  
Published Mar 15, 2004 by Prentice Hall.



# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ GALVANIC ISOLATION
- ❑ PROTECTION
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ **FILTERING (DIGITAL AND/OR ANALOGUE)**




# FILTERING


## ❑ WHY DO WE USE FILTERING?

Reduce the amplitude of the unwanted frequency components (usually called noise) from the input (measured) signal spectrum

Unfiltered signal

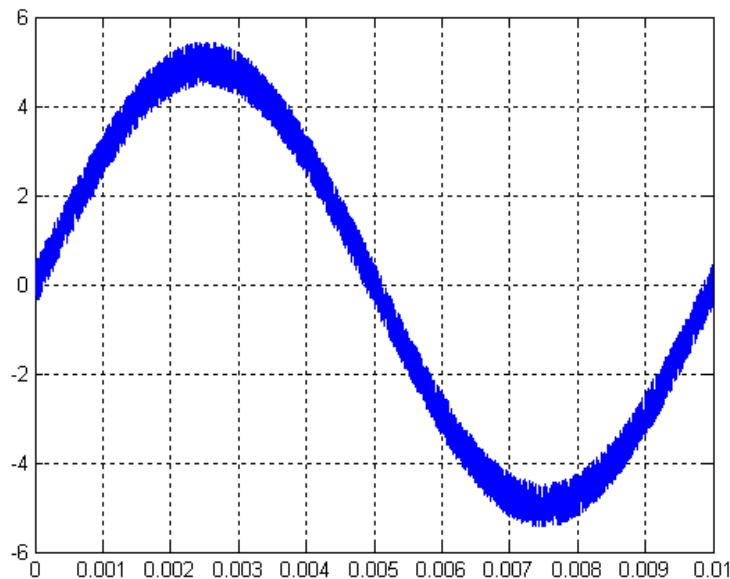

Filtered signal

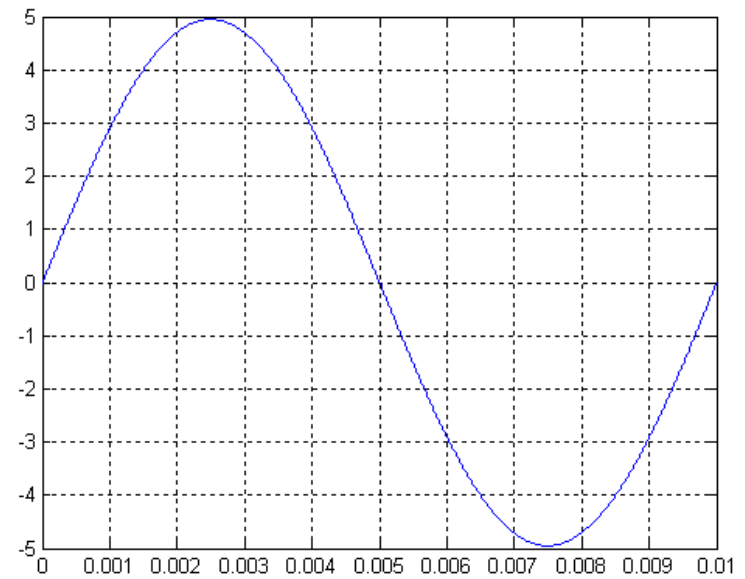


# TYPE OF FILTERS

## LOW PASS




- PASSES FREQUENCIES BELOW A CERTAIN FREQUENCY (CUT OFF FREQUENCY) AND REJECTS (ATTENUATES) FREQUENCIES ABOVE THE CUT OFF FREQUENCY

- EXAMPLES:

- FIRST ORDER

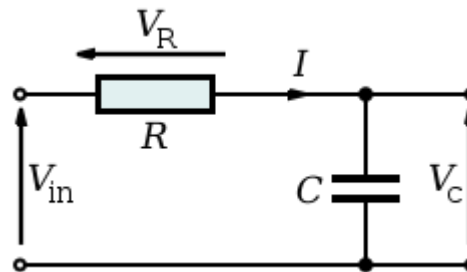


- SECOND ORDER

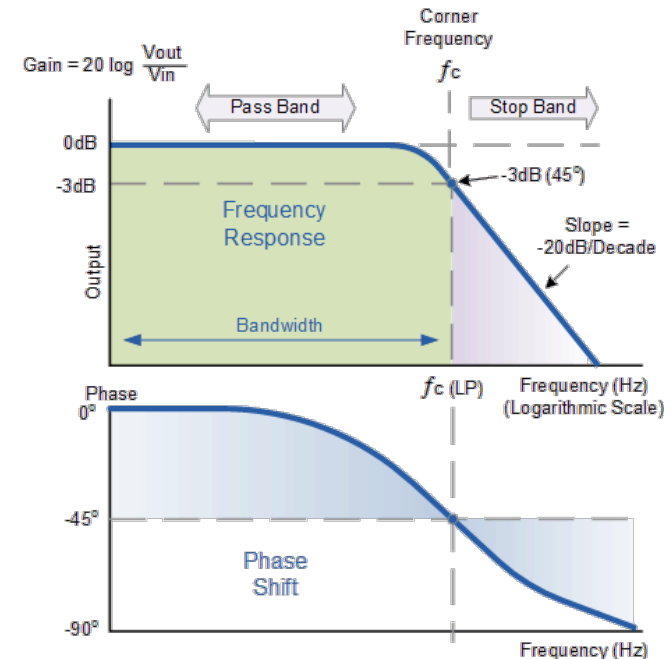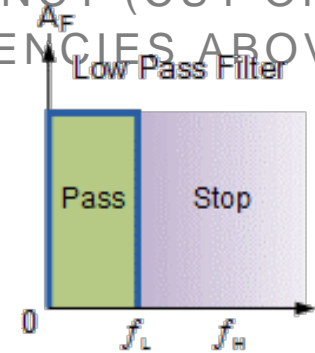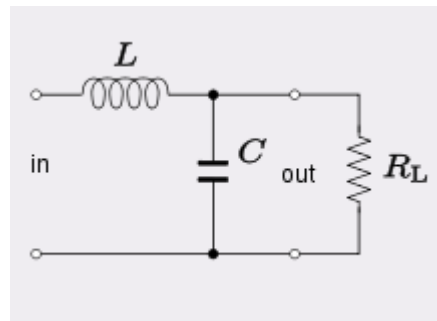


# TYPE OF FILTERS - HIGH PASS

- ❑ PASSES FREQUENCIES ABOVE A CERTAIN FREQUENCY (CUT OFF FREQUENCY) AND REJECTS (ATTENUATES) FREQUENCIES BELOW THE CUT OFF FREQUENCY


- ❑ EXAMPLE:

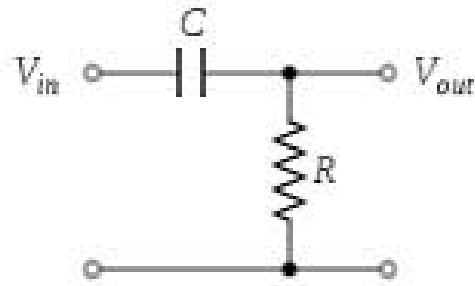

- ❑ FIRST ORDER

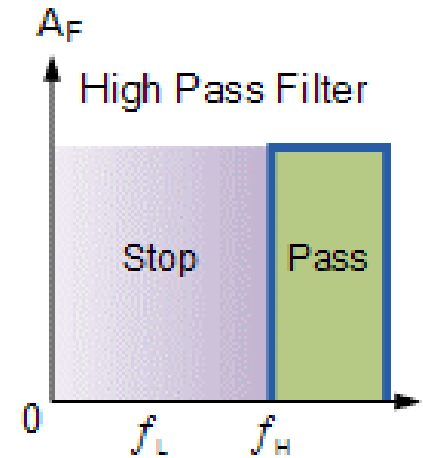


- ❑ SECOND ORDER

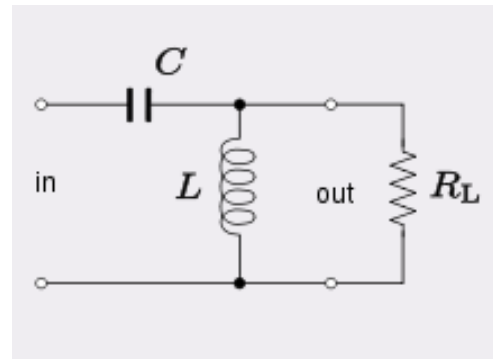


# TYPE OF FILTERS - BAND PASS

- ❑ PASSES FREQUENCIES WITHIN A CERTAIN RANGE AND REJECTS (ATTENUATES) FREQUENCIES OUTSIDE THAT RANGE

- ❑ EXAMPLE:

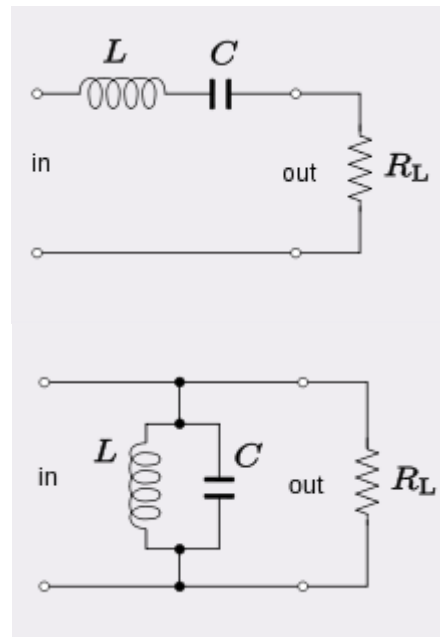

- ❑ SECOND ORDER

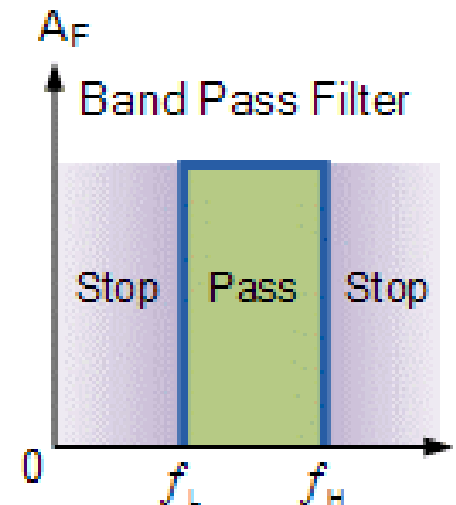





# TYPE OF FILTERS - BAND STOP (NOTCH)

- ❑ PASSES FREQUENCIES OUTSIDE A CERTAIN RANGE AND REJECTS (ATTENUATES) FREQUENCIES OUTSIDE THAT RANGE

- ❑ EXAMPLE:

- ❑ SECOND ORDER

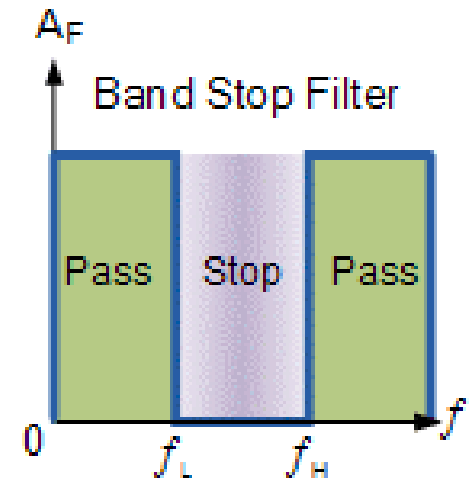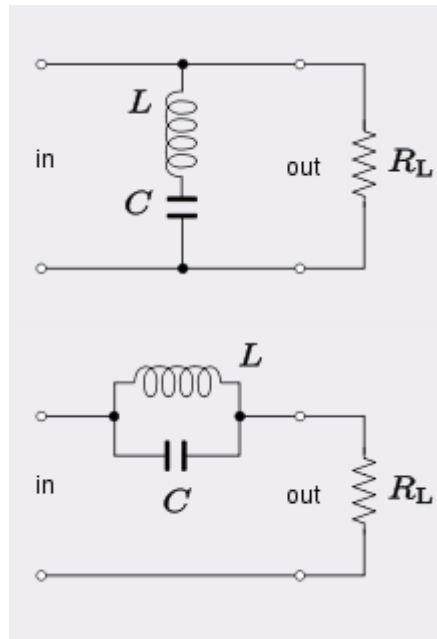

# OUTLINE

- ❑ VOLTAGE MEASUREMENT METHODS
- ❑ CURRENT MEASUREMENT METHODS
- ❑ GALVANIC ISOLATION
- ❑ PROTECTION
- ❑ ANALOGUE-TO-DIGITAL CONVERSION
- ❑ FILTERING (DIGITAL AND/OR ANALOGUE)



# EXERCISE

□ ON MOODLE

