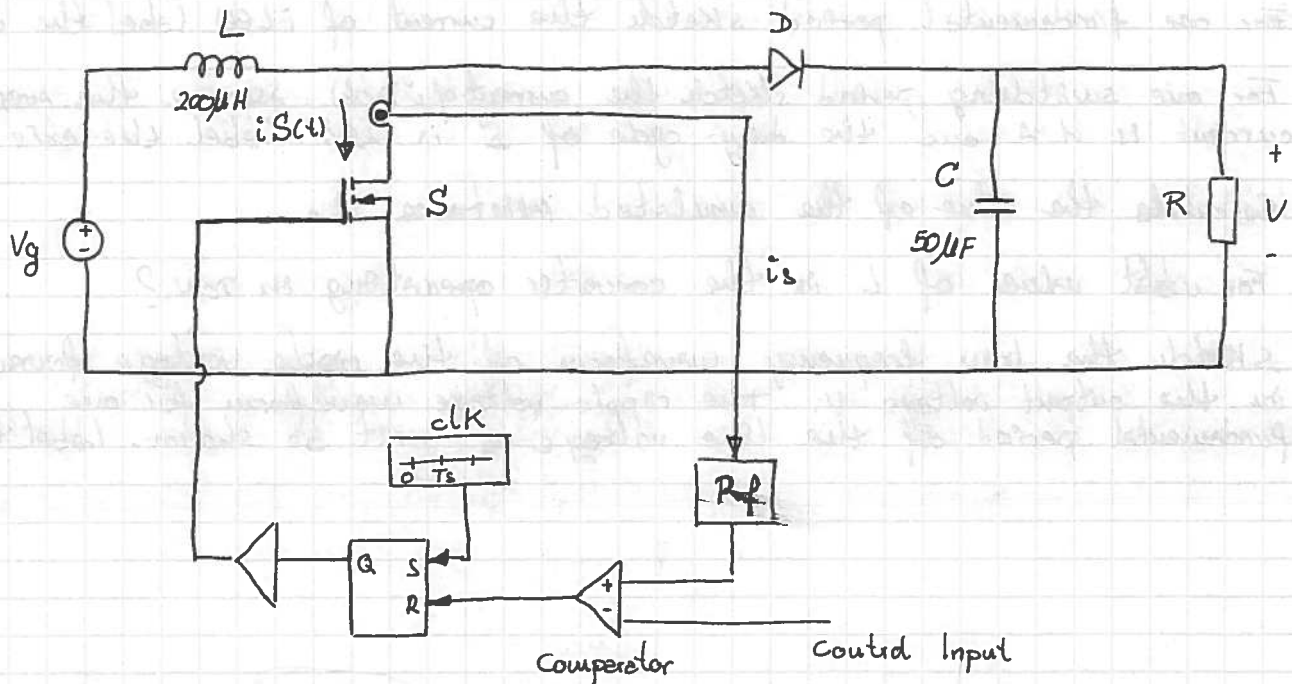


EXERCISE 2 (Switch mode)

Current Programmed Control of Boost converter, operation steady-state!



$$T_s = 10 \mu s, R = 20 \Omega$$


$$V_g = 20V, V = 100V, R_f = 1 \Omega$$

Assume ideal components (\Rightarrow no power loss in power conversion)

a) Calculate the average current of the switch S

b) Add a stabilizing ramp and calculate the minimum slope of the artificial ramp m_a that will give stability

Design a boost converter,

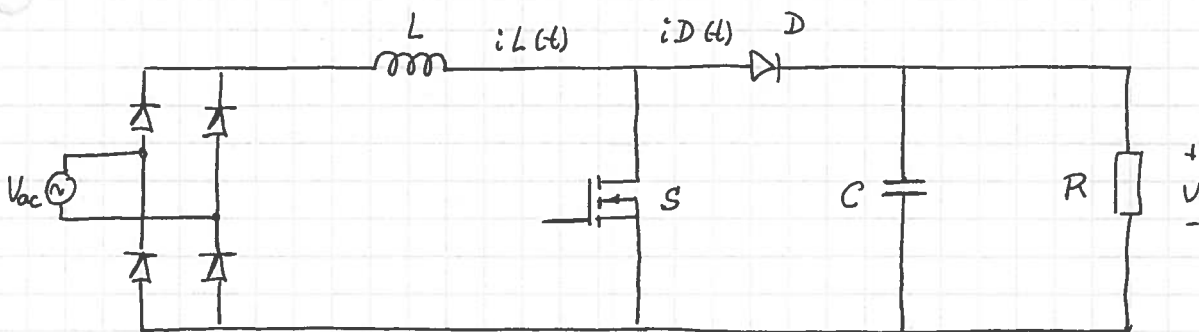

Specification:

Output voltage 390V

Output power 500W

Rms input voltage 230V

Efficiency 0.95

Fundamental frequency 50Hz

Switching frequency 100kHz

In question 2, b assume converter operate CCM and switching frequency ripple current in L is very small - so small you may ignore it.

- For one fundamental period sketch the current of $i_L(t)$ label the axes.
- For one switching period sketch the current of $i_D(t)$ assume the average current is 1 A and the duty-cycle of S is 25% . Label the axes.
- Calculate the value of the emulated resistance R_e .
- For what values of L is the converter operating in CCM?
- Sketch the low frequency waveform of the ripple voltage found on the output voltage V . The ripple voltage waveform for one fundamental period of the line voltage ~~is~~ must be shown. Label the axes.

- EXAM -

EXERCICE 2

Boost

a) $\langle I_a \rangle = D \langle I_L \rangle$

$$D = \frac{V_o - V_g}{V_o} = \frac{100 - 20}{100} = 0.8$$

$$\langle I_L \rangle = \frac{P_o}{V_g} = \frac{500}{20} = 25 \text{ A}$$

$$\langle I_a \rangle = 0.8 \cdot 25$$

$$\boxed{\langle I_a \rangle = 20 \text{ A}}$$



$$P_i = V_g \langle i_L \rangle$$

$$P_o = \frac{V_o^2}{R} = \frac{100^2}{20} = 500 \text{ W}$$

$$P_i = P_o$$

$$\langle i_L \rangle = \frac{500}{V_g}$$

b)

$$1 = \frac{m_2 - m_1}{m_1 + m_2} \cdot |\alpha| \quad (\text{stable } |\alpha| < 1) \quad (\text{Slide 15})$$

For a boost
(Slide 5 T-1)

$$\left\{ \begin{array}{l} m_1 = \frac{V_g}{L} = \frac{20}{200 \cdot 10^{-6}} = 0.1 \frac{\text{A}}{\mu\text{s}} \\ m_2 = -\frac{V_g - V_o}{L} = -\frac{20 - 100}{200 \cdot 10^{-6}} = 0.4 \frac{\text{A}}{\mu\text{s}} \end{array} \right.$$

$$\text{So: } m_1 + m_2 = m_2 - m_1 \Rightarrow m_1 = \frac{m_2 - m_1}{2} = \frac{0.4 - 0.1}{2} = 0.15 \frac{\text{A}}{\mu\text{s}}$$

$$|\alpha| < 1 \Rightarrow \boxed{m_1 \geq 0.15 \frac{\text{A}}{\mu\text{s}}}$$

- EXAM -

EXERCISE 3

Boost

$$\left. \begin{array}{l} V_o = 300 \text{ V} \quad P_o = 500 \text{ W} \\ V_g = 230 \text{ V}_{\text{rms}} \quad f = 50 \text{ Hz} \end{array} \right\} \eta = \frac{P_o}{P_i} = 0.95$$


$$f_s = 100 \text{ kHz} \Rightarrow T_s = 10^{-5} \text{ s}$$

a) sketch $i_L(t)$ - $i_L(t) = i_{ac}(t)$

$$i_{ac} = \frac{P_{ac}}{V_{ac}} = \frac{500/0.95}{230} = 2.29 \text{ A}_{\text{rms}}$$

$$f_1 = 50 \text{ Hz} \Rightarrow T_1 = \frac{1}{50} \text{ s}$$

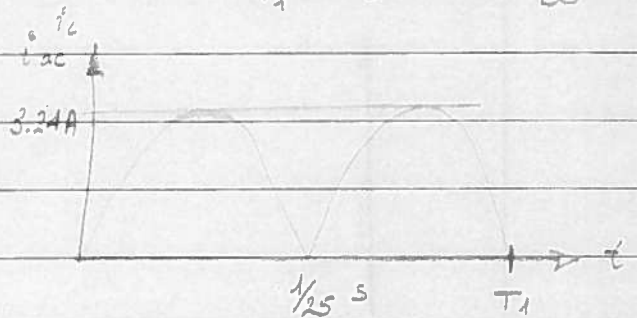
$$\tilde{i}_{ac} = \sqrt{2} \cdot i_{ac \text{ rms}} = 3.24 \text{ A}$$



b) $T_s \Rightarrow i_D(t)$ $\langle i_D \rangle = 1 \text{ A}$ $D = 25\%$

$$D = \frac{t_{on}}{T_s} \Rightarrow t_{on} = 0.25 T_s$$

$$t_{off} = 0.75 T_s$$

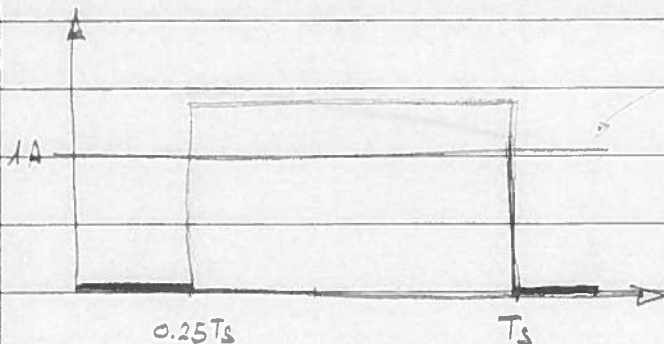

$$\langle i_D \rangle = 0.25 + 0.75 \cdot i_{D \text{ max}} = 1$$

$$i_{D \text{ max}} = \frac{1}{0.75} = 1.33 \text{ A}$$

c) R_e


$$R_e = \frac{V_g}{I_g} = \frac{230}{2.29} = 100.5 \Omega$$

d) Values of L for DCM -

$$\text{For DCM } R_e > \frac{2L}{T_s \left(1 - \frac{V_i(\text{peak})}{V_o}\right)} \Rightarrow L < \frac{R_e \cdot T_s \left(1 - \frac{V_i}{V_o}\right)}{2}$$

$$L < \frac{100.5 \cdot 10^{-5} \left(1 - \frac{230\sqrt{2}}{340}\right)}{2} = 83.4 \mu\text{F}$$

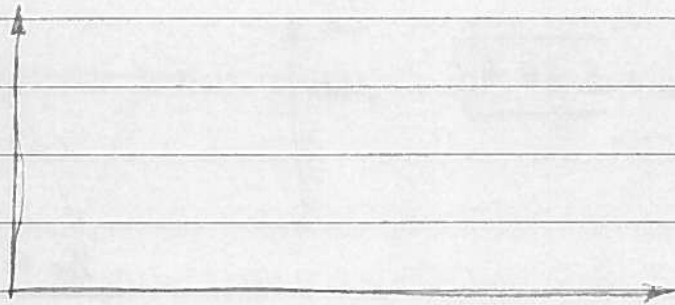e) Low frequency waveform of the ripple voltage in the output



$$V_o = \frac{1}{C} \int i_o dt$$

Exercise 2

wee

VESTAS & FAST PADS

a)

$$I_R = \frac{V}{R}$$

$$I_R = \frac{100}{20} = \underline{5A}$$

$$P_{out} = I_R V$$

$$P_{out} = 5 \cdot 100 = 500W$$

$$I_L = \frac{P_g}{V_g}$$

$$I_L = \frac{500}{20} = \underline{25A}$$

$$V = V_g \frac{1}{1-D}$$

$$V - VD = V_g \quad D = \frac{V - V_g}{V}$$

$$I_g = D \cdot I_L$$

$$D = \frac{100 - 20}{100}$$

$$I_g = 0.8 \cdot 25$$

$$\underline{\underline{D = 0.8}}$$

$$\underline{\underline{I_g = 20A}}$$

b)

$$m_1 = \frac{V_g}{L}$$

$$m_2 = \frac{V - V_g}{L}$$

$$m_2 = \frac{100 - 20}{200e-6}$$

$$m_1 = \frac{20}{200e-6}$$

$$m_2 = 0.4A/\mu s$$

$$m_1 = 0.1A/\mu s$$

$$a = - \frac{m_2 - m_1}{m_1 + m_2}$$

 $|a| < 1 \Rightarrow$ stable converter.

$$-1 = - \frac{m_2 - m_1}{m_1 + m_2}$$

$$m_1 + m_2 = m_2 - m_1$$

$$m_1 = \frac{m_2 - m_1}{2}$$


$$\underline{\underline{m_1 \geq 0.15 A/\mu s}} \Leftarrow$$

$$m_2 \geq \frac{0.4A/\mu s - 0.1A/\mu s}{2}$$


Exercise 3 : Design a boost converter.

a) $P_{ac} = \frac{500W}{0.95}$ $I_{ac} = \frac{P_{ac}/W}{V_{ac}}$ $I_{ac} = \frac{500/0.95}{230}$

$\hat{I}_{ac} = 3.2A$ $I_{ac} = 2.29A$

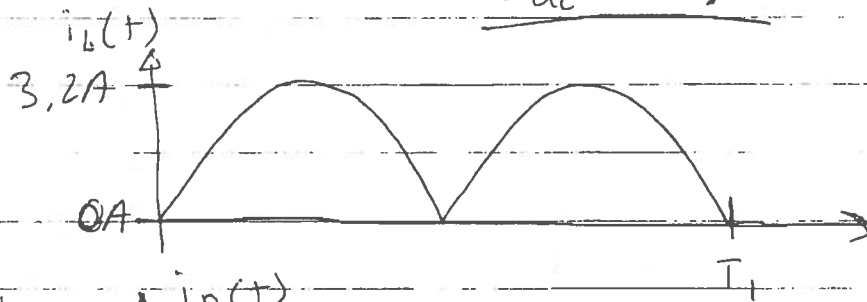

$f_s = \frac{1}{T_s} = 50kHz$

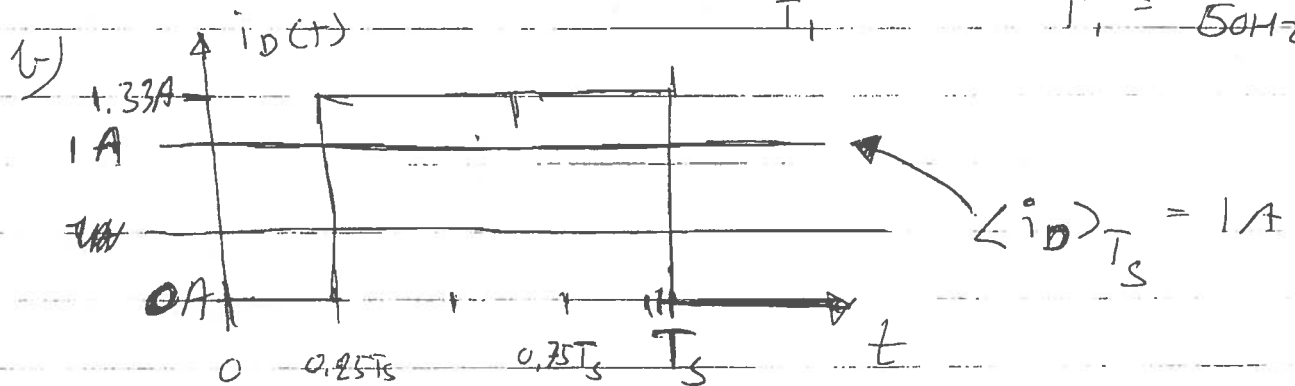

$\hat{I}_D \cdot 0.75 = 1$ $\hat{I}_D = \frac{4}{3}A$ $\hat{I}_D = 1.33A$

c) $R_e = \frac{V_{ac}}{I_{ac}}$ $R_e = \frac{230}{2.29}$ $R_e = 100.5 \Omega$

d) DCM mode $R_e > 2L / T_s (1 - \frac{V_m}{V})$

$R_e T_s (1 - \frac{V_m}{V}) > 2L$


$L < \frac{1}{2} R_e T_s (1 - \frac{V_m}{V})$

$L < \frac{1}{2} \cdot 100.5 \cdot 10\mu s (1 - \frac{230 - \sqrt{2}}{390})$

Cont : Exercice 3 Design a boost converter

$L < 83 \mu H$

e)

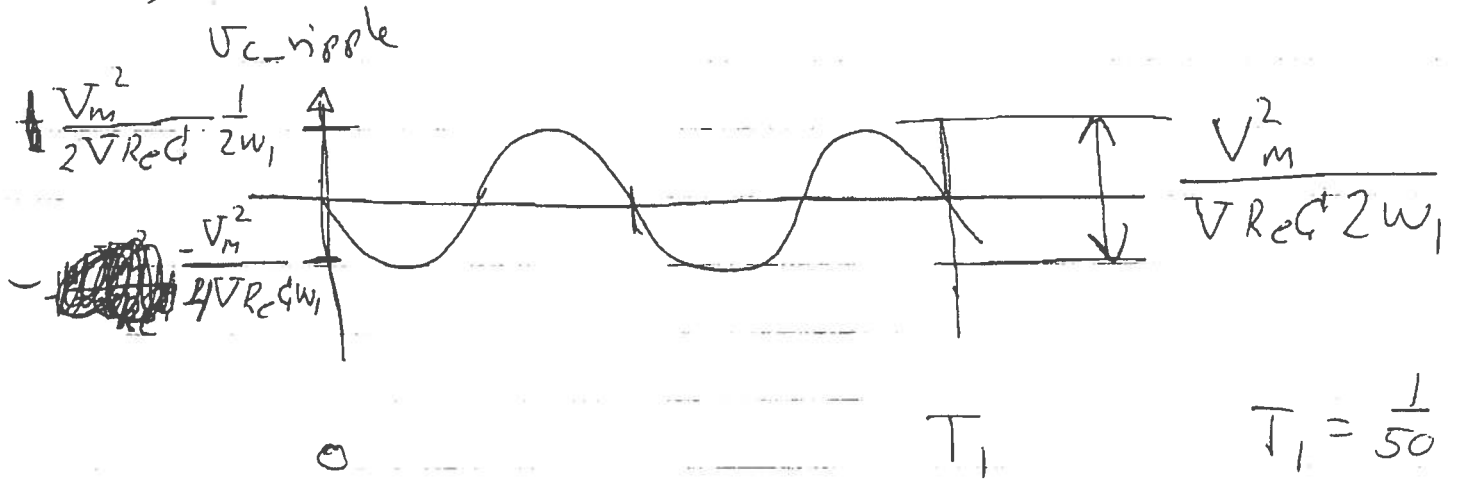

$$\underline{i_c = -\frac{V_m^2}{2VRe} \cos(2\omega t)}$$

$$V_{c_ripple} = \frac{1}{C} \int i_c dt$$

$$V_{c_ripple} = -\frac{V_m^2}{2VRe C' 2w_1} \sin(2\omega_1 t)$$

