

Dynamic modeling of electric machines


Kaiyuan Lu

Lecture 1 - content

Introduction & dynamic modeling of transformer

- Introduction – why dynamic modeling? How?
- Case study - transformer
 - How to model?
 - How to solve?

Introduction – why dynamic modeling?

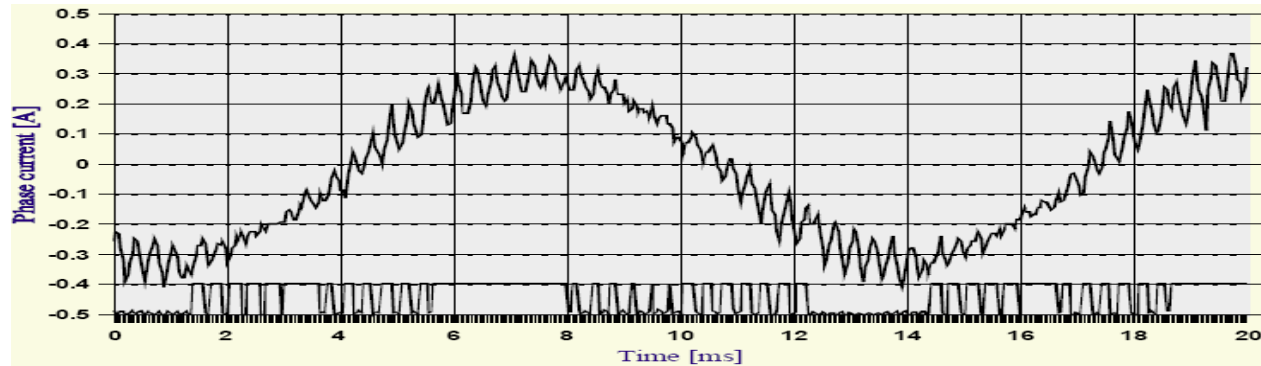

PWM voltage and current

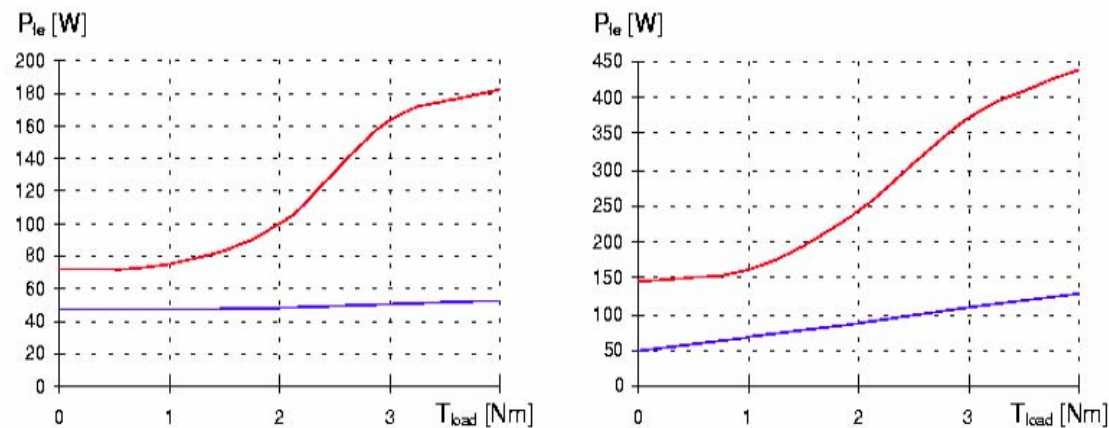


Figure 7.11 Comparison of calculated iron losses as function of the load for sinusoidal voltage, blue, and PAM-voltage, red. To the left for $f = 30$ Hz, To the right for $f = 50$ Hz.



Introduction – why dynamic modeling?

- Torque transient response, interested for dynamic performance of a motor drive system
- Transient current analysis, - detection of the dangerous peak current
- Dangerous situations, e.g. winding short-circuited of a generator
-

A dynamic model is a more ‘general’ model than the steady-state model

Understanding dynamic modeling case study – transformer

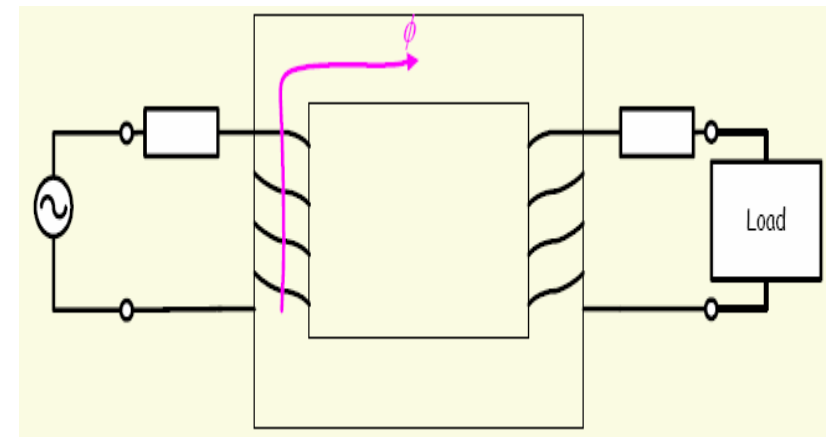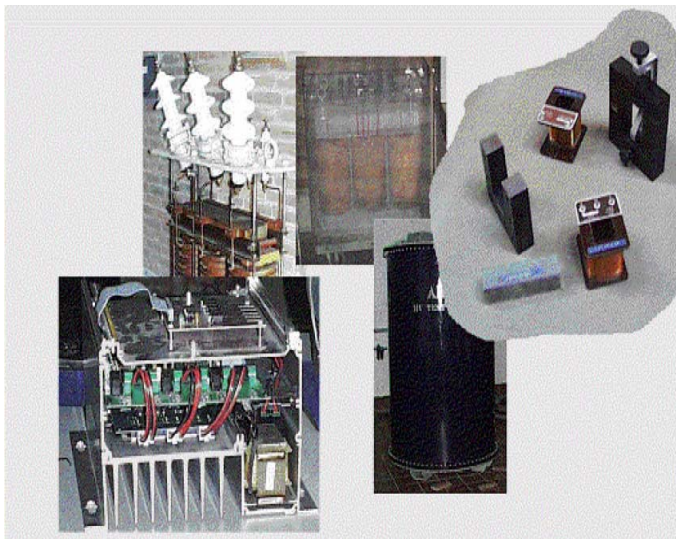- Transformer is an analog to the Induction Motor
- Cover some of the important issues regarding motor modeling



‘modeling’ – what we are looking for?

Equations linking terminal voltage and line current

For ANY electromagnetic devices, a general equation can always be written as

$$v = Ri + \frac{d\lambda}{dt}$$



Our task is to find how the flux linkage is obtained.

Remember, flux linkage is often linked to the inductance

$$\lambda = L_{11}i_1 + M_{12}i_2 + \dots$$


Find parameters based on the flux pattern

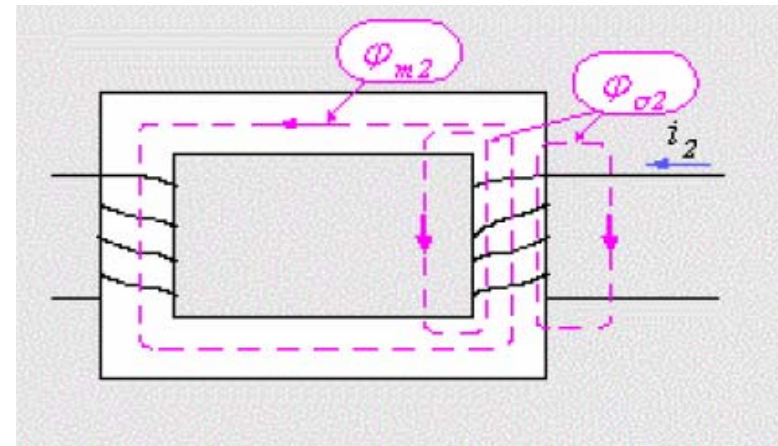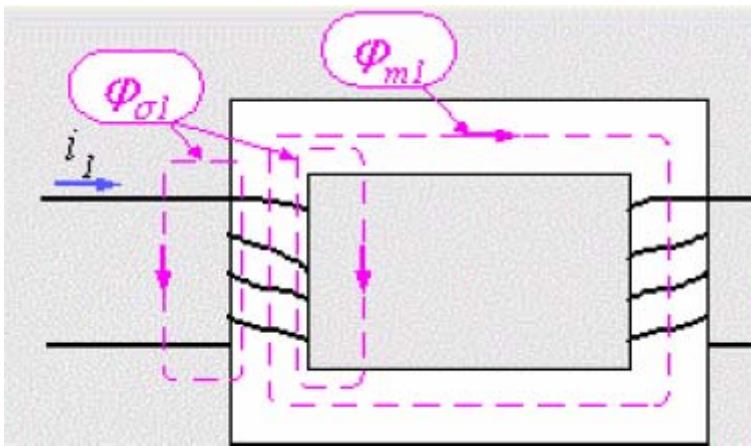- Mutual inductance (M) \ll flux linking both windings
- magnetization inductance (L_m) \ll flux linking both windings
- Leakage inductance (L_σ) \ll flux traveling in the air
- Winding inductance (self-inductance) $L = L_\sigma + L_m$
- $L_m = M$ only valid when both windings have 1-turn only




FE modeling of a transformer – observe the leakage flux

At no-load (Primary 25 A)

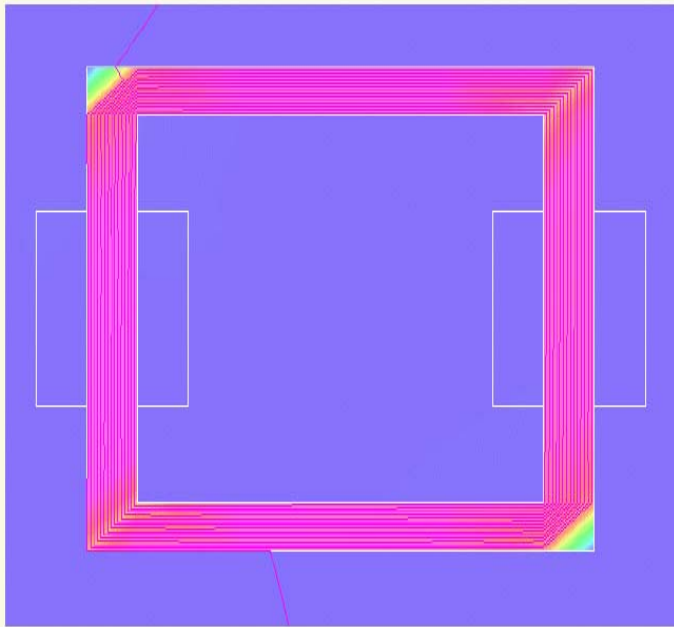


Component: BMOD (TIME=0.0)
3.1973E-05 0.762034 1.524036

Short-circuited (Primary 25 A)

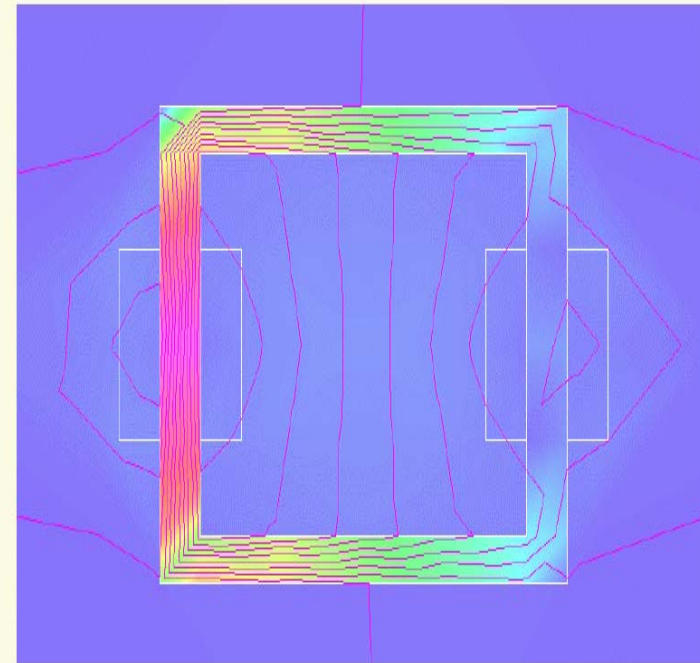

Component: BMOD (TIME=0.0)
6.0148E-05 0.0625627 0.125065

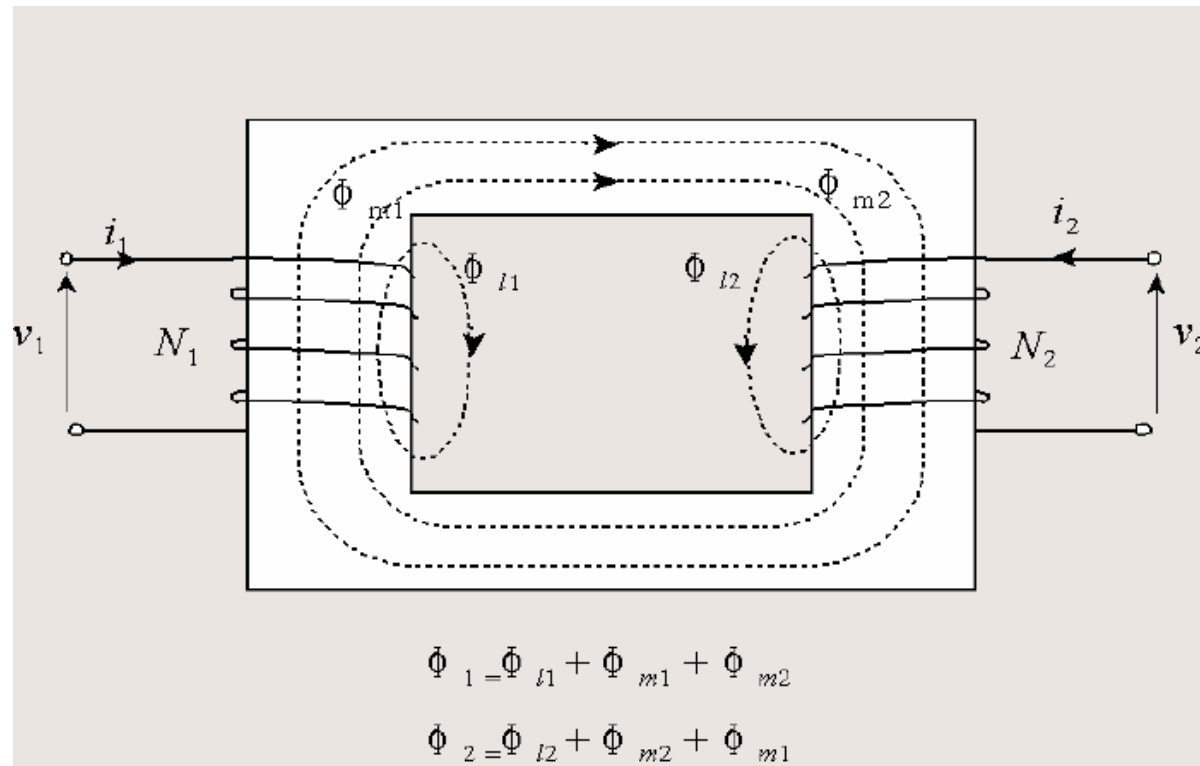Transformer – how the windings are coupled



Don't forget how the positive directions are defined!

Very important – flux linkage expression is based on the positive directions defined!

Step. 1 define all the voltage, current, and flux positive directions

Step. 2 Write down the flux linkage expression for each winding


E.g. winding 1

When no current in winding 2.
winding 1 carries positive current

$$\phi_1 = \phi_{l1} + \phi_{m1}$$

Flux linkage becomes

$$\lambda_1 = N_1 \phi_1$$

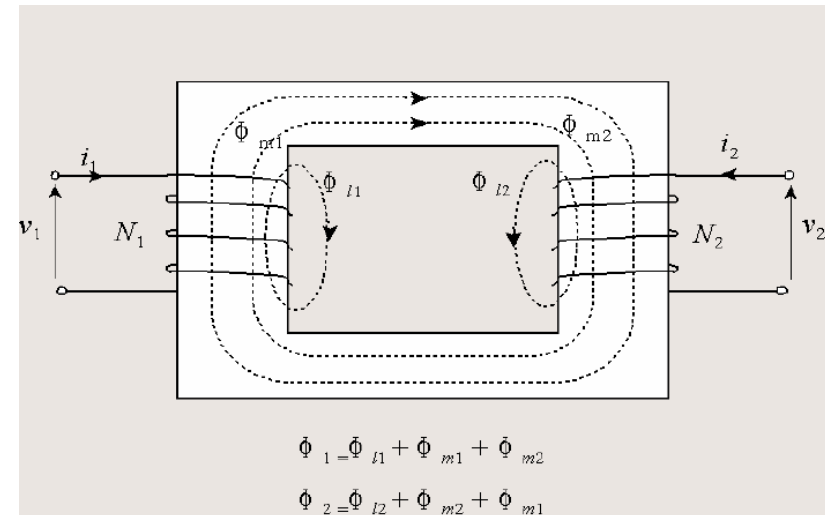

Very important – flux linkage expression is based on the positive directions defined!

Each flux linkage corresponds to an inductance

$$\lambda_1 = N_1 \phi_1 = N_1 \phi_{l1} + N_1 \phi_{m1} = L_{1\sigma} i_1 + L_{m1} i_1$$

$$L_{1\sigma} = \frac{N_1 \phi_{l1}}{i_1} \quad L_{m1} = \frac{N_1 \phi_{m1}}{i_1} \quad \text{Defined!}$$

Then no winding 1 current, but winding 2 carries current


$$\phi_1 = \phi_{m2}$$

Flux linkage becomes

$$\lambda_1 = N_1 \phi_1 = N_1 \phi_{m2}$$

The corresponding inductance
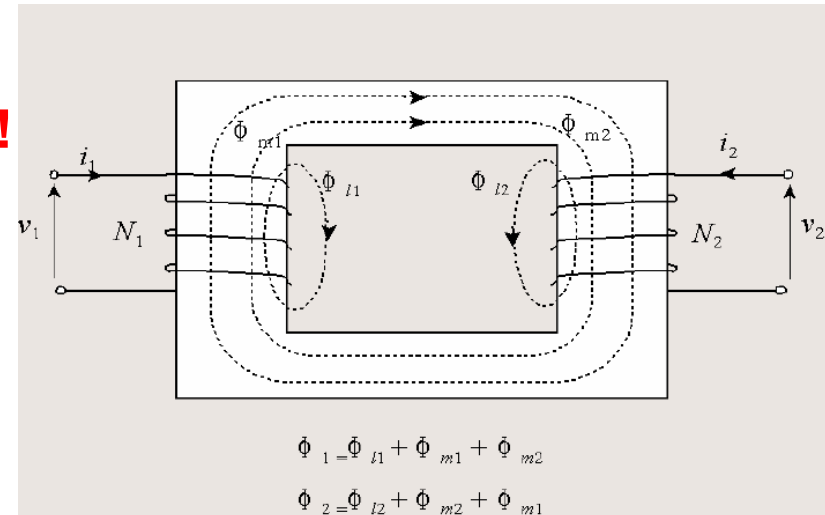
$$\lambda_1 = N_1 \phi_1 = N_1 \phi_{m2} = M i_2$$



$$M = \frac{N_1 \phi_{m2}}{i_2}$$

Very important – flux linkage expression is based on the positive directions defined!

When both windings (1 and 2) carry current, we have

$$\lambda_1 = L_{1\sigma} i_1 + L_{m1} i_1 + M i_2$$



$$L_{11} = L_{1\sigma} + L_{m1}$$

Defined!

Winding 1 self inductance

$$\lambda_1 = L_{11} i_1 + M i_2$$

Similarly, we can write down the flux linkage expression for winding 2

$$\lambda_2 = L_{22} i_2 + M i_1$$

What if we change the winding configuration?

Number of turns vs. inductance

We have

$$L_{m1} = \frac{N_1 \phi_{m1}}{i_1}$$



Double the number of turns

$$L_{m1,new} = \frac{2N_1 \phi_{m1}}{\boxed{i_1/2}} \quad \Rightarrow \quad L_{m1,new} = 2^2 \frac{N_1 \phi_{m1}}{i_1} = 2^2 L_{m1}$$



Half of the line current is needed in order to produce the same flux ϕ_{m1}

Inductance is proportional to square of the number of turns

Number of turns vs. inductance

Mutual inductance

$$M = \frac{N_1 \phi_{m2}}{i_2}$$

Double the number of turns of winding 2

$$M_{new} = \frac{N_1 \phi_{m2}}{i_2/2} \Rightarrow M_{new} = 2 \frac{N_1 \phi_{m2}}{i_2} = 2M$$

Half of the line current is needed in order to produce the same flux ϕ_{m1}


Double the number of turns of winding 1

$$M_{new} = \frac{2N_1 \phi_{m2}}{i_2} = 2M$$


Therefore $M \propto N_1 N_2$

Ideal transformer

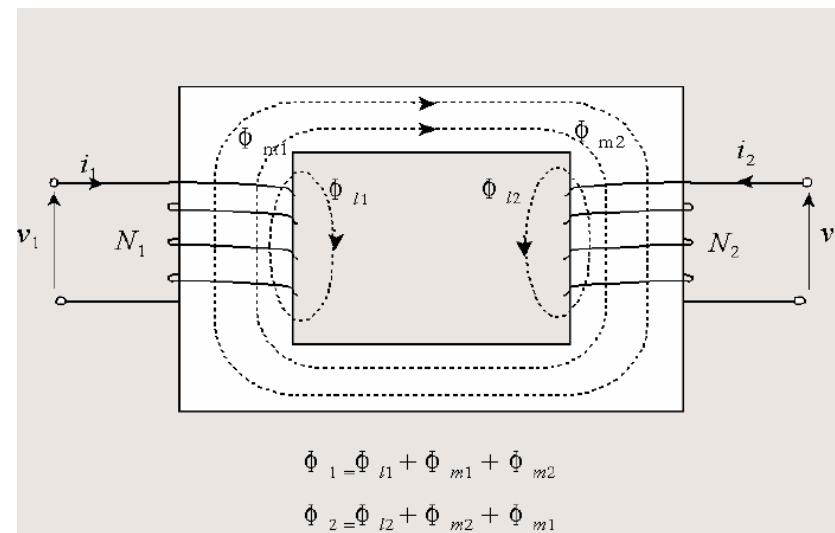- No leakage flux
- Winding resistance is small and may be neglected
- Core loss is small and may be neglected
- Permeability of the core is very high - MMF to establish the field is neglected



Ideal transformer

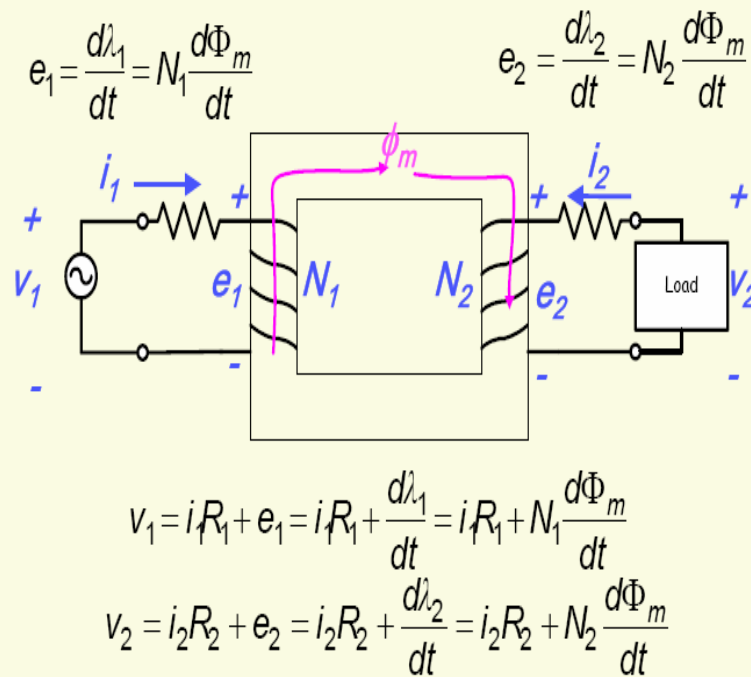

$$\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{N_1}{N_2} \quad v_1 = \frac{N_1}{N_2} v_2$$

$$F = N_1 i_1 + N_2 i_2 = 0$$

$$-i_1 = \frac{N_2}{N_1} i_2$$

$$v_1 i_1 = v_2 i_2$$

Transformer – differential equations

- Important but different concepts – flux vs. flux linkage
- The voltage differential equations

$$v_1 = R_1 i_1 + \frac{d\lambda_1}{dt}$$

$$\lambda_1 = L_{11} i_1 + M i_2$$

$$v_2 = R_2 i_2 + \frac{d\lambda_2}{dt}$$

$$\lambda_2 = L_{22} i_2 + M i_1$$

$$L_{11} = L_{m1} + L_{1\sigma} = N_1^2 L_{sgl} + L_{1\sigma}$$

$$L_{22} = L_{m2} + L_{2\sigma} = N_2^2 L_{sgl} + L_{2\sigma}$$

$$M = N_1 N_2 L_{sgl}$$

$$L_{sgl} = \frac{\Phi}{I_{tol}}$$

Modeling techniques using Matlab/Simulink - basics

How to solve differential equations?

- A Matlab M-file example (can be found in the help documents)

$$\begin{aligned}y_1' &= y_2 y_3 & y_1(0) &= 0 \\y_2' &= -y_1 y_3 & y_2(0) &= 1 \\y_3' &= -0.51 y_1 y_2 & y_3(0) &= 1\end{aligned}$$

```
options = odeset('RelTol',1e-4,'AbsTol',[1e-4 1e-4 1e-5]);  
[T,Y] = ode45(@rigid,[0 12],[0 1 1],options);
```


```
function dy = rigid(t,y)  
dy = zeros(3,1); % a column vector  
dy(1) = y(2) * y(3);  
dy(2) = -y(1) * y(3);  
dy(3) = -0.51 * y(1) * y(2);
```

Modeling techniques using Matlab/Simulink - basics

It might be easier to build a Simulink model

- Always try to use integrator block instead of derivative block!
- Define the input and output variables
- Change the differential equation as follow:
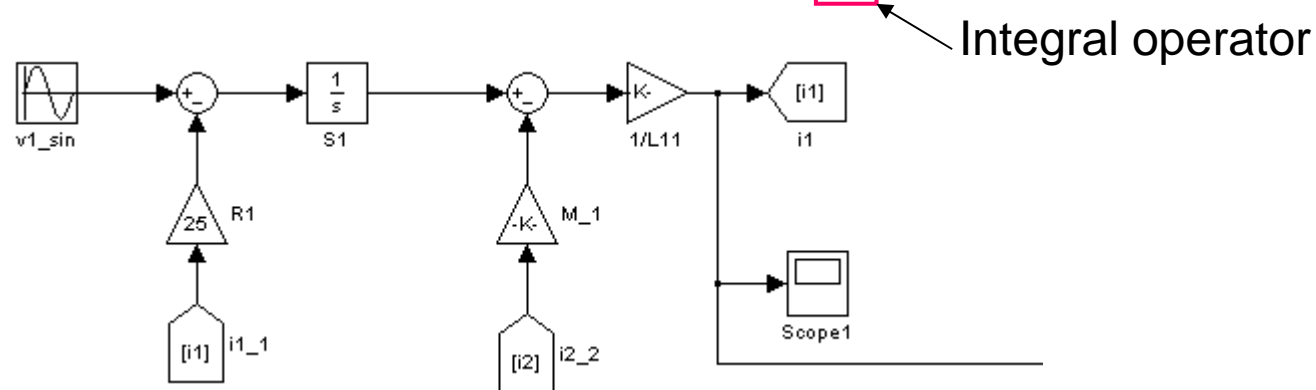
$$v_1 = R_1 i_1 + \frac{d\lambda_1}{dt} \quad \Rightarrow \quad (v_1 - R_1 i_1) \cdot \boxed{\frac{1}{s}} = \lambda_1 = L_{11} i_1 + M i_2$$



Understanding the turns ratio transformation

- Why?

- Defining a 'main inductance'

$$L_m = N_1^2 L_{sgl}$$

$$L_{11} = L_m + L_{1\sigma} \quad L_{22} = \left(\frac{N_2}{N_1}\right)^2 L_m + L_{2\sigma} \quad M = L_m \frac{N_2}{N_1}$$

$$\begin{aligned} \lambda_2 &= L_{2\sigma} i_2 + \left(\frac{N_2}{N_1}\right)^2 L_m i_2 + \frac{N_2}{N_1} L_m i_1 \\ \lambda'_2 &= \frac{N_1}{N_2} \lambda_2 = \frac{N_1}{N_2} L_{2\sigma} i_2 + L_m \left(\frac{N_2}{N_1} i_2\right) + L_m i_1 \\ \lambda'_2 &= L'_{2\sigma} i'_2 + L_m i'_2 + L_m i_1 \end{aligned}$$

$$\begin{aligned} L'_{2\sigma} &= \left(\frac{N_1}{N_2}\right)^2 L_{2\sigma} \\ i'_2 &= \frac{N_2}{N_1} i_2 \end{aligned}$$

Understanding the turns ratio transformation

$$\lambda_1 = L_{1\sigma} i_1 + L_m i_1 + L_m i_2'$$

$$\lambda_2' = L_{2\sigma}' i_2' + L_m i_2' + L_m i_1$$

$$v_1 = R_1 i_1 + \frac{d\lambda_1}{dt}$$

$$v_2' = R_2' i_2' + \frac{d\lambda_2'}{dt}$$

$$v_2' = \frac{N_1}{N_2} v_2 = \frac{N_1}{N_2} R_2 \frac{N_1}{N_2} \left(\frac{N_2}{N_1} i_2 \right) + \frac{d\lambda_2'}{dt}$$

$$L_{2\sigma}' = \left(\frac{N_1}{N_2} \right)^2 L_{2\sigma}$$

$$R_2' = \left(\frac{N_1}{N_2} \right)^2 R_2$$

$$i_2' = \frac{N_2}{N_1} i_1$$

$$v_2' = \frac{N_1}{N_2} v_2$$

$$\lambda_2' = \frac{N_1}{N_2} \lambda_2$$

Excises

- Build a Simulink model to solve the differential equation governing a R-L circuit with sinusoidal excitation. Assume: $R = 0.9$; $L=0.0021$; Input voltage: $V_{pk}=100$ (V), $f=50$ (Hz).
- Build a Simulink model to model a single phase transformer, described by the following differential equations:

$$v_1 = R_1 i_1 + \frac{d\lambda_1}{dt}$$

$$v_2 = -R_2 i_2 + \frac{d\lambda_2}{dt}$$

$$\lambda_1 = L_{11} i_1 - M i_2$$

$$\lambda_2 = -L_{22} i_2 + M i_1$$

- How the positive directions are defined for the voltage and current on the secondary side?
1. Assuming the secondary is short-circuited
 2. Assuming the secondary output is connected to a R-L load. How this load may be connected to the transformer model?

Parameters for the transformer are given in the next page.

Excises

```

Omega = 2*pi*50;           %primary side angular frequency

Nratio = 10;               % Turns ratio, primary vs. secondary

R1 = 0.72;                 % Primary resistance
L1lk = 0.92/Omega;         % Primary leakage inductance
L1m = 4370/Omega;          % Primary magnetizing inductance
L11 = L1m+L1lk;            % Primary total inductance

R2 = 0.007;                % Secondary resistance
L2lk = 0.009/Omega;        % Secondary leakage inductance
L2m = 43.7/Omega;          % Secondary magnetizing inductance
L22 = L2m+L2lk;            % Secondary total inductance

M = L1m/Nratio;            % Calculation of the mutual inductance

RL = 0.8962;               % Secondary load resistance
LL = 0.6721/Omega*0;       % Secondary load inductance

```